

Hall Ticket No

--	--	--	--	--	--	--	--	--	--

Question Paper Code: AEC002



INSTITUTE OF AERONAUTICAL ENGINEERING
(Autonomous)

B.Tech III Semester End Examinations (Supplementary) - January/February, 2018

Regulation: IARE – R16

DIGITAL SYSTEM DESIGN
(Electronics and Communication Engineering))

Time: 3 Hours

Max Marks: 70

Answer ONE Question from each Unit

All Questions Carry Equal Marks

All parts of the question must be answered in one place only

UNIT – I

1. (a) If a hamming code is constructed using even parity and the received code is 1110110. Detect and correct errors if any. [7M]
- (b) Convert the following into Excess-3 Code [7M]
 - i. $(4B9)_{16}$
 - ii. $(58)_{10}$
2. (a) Convert the following. [7M]
 - i. $(4C9)_{16} = ()_8$
 - ii. $(11011.11)_2 = ()_{10}$
- (b) Represent the following decimal numbers in BCD format [7M]
 - (i) 9
 - (iii) 25

UNIT – II

3. (a) Use the tabular method obtain the minimal expression for [7M]
 $F(A, B, C, D) = \sum m(0, 1, 5, 7, 8, 10, 14, 15)$
- (b) What are the limitations of K-Maps. [7M]
4. (a) Minimize the following expressions using K-Map and implement using logic gates. [7M]
 $F(A, B, C, D) = \sum(0, 1, 5, 7, 8, 10, 14, 15)$
- (b) Convert the following Sum of Product(SOP) to Product of Sums(POS) [7M]

$$F(A, B, C) = A'BC' + ABC + A'B'C + AB'C + ABC'$$

UNIT – III

5. (a) Design 3-bit binary to gray code converter using basic gates , NAND gates and NOR gates. [7M]
- (b) Design full adder combinational logic network using minimum number of NAND gates only. [7M]

6. (a) Design a combinational circuit whose output is true for two bit BCD input. [7M]
 (b) Design two bit BCD adder and explain its operation. [7M]

UNIT – IV

7. (a) Convert J-K Flip-Flop to S-R Flip-Flop. [7M]
 (b) With the help of logic Diagram and Functional Table explain the operation of 4-bit Johnson counter [7M]
8. (a) Sketch the logic networks for MOD-5 Johnson counter and explain its operation. [7M]
 (b) Design a Mod-6 Synchronous counter using clocked T flip-flops. [7M]

UNIT – V

9. (a) Differentiate between Mealy Machine and Moore Machine. [7M]
 (b) Minimize the State Table using Partition Technique as shown in Table-1 [7M]

Table 1

PS	NS,Z	
	X=0	X=1
A	E,0	D,1
B	F,0	D,0
C	E,0	B,1
D	F,0	B,0
E	C,0	F,1
F	B,0	C,0

10. (a) Write the state table for the state diagram shown in figure-1 [7M]

 


Figure 1

- (b) With an example, explain what is state reduction and also mention its advantages [7M]

