

--	--	--	--	--	--	--	--	--	--



# INSTITUTE OF AERONAUTICAL ENGINEERING

(Autonomous)

B.Tech IV Semester End Examinations (Supplementary) - July, 2018

Regulation: IARE – R16

## PULSE AND DIGITAL CIRCUITS

Time: 3 Hours

(ECE)

Max Marks: 70

Answer ONE Question from each Unit

All Questions Carry Equal Marks

All parts of the question must be answered in one place only

### UNIT – I

- Draw the output waveform of an high pass RC circuit excited by a square wave input under different time constants. Derive the expression for percentage of tilt. [7M]
  - Explain the types of series clippers with the neat circuit diagram and transfer characteristics. [7M]
- A square wave is applied to an low pass RC. Draw the output waveforms to scale the following cases i)  $T=RC$  ii)  $T \leq RC$  iii)  $T \geq RC$ . [7M]
  - With the neat circuit diagram and waveforms explain the operation of negative clamper. [7M]

### UNIT – II

- With a neat circuit diagram explain the operation of monostable multivibrator. [7M]
  - Design a bistable multivibrator to meet the following specifications,  $V_{CC} = V_{BB} = 12V$ ,  $I_C(\text{sat}) = 6\text{mA}$ ,  $h_{FE}(\text{min}) = 25$ , maximum triggering frequency = 25KHz. Assume  $V_{CE}(\text{sat}) = 0.4V$ ,  $V_{BE}(\text{sat}) = 0.8V$ ,  $I_B(\text{actual}) = 1.5I_B(\text{min})$ . [7M]
- Explain how the astable multivibrator circuit can act as a voltage to frequency converter. [7M]
  - Design a Schmitt trigger circuit using npn transistor for the following specifications  $V_{CC} = 15V$ ,  $I_C(\text{sat}) = 2\text{mA}$ ,  $U_{TP} = 8V$ ,  $L_{TP} = 5V$ ,  $h_{FE}(\text{min}) = 25$ . Assume  $V_T = 0.5V$  [7M]

### UNIT – III

- Explain the effects of control voltage on gate output of a unidirectional diode gate with neat sketches. [7M]
  - What are the methods of generating time base waveforms. Derive an expression for sweep speed error of exponential sweep circuit. [7M]
- With the circuit diagram explain the working of transistor boot strap sweep circuit. [7M]
  - Design a UJT sweep circuit with  $R_{B1} = R_{B2} = 0\Omega$ . The sweep amplitude is to be 10V. The sweep duration is 1ms sweep speed error is to be 10%, and the valley point voltage is 3V. Specify reasonable values for  $V_{BB}$ ,  $V_{YY}$ , R and C. [7M]

#### UNIT – IV

7. (a) What do you mean by relaxation circuit. Explain the principle of operation of sweep generator using UJT with neat sketches. [7M]
- (b) With the help of circuit diagram and waveforms explain frequency division by an astable multivibrator. [7M]
8. (a) Describe the method involved in synchronization of a sweep circuit with symmetrical signals with neat sketches. [7M]
- (b) With the neat sketch , explain the sine wave frequency division with a sweep circuit. [7M]

#### UNIT – V

9. (a) Draw and explain the two input TTL NAND gate with totem pole output. What are the advantages and disadvantages of totem pole. [7M]
- (b) Draw and explain the operation of ECL OR gate .What are the drawbacks of ECL family. [7M]
10. (a) Describe the operation of DTL NAND gate. Clearly mention the purpose served by the diodes D1 & D2. What are the conditions to be fulfilled for the output to be in saturation. [7M]
- (b) Draw the circuit of CMOS NOT gate and explain its operation . Mention the advantages over other digital logic families. [7M]

– ○ ○ ○ ○ –