

--	--	--	--	--	--	--	--	--	--



INSTITUTE OF AERONAUTICAL ENGINEERING

(Autonomous)

B.Tech IV Semester End Examinations (Supplementary) - July, 2018

Regulation: IARE – R16

DIGITAL AND PULSE CIRCUITS

Time: 3 Hours

(EEE)

Max Marks: 70

Answer ONE Question from each Unit

All Questions Carry Equal Marks

All parts of the question must be answered in one place only

UNIT – I

1. (a) State and prove De Morgan's theorem for 3 variables. [7M]
- (b) Perform the following operations [7M]
 - i) $(20.6875)_{10} = (?)_8$
 - ii) $(DF8.28)_{16} = (?)_{10}$
 - iii) $(2536)_{10} = (?)_{16}$
2. (a) Perform the following operation using 2's complement method. [7M]
 - i) $(10.0101)_2 - (101.111)_2$
 - ii) $(28)_{10} - (19)_{10}$
- (b) Solve the following boolean function and represent it in minterm and maxterm canonical form. [7M]
 $f(x, y, z) = (XY + X'Z)' + YZ.$

UNIT – II

3. (a) Simplify the following function using Karnaugh map $Y = f(a, b, c, d) = \sum m(2, 3, 4, 5, 13, 15) + \sum d(8, 9, 10, 11)$ [7M]
- (b) Draw the logic diagram for 2:4 decoder with an active low enable and active high data outputs. Construct a truth table and identify the data inputs, enable input and the output. Describe the circuit function. [7M]
4. (a) Realize the following boolean function $f(w, x, y, z) = \sum m(0, 1, 4, 6, 7, 9, 11, 14, 15)$ using logic gates. [7M]
- (b) Perform the following to design a full subtractor [7M]
 - i. Construct the truth table and simplify the output equations
 - ii. Draw the resulting logic diagram.

UNIT – III

5. (a) What is the difference between a flip flop and a latch. Explain the operation of SR latch with a logic diagram and excitation table. [7M]
- (b) Design a synchronous Mod-6 counter using D flip flop and draw its logic diagram. [7M]

6. (a) Explain the operation of positive edge triggered JK flip flop with neat timing diagram. [7M]
 (b) Design a 3-bit binary ripple counter using T flip flop. [7M]

UNIT – IV

7. (a) Explain the effects of feedback on output impedance for current series and input impedance for current shunt feedback amplifier. [7M]
 (b) In a transistorized Hartely oscillator $L_1 = 0.5\text{mH}$, $L_2 = 0.5\mu\text{H}$ while the frequency has been changed from 100kHz to 2000kHz. Determine the range of capacitor. Assume mutual inductance is negligible. [7M]
8. (a) Derive the expression for frequency of a RC phase shift oscillator and also explain its principle of operation. [7M]
 (b) A voltage series feedback amplifier has $A = -100$, $R_i = 25\text{K}\Omega$, $R_o = 10\text{K}\Omega$ and feedback factor $\beta = -0.1$ [7M]
 i. Determine overall gain, input impedance and output impedance of feedback amplifier.
 ii. If the gain has been reduced to -2.5, what will be the feedback factor.

UNIT – V

9. (a) Draw and explain the two stage transformer coupled common emitter amplifier circuit. [7M]
 (b) In common collector configuration a transistor has the following parameters: $h_{ic} = 1.5\Omega$, $h_{rc} = 1$, $h_{fc} = -55$, $h_{oc} = 50 \times 10^{-6}$, $R_s = 1.5\text{k}\Omega$ and $R_L = 2\text{k}\Omega$. Determine the current gain, voltage gain, input impedance and output impedance. [7M]
10. (a) Explain the operation of emitter follower circuit using darlington connection. Derive the current gain expression of the same using small ac equivalent circuit. [7M]
 (b) Explain the effect of bypass capacitor at a low frequency response on a single stage CE amplifier. [7M]

