

--	--	--	--	--	--	--	--	--	--



INSTITUTE OF AERONAUTICAL ENGINEERING

(Autonomous)

Four Year B.Tech III Semester End Examinations(Regular) - November, 2019

Regulation: IARE – R18

BASIC ELECTRONICS ENGINEERING

Time: 3 Hours

(CE)

Max Marks: 70

Answer ONE Question from each Unit

All Questions Carry Equal Marks

All parts of the question must be answered in one place only

UNIT – I

1. (a) Explain the V-I Characteristics of Zener diode. [7M]
 (b) A Zener diode has an impedance of 40Ω in the range for $I_Z = 1\text{mA}$ to 10mA . The voltage corresponding to I_Z of 1mA is 9V . For constant impedance over the given range, what is the minimum & maximum zener voltages can be expected if the diode is used in an application where the zener current varies from 2mA to 8mA . [7M]
2. (a) Demonstrate the working of full wave rectifier capacitor filter. Derive the expression for rectifier efficiency. [7M]
 (b) A full wave rectifier having load resistance of 100Ω is fed with 220V , Assuming the diodes are ideal, Find the following terms i) DC output voltage ii) Peak inverse voltage iii) Rectifier efficiency. [7M]

UNIT – II

3. (a) Draw the input and output characteristics of CB Configuration and explain [7M]
 (b) Determine the collector current and emitter current for a transistor with $\alpha = 0.99$ and $I_{CBO} = 490\mu\text{A}$ when the base current is $19\mu\text{A}$? [7M]
4. (a) Explain the construction & operation of D- MOSFET. [7M]
 (b) The N-channel FET has a $|I_{DS}|=20\text{mA}$, $|V_p|=5\text{V}$, V_{GS} is -3V . Determine I_D , g_m and g_{m0} ? [7M]

UNIT – III

5. (a) Define slew rate. Obtain slew rate equation for op-amp voltage follower. [7M]
 (b) The input signal to an op-amp is $0.03\sin(1.5 \times 10^5 t)$. calculate maximum gain of an op-amp with the slew rate of $0.4\text{V}/\mu\text{sec}$. [7M]
6. (a) Explain the operation of inverting and non inverting comparator. [7M]
 (b) Design a comparator circuit for input voltage = $2V_{pp}$ sine wave at 1KHz , $V_{ref}=500\text{mV}$, $R=100\Omega$, and supply voltage = $\pm 15\text{V}$. Draw the output waveform [7M]

UNIT – IV

7. (a) Explain the operation of monostable multi vibrator using IC555 & obtain the expression for its pulse width. [7M]
(b) Illustrate the working of flash type analog to digital converter. [7M]
8. (a) Explain the operation of R/2R ladder type D/A Converter. [7M]
(b) Design an a stable multi vibrator for an output frequency of 1KHZ with a variable duty cycle of 30% to 70%. Assume $V_{CC} = 12V$. [7M]

UNIT – V

9. (a) Demonstrate the operation of 4 bit synchronous counter with necessary sketches [7M]
(b) Subtract using 2's complement method
i) $(101011)_2$ from $(111001)_2$
ii) $(10001)_2$ from $(11001)_2$ [7M]
10. (a) Draw and explain master-slave JK flipflop. [7M]
(b) Convert the following Hexadecimal numbers to their decimal equivalent $(EAF1)_{16}$ and $(AE1)_{16}$. [7M]