

--	--	--	--	--	--	--	--	--	--



# INSTITUTE OF AERONAUTICAL ENGINEERING

(Autonomous)

Four Year B.Tech III Semester End Examinations(Regular) - November, 2019

Regulation: IARE – R18

**ANALOG ELECTRONICS**

**Time: 3 Hours**

**(EEE)**

**Max Marks: 70**

**Answer ONE Question from each Unit**

**All Questions Carry Equal Marks**

**All parts of the question must be answered in one place only**

## UNIT – I

- Obtain the expressions for DC voltage, RMS voltage, ripple factor and rectification efficiency of half wave rectifier. [7M]
  - For a diode current of 1mA at room temperature a germanium diode requires forward bias of 0.1435 V and silicon diode requires forward bias of 0.718 V. Find the ratio of reverse saturation current in germanium diode to that in silicon diode? [7M]
- Analyze CE amplifier using simplified hybrid CE model and obtain all the characteristic parameters. [7M]
  - Consider a single stage CE amplifier with  $R_S = 1K\Omega$ ,  $R_E = 500\Omega$ ,  $R_C = 1K\Omega$ ,  $R_L = 1.2K\Omega$ ,  $h_{fe} = 50$  and  $h_{ie} = 1.1K\Omega$ ,  $h_{oe} = 2 \times 10^{-6}$  mhos,  $h_{re} = 0$ . Calculate current gain, input impedance and voltage gain? [7M]

## UNIT – II

- Explain the principle of common drain FET amplifier with the help of circuit diagram. Derive the expressions for input impedance, output impedance and  $A_V$ . [7M]
  - A common drain FET amplifier circuit has the following circuit parameters:  $R_S = 4k\Omega$ ,  $R_G = 10M\Omega$ ,  $\mu = 50$  and  $r_d = 35K\Omega$ . Determine  $A_V$  and  $Z_i$  and  $Z_o$ . [7M]
- With neat diagram, explain the construction and working principle of N-channel depletion type MOSFET. [7M]
  - A common source FET amplifier circuit with un bypassed  $R_s$  has the following circuit parameters:  $R_d = 15K$ ,  $R_S = 0.5K\Omega$ ,  $R_g = 1M$ ,  $r_d = 5K$ ,  $g_m = 5mS$  and  $V_{DD} = 20$  V. Determine  $A_V$  &  $R_O$ . [7M]

## UNIT – III

- Discuss the frequency response characteristics of RC coupled amplifiers. Obtain general expression for gain at a low and high frequencies [7M]
  - A single transistor is acting as ideal Class B amplifier with load of  $1K\Omega$ , if DC collector current is 15mA,  $V_{CC} = 20V$ . Determine its efficiency. [7M]

6. (a) Explain the operation of complementary symmetry push pull amplifier. [7M]  
 (b) Define power amplifier and explain different types of power amplifiers. [7M]

#### UNIT – IV

7. (a) Discuss with mathematical expressions, how the negative feedback in amplifiers increases bandwidth and reduces distortions in amplifiers. [7M]  
 (b) A Hartley oscillator is designed with  $L = 20\mu\text{H}$  and a variable capacitance. Find the range of capacitance values if the frequency of oscillation is varied between 950 KHz to 2050 KHz. [7M]
8. (a) Draw the circuit and explain the principle of operation of RC phase shift oscillator circuit. Derive the expression for the frequency of oscillations. [7M]  
 (b) Find the frequency of oscillations of a Wein bridge oscillator with  $R=20\text{K}\Omega$  and  $C=1000\text{pF}$ . [7M]

#### UNIT – V

9. (a) Explain the terms i) PSRR ii) CMRR iii) Slew rate iv) Input bias current [7M]  
 (b) An inverting amplifier using 741C must have a flat response upto 40KHz. The gain of the amplifier is 10. What maximum peak to peak input signal can be applied without distorting the output? Note: The 741C has typical slew rate of  $0.5\text{V}/\mu\text{s}$ . [7M]
10. (a) Explain the characteristics of an ideal operational amplifier. Draw the equivalent circuit and open loop circuit of an Ideal Op-amp. [7M]  
 (b) In circuit shown below  $R_1 = 10\text{K}\Omega$ ,  $R_f = 100\text{K}\Omega$ ,  $v_i = 1\text{V}$ . A load of  $25\text{K}\Omega$  is connected to the output terminal. Calculate  
 i)  $i_1$   
 ii)  $v_o$   
 iii)  $i_l$  and total current  $i_o$  in to the output pin. [7M]

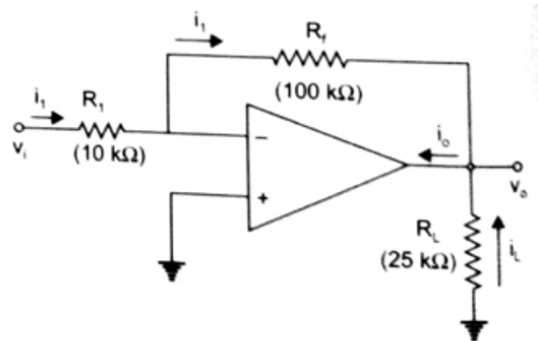


Figure 1