

Hall Ticket No

--	--	--	--	--	--	--	--	--	--

Question Paper Code: AECB03



INSTITUTE OF AERONAUTICAL ENGINEERING
(Autonomous)

Four Year B.Tech III Semester End Examinations(Regular) - November, 2019

Regulation: IARE – R18

DIGITAL ELECTRONICS

Time: 3 Hours

(EEE)

Max Marks: 70

Answer ONE Question from each Unit

All Questions Carry Equal Marks

All parts of the question must be answered in one place only

UNIT – I

1. (a) Define the following terms
i) Fan in
ii) Power Dissipation
iii) Propagation delay [7M]
(b) Construct 7 bit Hamming code using even parity for the message 0110. [7M]
2. (a) Explain the operation of TTL NAND gate. [7M]
(b) Add $(600)_{10} + (612)_{10}$ using BCD Arithmetic. [7M]

UNIT – II

3. (a) Design half adder and half subtracter circuit using NAND gates. [7M]
(b) Minimize the following function using K-map.
 $F(A, B, C, D) = \sum m(1,3,5,7,9,10,11,12,15)$ [7M]
4. (a) Differentiate between BCD and Gray code converters. Design BCD to gray code converter. [7M]
(b) Implement the following function with 8x1 MUX
 $F(A, B, C) = \sum m(0,2,6,7)$ [7M]

UNIT – III

5. (a) With the help of circuit diagram and functional table, explain the working of D flip-flop. [7M]
(b) Design a Mod-10 Asynchronous Counter using JK flip-Flop. [7M]
6. (a) Compare the asynchronous and synchronous counters. [7M]
(b) Draw the logic circuit of clocked SR flip-flop using NAND gates and explain its operation. [7M]

UNIT – IV

7. (a) Discuss the various specifications of digital to analog Converter. [7M]
(b) Explain the operation of successive approximation ADC with necessary diagrams. [7M]

8. (a) Explain the working of Sample and Hold circuit? [7M]
(b) With the help of circuit diagram and functional table, explain the working of Parallel Comparator A/D converter. [7M]

UNIT – V

9. (a) Demonstrate the organization of ROM and illustrate the features of a ROM cell? [7M]
(b) Implement the combinational circuit with a PLA having 3 inputs, 4 product terms and 2 outputs for the functions.
 $F1 = \sum m(3,5,6,7)$; $F2 = \sum m(0,2,4,7)$ [7M]
10. (a) Explain PLA with the help of block diagram. Mention the advantages of programmable logic devices. [7M]
(b) What is PROM? Implement full adder using PROM. [7M]