Hall	Ticket	No
man	TICKEU	110

Question Paper Code: AECB06

# **INSTITUTE OF AERONAUTICAL ENGINEERING**

(Autonomous)

Four Year B.Tech III Semester End Examinations (Regular) - November, 2019 Regulation: IARE – R18

## ELECTRONIC DEVICES AND CIRCUITS

Time: 3 Hours

current is 10mA.

(ECE)

Max Marks: 70

## Answer ONE Question from each Unit All Questions Carry Equal Marks All parts of the question must be answered in one place only

## $\mathbf{UNIT} - \mathbf{I}$

1. (a) Draw the V-I characteristics of a semiconductor diode and discuss the effect of temperature on Cut-in voltage and reverse saturation current. Define static and dynamic resistances

[7M]

- (b) Design a full wave rectifier with C filter to provide 10V DC at 100 mA with a maximum ripple of 2%, input frequency is 50Hz. [7M]
- 2. (a) Illustrate the working of bridge full wave rectifier with circuit diagram and waveforms and obtain expression for ripple factor . [7M]
  - (b) Draw a diode clipping circuit to convert 1 KHz sine-wave of 20V peak to peak, to a symmetric square-wave of 4 volt peak to peak amplitude.

[7M]

#### $\mathbf{UNIT}-\mathbf{II}$

- 3. (a) Draw and explain the input and output characteristics of Common emitter configuration and mention various parameters there in. [7M]
  (b) A transistor has β = 150. Calculate the approximate collector and base currents if the emitter
- 4. (a) Define operating point. Explain the DC and AC load line analysis of a BJT.

[7M]

[7M]

(b) Determine the parameters  $h_{fe}$ ,  $h_{oe}$ ,  $h_{ie}$  and  $h_{re}$  from the characteristic curves of CE transistor.

[7M]

### $\mathbf{UNIT} - \mathbf{III}$

- 5. (a) Explain the method of thermistor and sensistor compensation technique in transistor bias compensation. [7M]
  - (b) Calculate the quiescent current and voltage of collector to base bias arrangement using the following data:  $V_{CC} = 10$ V,  $R_B = 100$ K $\Omega$ ,  $R_C = 2$ K $\Omega$ ,  $\beta = 50$  and also specify a value of  $R_B$  so that  $V_{CE} = 7$ V. [7M]

- 6. (a) Explain the small signal equivalent of CB amplifier using accurate h-parameter model. Obtain the expression for  $A_V$ ,  $A_I$ ,  $R_I$  and  $R_0$  [7M]
  - (b) The emitter follower has the following circuit parameters:  $R_S = 500\Omega$ ,  $R_1 = R_2 = 50K\Omega$ ,  $R_L = 2K\Omega$ ,  $h_{fe} = 100$  and  $h_{ie} = 1.1K\Omega$ . Determine the input resistance, output resistance, current gain and voltage gain. [7M]

#### $\mathbf{UNIT}-\mathbf{IV}$

- 7. (a) Draw and explain the drain and transfer characteristics of enhancement n channel MOSFET with neat sketch. [7M]
  - (b) A common source MOSFET amplifier is to be constructed using a n-channel MOSFET which has a conduction parameter of 50mA/V and a threshold voltage of 2.0 volts. If the supply voltage is +15 volts and the load resistor is 470 Ohms, calculate the values of the resistors required to bias the MOSFET amplifier at  $1/3(V_{DD})$ . Draw the circuit diagram and Values given:  $V_{DD} = +15v$ ,  $V_{TH} = +2.0v$ , k = 50mA/V and  $R_D = 470\Omega$ . [7M]
- 8. (a) Define JFET parameters and establish the relations between them. Explain the operation of JFET with a neat diagram and also draw drain and transfer characteristics. [7M]
  - (b) The following information is included on the data sheets for an N-channel JFET.  $I_{DSS} = 25$ mA,  $V_P = -10$ V and  $g_{m0} = 4000 \mu$ s. Determine the values of transconductance at  $V_{GS} = -5$ V.

[7M]

[7M]

#### $\mathbf{UNIT} - \mathbf{V}$

9. (a) Explain the small signal equivalent circuit of common drain amplifier with necessary diagrams.

[7M]  $5KO_{ra} = 10MO_{ra} = 50 \text{ and } ra = 25KO_{ra}$ 

- (b) The CS amplifier has the following components:  $R_D = 5K\Omega$ ,  $R_G = 10M\Omega$ ,  $\mu = 50$  and  $r_d = 35K\Omega$ . Evaluate  $A_v$ ,  $Z_i$  and  $Z_0$ . [7M]
- 10. (a) Explain the V-I Characteristics of Zener diode and analyze its breakdown mechanisms. [7M]
  - (b) A 5.0V stabilized power supply is required to be produced from a 12V DC power supply input source. The maximum power rating PZ of the zener diode is 2W. Using the zener regulator circuit above calculate:
    - i) The maximum current flowing through the zener diode.
    - ii) The minimum value of the series resistor,  $R_S$ .
    - iii) The load current  $I_L$  if a load resistor of  $1k\Omega$  is connected across the zener diode.
    - iv) The zener current  $I_Z$  at full load.

Page 2 of 2