



INSTITUTE OF AERONAUTICAL ENGINEERING

(Autonomous)

B.Tech I/II Semester Supplementary Examinations - July, 2017

Regulation: IA-R16

FUNDAMENTAL OF ELECTRICAL AND ELECTRONICS ENGINEERING

[Common for : II Semester (CSE and IT)]

Time: 3 Hours

Max Marks: 70

Answer ONE Question from each Unit

All Questions Carry Equal Marks

All parts of the question must be answered in one place only

UNIT – I

1. (a) State and explain Faraday's laws of Electromagnetic Induction? [6M]
- (b) For the network shown in Figure 1, find all the branch currents and voltage drops across all resistors. [8M]

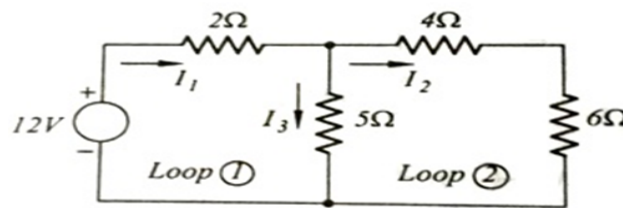


Figure 1

2. (a) Derive the expression for the voltage across capacitor and prove that the energy stored in the capacitor $E_c = \frac{1}{2} CV^2$ [7M]
- (b) Derive an expression for finding the equivalent capacitance when 'n' capacitors are connected in series. [7M]

UNIT – II

3. (a) Using nodal analysis, find the voltage across BC and the current in the 12V source for the circuit shown in Figure 2. [7M]

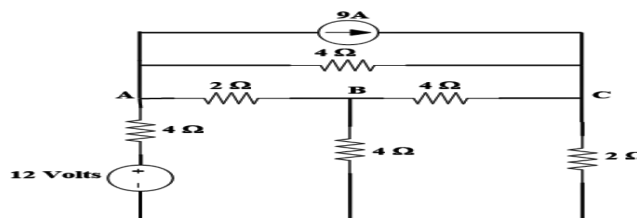


Figure 2

- (b) State and explain Tellegen's theorem and superposition theorem with an example. [7M]
4. (a) Prove that the maximum power could be transferred only when load resistance equals Thevenin's resistance [7M]
- (b) Determine the current through 6 ohm resistance connected across A-B terminals in the circuit shown in Figure 3 using Thevenin's theorem. [7M]

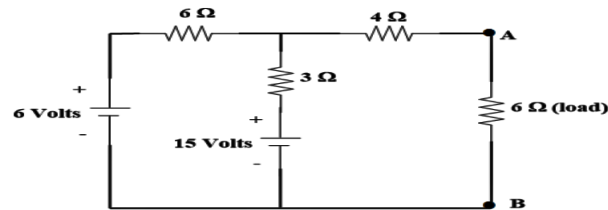


Figure 3

UNIT – III

5. (a) Two impedances $(5+j31.4)$ and $(50+j4.71)$ are connected in parallel across a 230V, 50Hz supply. Calculate the branch currents, total current drawn from the supply and the total power consumed. [7M]
- (b) Show that two watt meters are sufficient to measure the total power in a balanced three phase system. Draw the phasor diagram. [7M]
6. (a) Determine the equivalent resistance between 'X' & 'Y' for the network shown in Figure 4 using star – delta transformation. [8M]

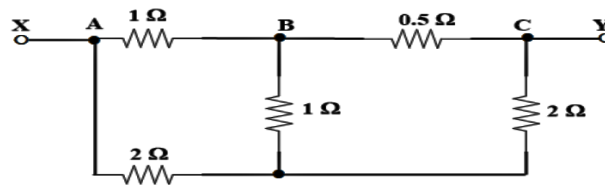


Figure 4

- (b) With the help of a power triangle explain the relation between active, reactive and apparent power for inductive as well as capacitive loads. Mention their units. [6M]

UNIT – IV

7. (a) Explain the operation of a full wave bridge rectifier with filter. [7M]
- (b) Draw and explain the v-I characteristics of a p-n junction diode. [7M]
8. (a) Draw the circuit diagram of a half wave rectifier. Explain the operation of the circuit with relevant waveforms. [7M]
- (b) Explain the operation of a zener diode as a voltage regulator with its connection diagram and characteristic curve. [7M]

UNIT – V

9. (a) Explain forward and reverse bias with respect to an npn transistor. [7M]
(b) With a neat circuit diagram explain the cc configuration of a transistor. [7M]
10. (a) Draw a neat circuit diagram of a single stage CE amplifier? Explain [7M]
(b) Explain how PNP transistor can be used as an amplifier. [7M]

- o o ○ o o -