

--	--	--	--	--	--	--	--	--	--



INSTITUTE OF AERONAUTICAL ENGINEERING

(Autonomous)

B.Tech II Semester End Examinations (Regular/Supplementary) - May, 2018

Regulation: IARE – R16

FUNDAMENTALS OF ELECTRICAL AND ELECTRONICS ENGINEERING

Time: 3 Hours

(Common to CSE | IT)

Max Marks: 70

Answer ONE Question from each Unit

All Questions Carry Equal Marks

All parts of the question must be answered in one place only

UNIT – I

1. (a) Determine the current through 6Ω resistor and the power supplied by the current source for the circuit shown in Figure 1. [7M]

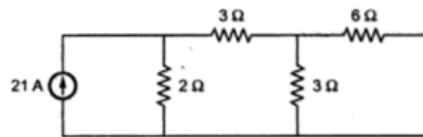


Figure 1

- (b) Differentiate the following elements with examples [7M]
- linear and non-linear elements
 - active and passive elements
2. (a) Find the equivalent resistance between A and B in the network shown in Figure 2. [7M]

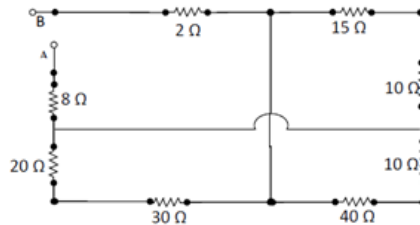


Figure 2

- (b) The current in the 6Ω of the network is $2A$. Determine the currents in all the resistances and the supply voltage V as shown in Figure 3. [7M]

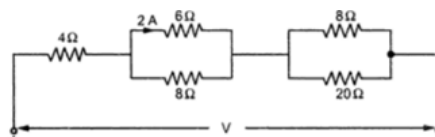


Figure 3

UNIT – II

3. (a) Using loop method of analysis, determine the current in 2Ω resistors as shown in Figure 4. [7M]

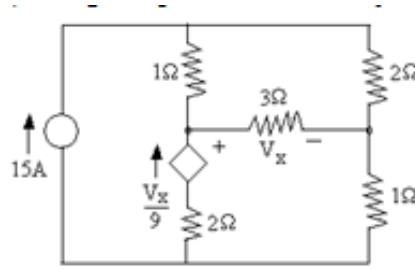


Figure 4

- (b) For the network shown in Figure 5, select a tree with branches having resistances 3Ω and 4Ω . [7M]

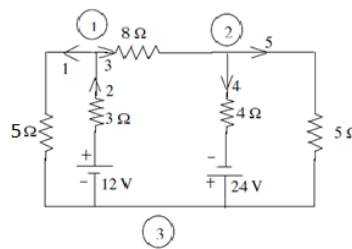


Figure 5

4. (a) State and explain compensation theorem with suitable example. [7M]
 (b) Find R_{AB} required to be connected across A-B terminals for a maximum power transfer shown in Figure 6. Also calculate maximum power. [7M]

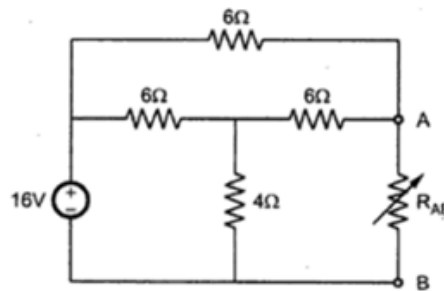


Figure 6

UNIT – III

5. (a) Give the steady state response of series RL circuit using sinusoidal input. [7M]
 (b) Derive the relationship between line and phase voltages and currents in star connection. [7M]
6. (a) Derive the expression for measurement of power and power factor of a balanced three phase load. [7M]
 (b) A three phase balanced system supplies 110V to a delta connected load whose phase impedances are equal to $(3.54+j3.54)\Omega$. Determine the line currents. [7M]

UNIT – IV

7. (a) Explain the working of bridge rectifier with neat suitable diagram. [7M]
(b) A voltage of $200 \cos \omega t$ is applied to half-wave rectifier with load resistance of $5k\Omega$. Find the maximum dc current component, rms current, ripple factor and efficiency. [7M]
8. (a) Explain the working of Zener diode act as a voltage regulator. [7M]
(b) Derive the expression for I_{dc} , I_{rms} and ripple factor for half-wave rectifier. [7M]

UNIT – V

9. (a) Explain the operation of NPN transistor. [7M]
(b) Draw and explain the input and output characteristics of common emitter configuration. [7M]
10. (a) Explain the operation of transistor as an amplifier. [7M]
(b) A transistor has $\beta = 100$. If the collector current is 40 mA, find the value of emitter current. [7M]

– ○ ○ ○ ○ –