

--	--	--	--	--	--	--	--	--	--



INSTITUTE OF AERONAUTICAL ENGINEERING

(Autonomous)

B.Tech II Semester End Examinations (Regular) - May, 2017

Regulation: IARE – R16

ELECTRICAL CIRCUITS

(Common for ECE/EEE)

Time: 3 Hours

Max Marks: 70

Answer ONE Question from each Unit

All Questions Carry Equal Marks

All parts of the question must be answered in one place only

UNIT – I

1. (a) Using Kirchoff's current law, find the value of I_s in the circuit shown in figure1. Take $V_1 = 2V$. [7M]

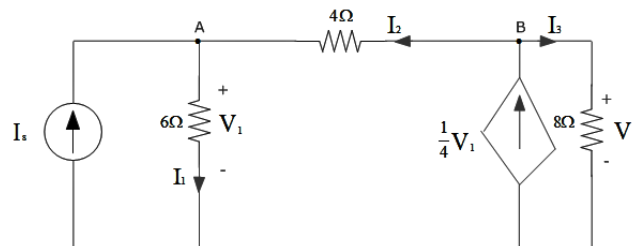


Figure 1

- (b) Differentiate between [7M]
- i. dependent and independent sources
 - ii. ideal and practical sources.
2. (a) A bulb rated 110V, 60W is connected with another bulb rated 110V, 100 W across a 220V mains. Calculate the resistance which should be joined in parallel with the first bulb so that both the bulbs may take their rated power. [7M]
- (b) A current as shown in figure2 is applied across a 5Ω resistor. Find and Plot $v(t)$ and $p(t)$. [7M]

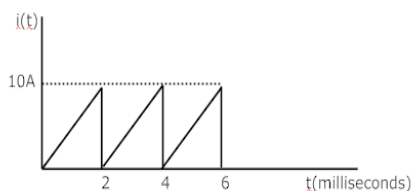


Figure 2

UNIT – II

3. (a) What is meant by dual of a network? Draw the dual circuit for the given circuit shown in figure3 [7M]

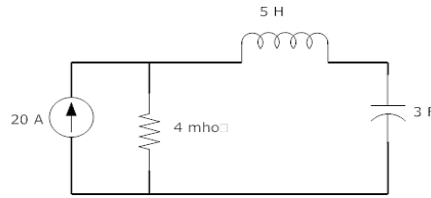


Figure 3

- (b) Using nodal analysis find the current through the branch AB for the network shown in figure4. [7M]

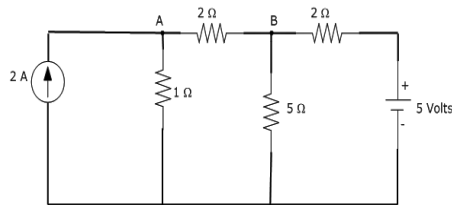


Figure 4

4. (a) In the network shown in figure5, find the current I_1 supplied by the battery using star/delta transformation. [7M]

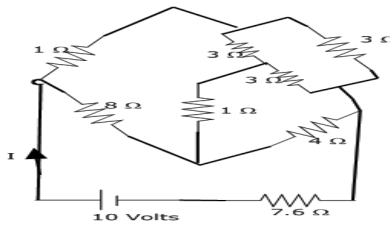


Figure 5

- (b) Using an appropriate circuit, explain graph, tree and basic tie set matrix. [7M]

UNIT – III

5. (a) Draw the phasor diagram for the series circuit shown in figure6 when the current in the circuit is 2A. Find the values of V_1 and V_2 and show these voltages on the phasor diagram. [7M]
 (b) A inductive coil draw 10A current and consumes 1KW power from a 200V, 50HZ AC supply. Determine Impedance, power factor, Real power and Reactive power. [5M]
6. (a) A resistance of 24Ω , a capacitor of $150\mu\text{F}$ and an inductor of 0.16H are connected in series with each other. A supply of 240V, 50Hz is applied to the ends. Calculate [7M]
 i. the current in the circuit

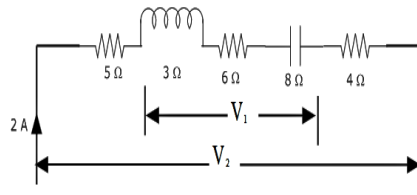


Figure 6

- ii. the potential difference across each element
 - iii. the frequency to which the supply would need to be changed so that the current would be at unity power factor
 - iv. find the current at this frequency.
- (b) Explain the relation between apparent power, active power and reactive power. Write their units. Also explain the significance of power factor. [7M]

UNIT – IV

7. (a) State and Explain Maximum Transfer Theorem for AC and DC excitations. [7M]
- (b) A series RLC circuit has $R=10\Omega$, $C=10\mu F$ and $L=60mH$. At a frequency of 25HZ the power factor of the circuit is 45° lead. At what frequency will the circuit be resonant? [7M]
8. (a) Explain [7M]
- i. Faraday's laws of electromagnetic induction
 - ii. band width and Q factor of series resonance circuits.
- (b) A cast steel electromagnet has an air gap length of 3mm and iron path of length 40cm. Find the number of ampere-turns necessary to produce a flux density of $0.7wb/m^2$ in the gap. Neglect leakage and fringing. Assume ampere turns required for air gap to be 70% of the total ampere turns. [7M]

UNIT – V

9. (a) State and explain reciprocity theorem. [7M]
- (b) State Millman's theorem. Calculate the current I for the circuit shown in Figure7 using Millman's theorem. [7M]

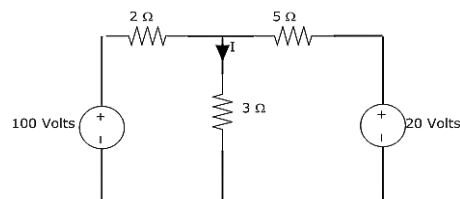


Figure 7

10. (a) State and Explain Tellegen's theorem. [7M]
- (b) With a suitable circuit explain the solution of a circuit using Thevenin's theorem. [7M]

