



**INSTITUTE OF AERONAUTICAL ENGINEERING**  
(Autonomous)

B.Tech II Semester End Examinations (Supplementary) - July, 2018

Regulation: IARE – R16

**ELECTRICAL CIRCUITS**

(Common to ECE | EEE)

**Time: 3 Hours**

**Max Marks: 70**

**Answer ONE Question from each Unit**  
**All Questions Carry Equal Marks**  
**All parts of the question must be answered in one place only**

**UNIT – I**

1. (a) State and explain Kirchoff's laws with relevant circuits. [7M]  
 (b) A dc circuit comprises of two resistors; resistor A of value 25 ohm and resistor B of unknown value, connected in parallel, together with a third resistor C of value 5 ohm, connected in series with the parallel branch. Find the voltage to be applied across the whole circuit and the value of the resistor B if the potential difference across C is 90V, and the total power consumed is 4320W. [7M]
  
2. (a) Classify different types of Ideal and Practical sources and dependent and independent sources. [7M]  
 (b) In the circuit shown in Figure 1 , Find I, IL and voltage drop across RL. [7M]

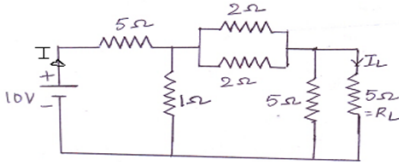


Figure 1

**UNIT – II**

3. (a) Determine the current in 5Ω resistor for the circuit shown in Figure 2. [7M]

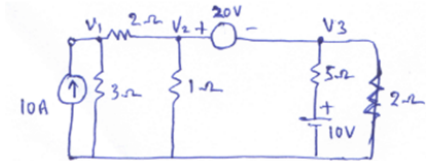


Figure 2

- (b) Find current  $I$  in the network shown in Figure 3 using star/delta transformation [7M]

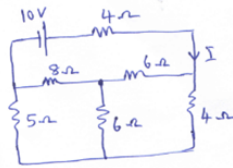


Figure 3

4. (a) Find node voltages in the circuit shown in Figure 4 using nodal analysis. [7M]

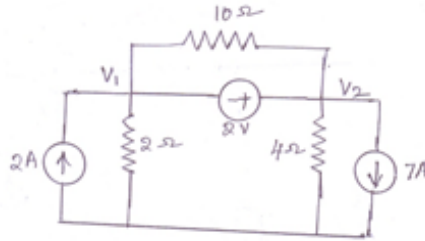


Figure 4

- (b) Obtain the dual of the network given in Figure 5 [7M]

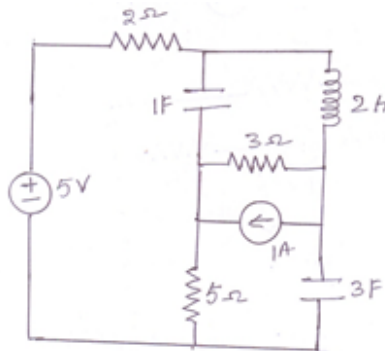


Figure 5

### UNIT – III

5. (a) Define active and reactive power. Mention their units. Also explain the importance of power factor in an ac circuit. [7M]
- (b) The current in a circuit is given by  $(5+j10)A$  when the applied voltage is  $(225+j150)V$ . Determine (i) the complex expression for the impedance stating whether it is inductive or capacitive (ii) power (iii) phase angle between current and voltage. [7M]

6. (a) Derive the expression for current of a series R-C circuit excited with an AC sinusoidal voltage source. [7M]  
 (b) Find the RMS value of the periodic waveform given in Figure 6 with time period T. [7M]

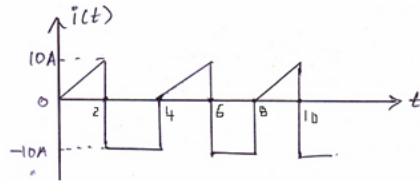


Figure 6

#### UNIT – IV

7. (a) Explain the concept of Self Inductance and Mutual Inductance. [7M]  
 (b) Determine the value of Q at resonance and bandwidth for the circuit given in Figure 7 [7M]

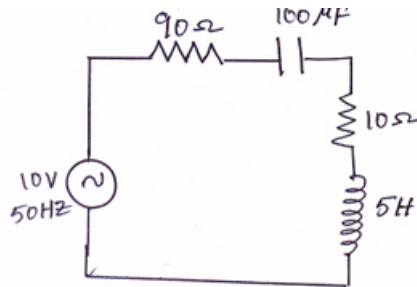


Figure 7

8. (a) Write a short notes on Dot Convention. [7M]  
 (b) An iron ring of cross-sectional area  $6\text{cm}^2$  is wound with a wire of 100 turns and has a sawcut (length) of 2mm. Calculate the magnetizing current required to produce a magnetic flux of 0.1mwb if mean length of magnetic path is 30cm and relative permeability of iron is 470. [7M]

## UNIT – V

9. (a) State and explain Maximum power transfer Theorem for AC and DC excitations. [7M]  
 (b) Find the Thevenin's Equivalent circuit across the terminals a-b shown in Figure 8 .also find I. [7M]

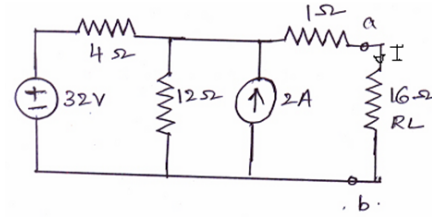


Figure 8

10. (a) State and explain Millman's Theorem. [7M]  
 (b) Calculate current I in the circuit given in Figure 9 using superposition theorem. [7M]

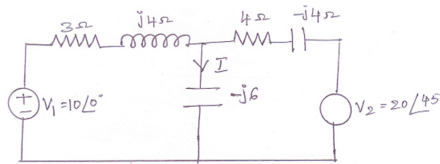


Figure 9

- o o ○ o o -