

Hall Ticket No

|  |  |  |  |  |  |  |  |  |  |
|--|--|--|--|--|--|--|--|--|--|
|  |  |  |  |  |  |  |  |  |  |
|--|--|--|--|--|--|--|--|--|--|

Question Paper Code: AECB05



# INSTITUTE OF AERONAUTICAL ENGINEERING (Autonomous)

Dundigal, Hyderabad - 500 043

MODEL QUESTION PAPER-II

B.Tech III Semester End Examinations, November 2020

Regulations: IARE - R18

## ANALOG AND DIGITAL ELECTRONICS

### INFORMATION TECHNOLOGY

Time: 3 hour

Maximum Marks: 70

**Answer ONE Question from each MODULE**

**All Questions Carry Equal Marks**

**All parts of the question must be answered in one place only**

#### MODULE-I

- (a) Explain the formation of depletion region in an open-circuited p-n junction diode and also the effect of forward and reverse biasing of p-n junction on the depletion region with neat sketches? [7m]

(b) A P-N junction germanium diode has a reverse saturation current of 0.10 A at the room temperature of 270C. It is observed to be 30A, when the room temperature is increased. Evaluate the room temperature? [7m]
- (a) Construct the circuit diagrams of a full wave rectifier and Bridge rectifier. Explain the operation of the circuit with relevant waveforms. [7m]

(b) A full wave bridge rectifier having load resistance of 100 is fed with 220V, Assuming the diodes are ideal, Find the following terms: [7m]

  - DC output voltage
  - Peak inverse voltage
  - Rectifier efficiency

#### MODULE-II

- (a) Explain clearly the DC and AC load line and also explain how to obtain quiescent point graphically for a transistor amplifier of CE configuration. [7m]

(b) Common emitter circuit has the following components.  $R_s = 1k\Omega$ ,  $R_1 = 110k\Omega$ ,  $R_2 = 12k\Omega$ ,  $R_c = 6k\Omega$ . H-parameters are  $h_{ie} = 1.2k\Omega$ ,  $h_{fe} = 75$  and  $h_{oe} = 25\mu A/V$ ,  $h_{re} = 25 \times 10^{-4}$ . Draw the equivalent hybrid model and calculate  $A_i$ ,  $R_i$ ,  $A_v$ ,  $R_o$ ? [7m]
- (a) Explain following terms with neat sketch : [7m]

  - cut off region,
  - saturation region
  - active region

- (b) Compute current gain, voltage gain, input and output impedance of the CB amplifier if it is driven by a voltage source of internal resistance  $R_s = 1k$ . The load impedance is  $R_L = 1K$ . The transistor parameters are  $h_{ib} = 22$ ,  $h_{fb} = -0.98$ ,  $h_{rb} = 2.910^{-4}$ ,  $h_{ob} = 0.5\mu A/V$ . [7m]

### MODULE-III

5. (a) Develop the gray to binary and binary to gray conversion logic with neat sketches. [7m]  
 (b) Perform the subtraction using 1s complement and 2s Complement [7m]  
 (i)  $(11010)_2 - (10000)_2$   
 (ii)  $(1000100)_2 - (1010100)_2$
6. (a) Give the Boolean expressions, symbols and truth tables for following gates: (i) AND NOR  
 (ii) EX-OR (iii) OR (iv) EX-NOR. [7m]  
 (b) Obtain the canonical SOP form of the following functions: [7m]  
 (i)  $Y(A,B) = A+B$ .  
 (ii)  $Y(A,B,C,D) = AB+ACD$

### MODULE-IV

7. (a) Construct a 64:1 MUX using 8:1 MUXs with suitable neat block diagram. [7m]  
 (b) Solve the following Boolean expressions using K-map and implement it by using NOR gates. [7m]  
 (i)  $F(A, B, C, D) = AB'C' + AC + A'CD'$   
 (ii)  $F(W, X, Y, Z) = w'x'y'z' + wxy'z' + w'x'yz + wxyz$
8. (a) Implement the given function in 4:1 mux  $f = m(0,1,3,5,6)$  [7m]  
 (b) Build a De-Multiplexer using  $F(w,x,y,z) = m(1,4,5,6,7,9,14,15)$  [7m]

### MODULE-V

9. (a) Write short notes on shift register? Mention its application along with the Serial Transfer in 4-bit shift Registers? [7m]  
 (b) Identify the steps involved in design of asynchronous sequential circuit in detail with an example? [7m]
10. (a) Explain 3 bit ring counter? Discuss how ring counters differ from twisted ring counter? [7m]  
 (b) Construct and implement 4-bit binary counter (using D flip flops) which counts all possible odd numbers only? [7m]

---

**\*\*END OF EXAMINATION\*\***

## **COURSE OBJECTIVES:**

**The course should enable the students to:**

|   |                                                                                                                                                                            |
|---|----------------------------------------------------------------------------------------------------------------------------------------------------------------------------|
| 1 | The Fundamental knowledge of the operational principles and characteristics of semiconductor devices and their applications.                                               |
| 2 | The basic concept of number systems, boolean algebra and optimized implementation of combinational and sequential circuits.                                                |
| 3 | The perceive subsequent studies in the area of microprocessors, microcontrollers, VLSI design and embedded systems effectively use of fundamentals of digital electronics. |

## **COURSE OUTCOMES:**

**After successful completion of the course, students should be able to:**


|       |                                                                                                                                                                                              |
|-------|----------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|
| CO 1  | Recall the properties of semiconductor materials which form the basis for the formation of PN junction diode.                                                                                |
| CO 2  | Illustrate the volt-ampere characteristics of semiconductor devices for finding cut-in voltage, static, dynamic resistance and transition, diffusion capacitance.                            |
| CO 3  | Apply the pn junction characteristics for the diode.Applications such as switch and rectifiers.                                                                                              |
| CO 4  | Explain half wave and full wave rectifier circuits with filter and without filters for conversion of alternating current in to direct current.                                               |
| CO 5  | Interpret DC and AC load line analysis of different amplifiers for optimal operating level regardless of input, load placed on the device.                                                   |
| CO 6  | Analyse the input and output characteristics of transistor configurations and small signal h-parameter models for determining the input - output resistances, current gain and voltage gain. |
| CO 7  | Compare the binary decimal, octal and hexadecimal number systems in terms of basic arithmetic operations.                                                                                    |
| CO 8  | Identify the functionality of logic gates, parity code and hamming code techniques for error detection and correction of single bit in digital systems.                                      |
| CO 9  | Apply Boolean postulates and theorems, k-map and tabular methods for obtaining minimized Boolean expressions.                                                                                |
| CO 10 | Develop gate level combinational circuits to built adders, subtractors, multiplexers, demultiplexers, encoder and decoders.                                                                  |
| CO 11 | Describe the operation of Flip-Flops and latches for constructing sequential circuits .                                                                                                      |
| CO 12 | Implement the synchronous& asynchronous counters for memory storing applications.                                                                                                            |

## MAPPING OF SEMESTER END EXAMINATION QUESTIONS TO COURSE OUTCOMES

| Q.No |   | All Questions carry equal marks                                                                                                                                                                                                                                                                                                       | Taxonomy   | CO's | PO's   |
|------|---|---------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|------------|------|--------|
| 1    | a | Explain the formation of depletion region in an open-circuited p-n junction diode and also the effect of forward and reverse biasing of p-n junction on the depletion region with neat sketches?                                                                                                                                      | Remember   | CO 1 | PO 1   |
|      | b | A P-N junction germanium diode has a reverse saturation current of 0.10 A at the room temperature of 270C.It is observed to be 30A, when the room temperature is increased. Evaluate the room temperature?                                                                                                                            | Understand | CO 2 | PO 1,2 |
| 2    | a | Construct the circuit diagrams of a full wave rectifier and Bridge rectifier. Explain the operation of the circuit with relevant waveforms.                                                                                                                                                                                           | Apply      | CO 3 | PO 2   |
|      | b | A full wave bridge rectifier having load resistance of 100 is fed with 220V, Assuming the diodes are ideal, Find the following terms: (i) DC output voltage (ii) Peak inverse voltage (iii) Rectifier efficiency                                                                                                                      | Understand | CO 4 | PO 1   |
| 3    | a | Explain clearly the DC and AC load line and also explain how to obtain quiescent point graphically for a transistor amplifier of CE configuration.                                                                                                                                                                                    | Understand | CO 5 | PO 1,3 |
|      | b | Common emitter circuit has the following components. $R_s = 1k\Omega$ , $R_1 = 110k\Omega$ , $R_2 = 12k\Omega$ , $R_c = 6k\Omega$ . H-parameters are $h_{ie} = 1.2k\Omega$ , $h_{fe} = 75$ and $h_{oe} = 25\mu A/V$ , $h_{re} = 25 * 10^{-4}\mu A/V$ . Draw the equivalent hybrid model and calculate $A_i$ , $R_i$ , $A_v$ , $R_o$ ? | Analyze    | CO 6 | PO 1,3 |
| 4    | a | Explain following terms with neat sketches (i) cut off region, (ii) saturation region (iii) active region                                                                                                                                                                                                                             | Understand | CO 5 | PO 1,3 |
|      | b | Compute current gain, voltage gain, input and output impedance of the CB amplifier if it is driven by a voltage source of internal resistance $R_s=1k$ . The load impedance is $R_L=1K$ . The transistor parameters are $h_{ib} = 22$ , $h_{fb} = -0.98$ , $h_{rb} = 2.910^{-4}$ , $h_{ob} = 0.5\mu A/V$                              | Analyze    | CO 6 | PO 1,3 |
| 5    | a | Develop the gray to binary and binary to gray conversion logic with neat sketches.                                                                                                                                                                                                                                                    | Apply      | CO 8 | PO 1,2 |

|    |   |                                                                                                                                                                                                  |            |       |        |
|----|---|--------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|------------|-------|--------|
|    | b | Perform the subtraction using 1s complement and 2s Complement (i) $(11010)_2(10000)_2$<br>(ii) $(1000100)_2(1010100)_2$                                                                          | Analyze    | CO 7  | PO 1   |
| 6  | a | Give the Boolean expressions, symbols and truth tables for following gates: (i) AND NOR<br>(ii) EX-OR (iii) OR (iv) EX-NOR.                                                                      | Apply      | CO 8  | PO 1,2 |
|    | b | Obtain the canonical SOP form of the following functions: (i) $Y(A,B) = A+B$ . (ii) $Y(A,B,C,D) = AB+ACD$                                                                                        | Apply      | CO 9  | PO 1,2 |
| 7  | a | Construct a 64:1 MUX using 8:1 MUXs with suitable neat block diagram.                                                                                                                            | Apply      | CO 10 | PO 1,2 |
|    | b | Solve the following Boolean expressions using K-map and implement it by using NOR gates.<br>(i) $F(A, B, C, D) = AB'C' + AC + A'CD'$<br>(ii) $F(W, X, Y, Z) = w'x'y'z' + wxy'z' + w'x'yz + wxyz$ | Apply      | CO 9  | PO 1,2 |
| 8  | a | Implement the given function in 4:1 mux<br>$F = \sum m(0, 1, 3, 5, 6)$                                                                                                                           | Apply      | CO 10 | PO 1,2 |
|    | b | Build a De-Multiplexer using<br>$F(w, x, y, z) = \sum m(1, 4, 5, 6, 7, 9, 14, 15)$                                                                                                               | Apply      | CO 9  | PO 1,2 |
| 9  | a | Write short notes on shift register? Mention its application along with the Serial Transfer in 4-bit shift Registers?                                                                            | Understand | CO 11 | PO 1,3 |
|    | b | Identify the steps involved in design of asynchronous sequential circuit in detail with an example?                                                                                              | Apply      | CO 12 | PO 2,3 |
| 10 | a | Explain 3 bit ring counter? Discuss how ring counters differ from twisted ring counter?                                                                                                          | Understand | CO 12 | PO 1,3 |
|    | b | Construct and implement 4-bit binary counter (using D flip flops) which counts all possible odd numbers only?                                                                                    | Apply      | CO 10 | PO 2,3 |
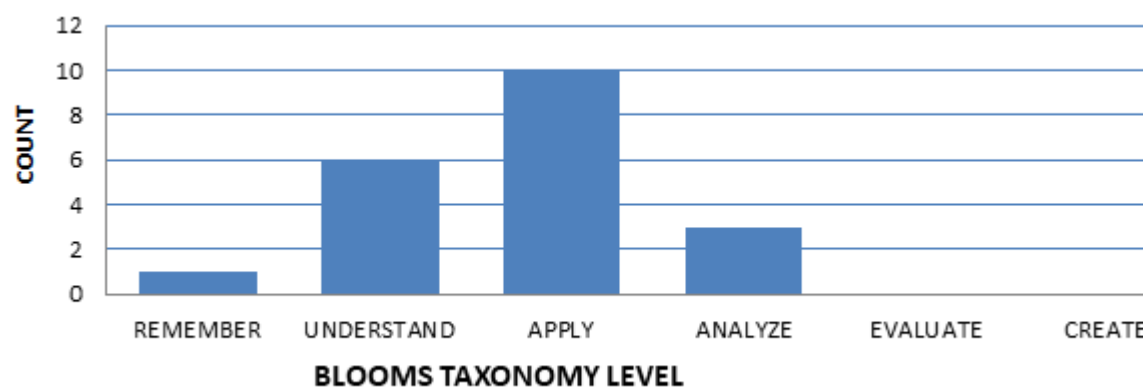
## KNOWLEDGE COMPETENCY LEVELS OF MODEL QUESTION PAPER



Signature of Course Coordinator

HOD, IT