

Hall Ticket No

Question Paper Code: AEC008



# INSTITUTE OF AERONAUTICAL ENGINEERING

(Autonomous)

Dundigal, Hyderabad - 500 043

## MODEL QUESTION PAPER-I

B.Tech V Semester End Examinations, November - 2019

Regulation: IARE-R16

### INTEGRATED CIRCUITS APPLICATIONS

(Electrical and Electronics Engineering)

Time: 3 Hours

Max Marks: 70

Answer any ONE question from each Unit

All questions carry equal marks

All parts of the question must be answered in one place only

#### UNIT – I

- 1 a) Explain the use of constant current bias method for Dual input balanced output differential amplifier. [7M]
- b) An op-amp with a slew rate =  $0.5V/\mu s$  is used as an inverting amplifier to obtain a gain of 100. The voltage gain Vs frequency characteristic of the amplifier is flat up to 10 KHz. Determine [7M]
  - i. The maximum peak-to-peak input signal that can be applied without any distortion to the output
  - ii. The maximum frequency of the input signal to obtain a sine wave output of 2V peak.
- 2 a) Explain the operation of Differential amplifier with neat circuit diagram. [7M]
- b) For an op-amp PSRR =60 db(min), CMRR=  $10^4$  and the differential mode gain is  $10^5$ , the voltage changes by 20 V in 4  $\mu$  sec. calculate (i) numerical value of the PSRR (ii) common mode gain. (iii) Slew rate. [7M]

#### UNIT – II

- 3 a) What is the instrumentation amplifier? What are the required parameters of an instrumentation amplifier? Explain the working of instrumentation amplifier with neat circuit diagram. [7M]
- b) Design a phase shift oscillator for  $f_o=500$  Hz and design a wein bridge oscillator for  $f_o=1000$ Hz. [7M]
- 4 a) What are the limitations of an ordinary op-amp differentiator? Draw and explain the practical differentiator that will eliminate these limitations? [7M]
- b) Design a differentiator to differentiate an input signal that varies in frequency from 10 Hz to about 1 KHz. If a sine wave of 1V peak at 1000 Hz is applied to this differentiator draw the output waveforms. [7M]

### UNIT – III

- 5 a) Explain first order high pass filter with neat circuit diagram and also derive its transfer function. [7M]  
b) Design a second order Butterworth low-pass filter having upper cut-off frequency 1 kHz. Then determine its frequency response. Given parameters:  $f_c=1$  kHz,  $C=0.1\mu\text{F}$ ,  $R=1.6\text{K}\Omega$  and damping factor  $\alpha=1.414$ . [7M]
- 6 a) Explain an Astable multivibrator using 555 timer and derive the expression for its frequency of oscillation [7M]  
b) Design a 555 based square wave generator to produce an asymmetrical square wave of 2 KHz. If  $V_{cc}=12\text{V}$ , draw the voltage curve across the timing capacitor and output waveform. [7M]

### UNIT – IV

- 7 a) With neat diagram, explain the working principle of R-2R ladder type DAC and list the advantages and disadvantages. [7M]  
b) Design a 4 – bit R-2R ladder type D/A converter and plot the transfer characteristics that is binary input versus output voltage and calculate the resolution and linearity . [7M]
- 8 a) Explain successive approximation A/D converter with functional diagram for a given analog input. [7M]  
b) Design a dual slope ADC uses a 16 bit counter and a 4 MHz clock rate. The maximum input voltage is +10V. The maximum integrator output voltage should be - 8V when the counter has cycled through  $2^n$  counts. The capacitor used in the integrator is  $0.1\mu\text{f}$ . Find the value of the resistor R of the integrator. [7M]

### UNIT – V

- 9 a) Explain the following terms with reference to CMOS logic. [7M]  
i. Logic Levels  
ii. Noise margin  
iii. Power supply rails  
iv. Propagation delay  
b) Design combinational circuit for common anode 7 segment display / driver. [7M]
- 10 a) Design 3 bit synchronous counter using JK flip flops [7M]  
b) Using two  $74\times 138$  decoders design a 4 to 16 decoder. [7M]



# INSTITUTE OF AERONAUTICAL ENGINEERING

(Autonomous)

Dundigal, Hyderabad - 500 043

## COURSE OBJECTIVES

S.No	Description
I	Be acquainted to principles and characteristics of op-amp and apply the techniques for the design of comparators, instrumentation amplifier, integrator, differentiator, multivibrators, waveform generators, log and anti-log amplifiers.
II	Analyze and design filters, timer, analog to digital and digital to analog Converters.
III	Understand the functionality and characteristics of commercially available digital integrated circuits.

## COURSE OUTCOMES (COs):

CO 1	Discuss the analysis of Op-Amp for different configurations and its properties.
CO 2	Analyze and design the linear and non linear applications of Op-Amp
CO 3	Design the various filters using Op-Amp and analysis of Multivibrators using 555 Timer
CO 4	Describe the various ADC and DAC techniques
CO 5	Explore the concepts of Combinational and sequential logic circuits using digital IC's

## COURSE LEARNING OUTCOMES

AEC008.01	Illustrate the block diagram, classifications, package types, temperature range , specifications and characteristics of Op-Amp.
AEC008.02	Discuss various types of configurations in differential amplifier with balanced and unbalanced outputs.
AEC008.03	Evaluate DC and AC analysis of dual input balanced output configuration and discuss the properties of differential amplifier and Discuss the operation of cascaded differential amplifier.
AEC008.04	Analyze and design linear applications like inverting amplifier, non-inverting amplifier, instrumentation amplifier and etc. using Op-Amp.
AEC008.05	Analyze and design non linear applications like multiplier, comparator, log and anti log amplifiers, waveform generators and etc, using Op-Amp.
AEC008.06	Discuss various active filter configurations based on frequency response and construct using 741 Op- Amp.
AEC008.07	Design bistable, monostable and astable multivibrators operation by using IC 555 timer.
AEC008.08	Determine the lock range and capture range of PLL and use in various applications of communications.
AEC008.09	Understand the classifications, characteristics and need of data converters such as ADC and DAC .
AEC008.10	Analyze the Digital to Analog converter technique such as weighted resistor DAC, R-2R ladder DAC, inverted R-2R ladder DAC and IC 1408 DAC.
AEC008.11	Analyze the Analog to Digital converter technique such as integrating, successive approximation and flash converters.
AEC008.12	Design Adders, multiplexers, demultiplexers, decoders, encoders by using TTL/CMOS integrated circuits and study the TTL and CMOS logic families.

AEC008.13	Design input/output interfacing with transistor – transistor logic or complementary metal oxide semiconductor integrated circuits.
AEC008.14	Understand the operation of SR, JK, T and D flip-flops with their truth tables and characteristic equations. Design TTL/CMOS sequential circuits.
AEC008.15	Design synchronous, asynchronous and decade counter circuits and also design registers like shift registers and universal shift registers.

**MAPPING OF SEMESTER END EXAMINATION TO COURSE LEARNING OUTCOMES:**

SEE Question No.		Course Learning Outcomes	Course Outcomes	Blooms Taxonomy Level
1	a	AEC008.02 Discuss various types of configurations in differential amplifier with balanced and unbalanced outputs.	CO 1	Understand
	b	AEC008.01 Illustrate the block diagram, classifications, package types, temperature range, specifications and characteristics of Op-Amp.	CO 1	Remember
2	a	AEC008.01 Illustrate the block diagram, classifications, package types, temperature range, specifications and characteristics of Op-Amp.	CO 1	Understand
	b	AEC008.03 Evaluate DC and AC analysis of dual input balanced output configuration and discuss the properties of differential amplifier and Discuss the operation of cascaded differential amplifier.	CO 1	Remember
3	a	AEC008.04 Analyze and design linear applications like inverting amplifier, non-inverting amplifier, instrumentation amplifier and etc. using Op-Amp.	CO 2	Remember
	b	AEC008.05 Analyze and design non linear applications like multiplier, comparator, log and anti log amplifiers, waveform generators and etc, using Op-Amp.	CO 2	Apply
4	a	AEC008.04 Analyze and design linear applications like inverting amplifier, non-inverting amplifier, instrumentation amplifier and etc. using Op-Amp.	CO 2	Remember
	b	AEC008.04 Analyze and design linear applications like inverting amplifier, non-inverting amplifier, instrumentation amplifier and etc. using Op-Amp.	CO 2	Apply
5	a	AEC008.06 Discuss various active filter configurations based on frequency response and construct using 741 Op- Amp.	CO 3	Remember
	b	AEC008.06 Discuss various active filter configurations based on frequency response and construct using 741 Op- Amp.	CO 3	Apply
6	a	AEC008.07 Design bistable, monostable and astable multivibrators operation by using IC 555 timer and study their applications.	CO 3	Understand
	b	AEC008.07 Design bistable, monostable and astable multivibrators operation by using IC 555 timer and study their applications.	CO 3	Apply

SEE Question No.		Course Learning Outcomes		Course Outcomes	Blooms Taxonomy Level
7	a	AEC008.10	Analyze the Digital to Analog converter technique such as weighted resistor DAC, R-2R ladder DAC, inverted R-2R ladder DAC and IC 1408 DAC.	CO 4	Understand
	b	AEC008.10	Analyze the Digital to Analog converter technique such as weighted resistor DAC, R-2R ladder DAC, inverted R-2R ladder DAC and IC 1408 DAC.	CO 4	Apply
8	a	AEC008.11	Analyze the Analog to Digital converter technique such as integrating, successive approximation and flash converters.	CO 4	Remember
	b	AEC008.11	Analyze the Analog to Digital converter technique such as integrating, successive approximation and flash converters.	CO 4	Apply
9	a	AEC008.12	Design Adders, multiplexers, demultiplexers, decoders, encoders by using TTL/CMOS integrated circuits and study the TTL and CMOS logic families.	CO 5	Understand
	b	AEC008.12	Design Adders, multiplexers, demultiplexers, decoders, encoders by using TTL/CMOS integrated circuits and study the TTL and CMOS logic families.	CO 5	Understand
10	a	AEC008.15	Design synchronous, asynchronous and decade counter circuits and also design registers like shift registers and universal shift registers.	CO 5	Apply
	b	AEC008.12	Design Adders, multiplexers, demultiplexers, decoders, encoders by using TTL/CMOS integrated circuits and study the TTL and CMOS logic families.	CO 5	Apply

**Signature of Course Coordinator**

**HOD, EEE**