

Hall Ticket No

| | | | | | | | | | |
|--|--|--|--|--|--|--|--|--|--|
| | | | | | | | | | |
|--|--|--|--|--|--|--|--|--|--|

Question Paper Code: AECB06



INSTITUTE OF AERONAUTICAL ENGINEERING

(Autonomous)

Dundigal, Hyderabad - 500 043

MODEL QUESTION PAPER – I

B.Tech III Semester End Examinations, November - 2019

Regulations: IARE-R18

ELECTRONIC DEVICES AND CIRCUITS

(Common to ECE/EEE)

Time: 3 hours

Max. Marks: 70

Answer ONE Question from each Unit

All Questions Carry Equal Marks

All parts of the question must be answered in one place only

MODULE – I

- 1 a) Derive an expression for total diode current starting from Boltzmann relationship in terms of the applied voltage. [7M]
- b) Find the value of D.C. resistance and A.C resistance of a Germanium junction diode at 25°C with reverse saturation current, $I_o = 25\mu\text{A}$ and at an applied voltage of 0.2V across the diode? [7M]
- 2 a) With suitable diagrams, explain the working of centre-tapped full wave rectifier. Derive an expression for V_{DC} , I_{DC} , V_{rms} and I_{rms} for it? [7M]
- b) Determine the ripple factor of an L-section filter comprising a 10H choke and 8 μF capacitor, used with a Full Wave Rectifier. The DC voltage at the load is 50V. Assume the line frequency as 50Hz? [7M]

MODULE – II

- 3 a) Define Early-effect; explain why it is called as base-width modulation? Discuss its consequences in transistors in detail? [7M]
- b) The reverse leakage current of the transistor when connected in CB configuration is 0.2 μA while it is 18 μA when the same transistor is connected in CE configuration. Determine α and β of the transistor? [7M]
- 4 a) Define Thermal Runaway in transistors? Derive the condition to prevent Thermal Runaway in Bipolar Junction Transistors? [7M]
- b) Design a collector to base bias circuit using silicon transistor to achieve a stability factor of 20, with the following specifications: $V_{CC} = 16\text{V}$, $V_{BE} = 0.7\text{V}$, $V_{CEQ} = 8\text{V}$, $I_{CQ} = 4\text{mA}$ & $\beta = 50$? [7M]

MODULE – III

- 5 a) Define biasing? Draw the fixed bias circuit and obtain the expression for the stability factor? List various disadvantages of fixed bias circuits? [7M]
- b) Design a self bias circuit using silicon transistor to achieve a stability factor of 10, with the following specifications: $V_{CC} = 16\text{V}$, $V_{BE} = 0.7\text{V}$, $V_{CEQ} = 8\text{V}$, $I_{CQ} = 4\text{mA}$ & $\beta = 50$? [7M]
- 6 a) Draw the circuit diagram and small signal equivalent of CB amplifier using accurate h-parameter model. Derive an expression for A_v , A_i , R_i and R_o ? [7M]

- b) A common Emitter circuit has the following, components: $R_s=1k\Omega$, $R_1=110K\Omega$, $R_2=12K\Omega$, $R_c=6K\Omega$. h- Parameters are $h_{ie}=1.2K$, $h_{re}=2.5 \times 10^{-4}$, $h_{fe}=75$, $h_{oe}=25\mu A/V$. Determine A_v , A_i , R_i and R_o . [7M]

MODULE – IV

- 7 a) Sketch the drain characteristics of MOSFET for different values of V_{GS} and mark different regions of operation. [7M]
- b) The P-channel FET has a $|I_{DS}|=-12mA$, $|V_p|=5V$, V_{GS} is 1.6 V. Determine drain current I_D , G_m and G_{m0} . [7M]
- 8 a) Explain with the help of neat diagrams, the structure of N-channel FET, and its volt-ampere characteristic. In what way it is different from a bipolar junction transistor. [7M]
- b) The following information is included on the data sheet for an N-channel JFET. $I_{DSS}=20mA$, $V_p=-8V$ and $g_{m0}=5mS$. Determine the values of drain current and transconductance at $V_{GS}=-4V$. [7M]

MODULE – V

- 9 a) Explain the V-I characteristics of Zener diode and analyze Avalanche and Zener Break downs? [7M]
- b) A 5.0V stabilised power supply is required to be produced from a 12V DC power supply input source. The maximum power rating P_Z of the zener diode is 2W. Using the zener regulator circuit above calculate: a) The maximum current flowing through the zener diode. b) The minimum value of the series resistor, R_s . c) The load current I_L if a load resistor of $1k\Omega$ is connected across the zener diode. d) The zener current I_Z at full load. [7M]
- 10 a) Explain the effect of external source resistance on the voltage gain of a common source amplifier? Explain with necessary derivations? [7M]
- b) A Common Source FET amplifier circuit with un bypassed R_s has the following circuit parameters: $R_d = 15K$, $R_S = 0.5K$, $R_g = 1M$, $r_d = 5K$, $g_m = 5mS$ and $V_{DD} = 20 V$. Determine A_V & R_O ? [7M]



INSTITUTE OF AERONAUTICAL ENGINEERING

(Autonomous)

I. COURSE OBJECTIVES

The course should enable the students to:

| The course should enable the students to: | |
|---|--|
| I | Introduce components such as diodes, BJTs and FETs. |
| II | Know the applications of components |
| III | Know the switching characteristics of components. |
| IV | Give understanding of various types of amplifier circuits. |

II. COURSE OUTCOMES

Students who complete the course will have demonstrated the ability to do the following

| COs | Course Outcome | CLOs | Course Learning Outcome |
|------|--|--------|---|
| CO 1 | Describe diode operation, transition capacitance, diffusion capacitance and the use of diode in various electronic circuits. | CLO 1 | Understand and analyze diodes operation and static and dynamic resistance in order to design basic circuits. |
| | | CLO 2 | Understand diffusion and transition capacitance of diode in forward and reverse bias conditions. |
| | | CLO 3 | Understand and analyze diode applications and how the diode acts as a switch. |
| | | CLO 4 | Design rectifier without and with capacitive filters for the given specifications. |
| | | CLO 5 | Understand the use of diodes in typical circuits like, clipping, clamping circuits and comparator circuits. |
| CO 2 | Understand the principle of operation of BJT in CE, CB, CC configuration and analyze transistor hybrid model. | CLO 6 | Understand the principle of operation and characteristics of common emitter, common base and common collector configurations. |
| | | CLO 7 | Understand the concept of operating point, DC & AC load lines. |
| | | CLO 8 | Analyze transistor hybrid parameter model for CE, CB and CC configurations. |
| | | CLO 9 | Determine of h-parameters of BJT amplifier from transistor characteristics. |
| CO 3 | Bias the transistors and analyze the low frequency response of BJT amplifiers. | CLO 10 | Understand the use of conversion of h-parameters among CE, CB and CC configurations. |
| | | CLO 11 | Identify the various transistor biasing circuits, compensation circuits and its usage in applications like amplifiers. |
| | | CLO 12 | Analyze various transistor configurations and asses merits and demerits for different applications. |
| | | CLO 13 | Analyze CE Amplifier with emitter resistance. |
| | | CLO 14 | Analyze low frequency response of BJT Amplifiers. |
| | | CLO 15 | Understand the effect of coupling and bypass capacitors on CE Amplifier. |

| COs | Course Outcome | CLOs | Course Learning Outcome |
|------|--|--------|--|
| CO 4 | Study and analyze the behaviour of FET and MOSFET. | CLO 16 | Explain construction and principle of operation of JFET. |
| | | CLO 17 | Understand the concept of pinch-off voltage and volt-ampere characteristic of JFET. |
| | | CLO 18 | Distinguish the constructional features and operation of BJT and FET and their applications. |
| | | CLO 19 | Understand biasing of FET and how it acts as voltage variable resistor. |
| | | CLO 20 | Discuss the construction of MOSFET and steady the VI characteristics, as it is the prime component in VLSI technology. |
| CO 5 | Analyze FET amplifiers in CS,CG,CD modes using small signal model and study the behaviour of special purpose diodes. | CLO 21 | Apply small-signal models to field effect transistors and determine the voltage gain and input and output impedances. |
| | | CLO 22 | Analyzes CS, CD, CG JFET amplifiers using small signal model. |
| | | CLO 23 | Understand basic concepts of MOSFET amplifiers. |
| | | CLO 24 | Explain the operation of Zener diode and its usage in voltage regulating application. |
| | | CLO 25 | Understand the principle of operation and characteristics of silicon controlled rectifier, tunnel diode, UJT and varactor diode. |

MAPPING OF SEMESTER END EXAMINATION TO COURSE OUTCOMES

| SEE Question No. | CO | Course Outcomes | Blooms Taxonomy Level |
|------------------|----|--|-----------------------|
| 1 | a | Describe diode operation, transition capacitance, diffusion capacitance and the use of diode in various electronic circuits. | Understand |
| | b | Describe diode operation, transition capacitance, diffusion capacitance and the use of diode in various electronic circuits. | Understand |
| 2 | a | Describe diode operation, transition capacitance, diffusion capacitance and the use of diode in various electronic circuits. | Remember |
| | b | Describe diode operation, transition capacitance, diffusion capacitance and the use of diode in various electronic circuits. | Understand |
| 3 | a | Understand the principle of operation of BJT in CE, CB, CC configuration and analyze transistor hybrid model. | Understand |
| | b | Understand the principle of operation of BJT in CE, CB, CC configuration and analyze transistor hybrid model. | Understand |

| SEE Question No. | CO | Course Outcomes | Blooms Taxonomy Level | |
|-------------------------|-----------|------------------------|--|------------|
| 4 | a | CO 2 | Understand the principle of operation of BJT in CE, CB, CC configuration and analyze transistor hybrid model. | Remember |
| | b | CO 23 | Understand the principle of operation of BJT in CE, CB, CC configuration and analyze transistor hybrid model. | Understand |
| 5 | a | CO 3 | Bias the transistors and analyze the low frequency response of BJT amplifiers. | Remember |
| | b | CO 3 | Bias the transistors and analyze the low frequency response of BJT amplifiers. | Remember |
| 6 | a | CO 3 | Bias the transistors and analyze the low frequency response of BJT amplifiers. | Understand |
| | b | CO 3 | Bias the transistors and analyze the low frequency response of BJT amplifiers. | Remember |
| 7 | a | CO 4 | Study and analyze the behaviour of FET and MOSFET. | Remember |
| | b | CO 4 | Study and analyze the behaviour of FET and MOSFET. | Understand |
| 8 | a | CO 4 | Study and analyze the behaviour of FET and MOSFET. | Remember |
| | b | CO 4 | Study and analyze the behaviour of FET and MOSFET. | Understand |
| 9 | a | CO 5 | Analyze FET amplifiers in CS,CG,CD modes using small signal model and study the behaviour of special purpose diodes. | Understand |
| | b | CO 5 | Analyze FET amplifiers in CS,CG,CD modes using small signal model and study the behaviour of special purpose diodes. | Remember |
| 10 | a | CO 5 | Analyze FET amplifiers in CS,CG,CD modes using small signal model and study the behaviour of special purpose diodes. | Understand |
| | b | CO 5 | Analyze FET amplifiers in CS,CG,CD modes using small signal model and study the behaviour of special purpose diodes. | Understand |

Signature of Course Coordinator

HOD, ECE