

INSTITUTE OF AERONAUTICAL ENGINEERING (Autonomous) Dundigal, Hyderabad -500 043

LINEAR AND DIGITAL IC APPLICATIONS

Prepared by

1. Mr. D Kalandar Basha, Associate Professor

2. Mr. B Naresh, Assistant Professor

3. Mr. N NAGARAJU, Assistant professor

Course Contents

- Unit 1 Operational Amplifier
- Unit 2 OP-Amp,IC555 & IC565 Applications
- Unit 3 Data Converters
- Unit 4 Digital Integrated circuits
- Unit 5 Sequential Logic IC's & Memories

Text Books:

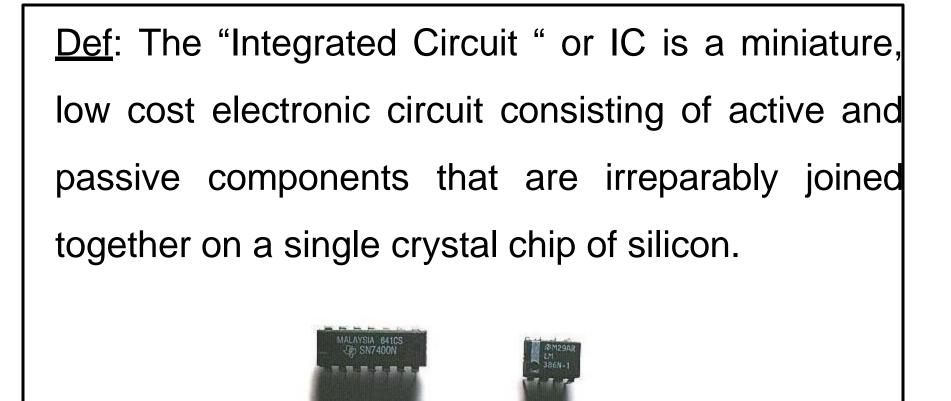
- 1. Linear Integrated Circuits D. Roy Choudhury
- 2. Op-Amps & Linear ICs Ramakanth A. Gayakwad.
- 3. Digital Fundamentals Floyd and Jain





Unit 1- Integrated Circuits

- What is an Integrated Circuit?
- Where do you use an Integrated Circuit?
- Why do you prefer an Integrated Circuit to the circuits made by interconnecting discrete components?



In 1958 Jack Kilby of Texas Instruments invented first IC





Applications of an Integrated Circuit


- Communication
- Control
- Instrumentation
- Computer
- Electronics





Advantages:

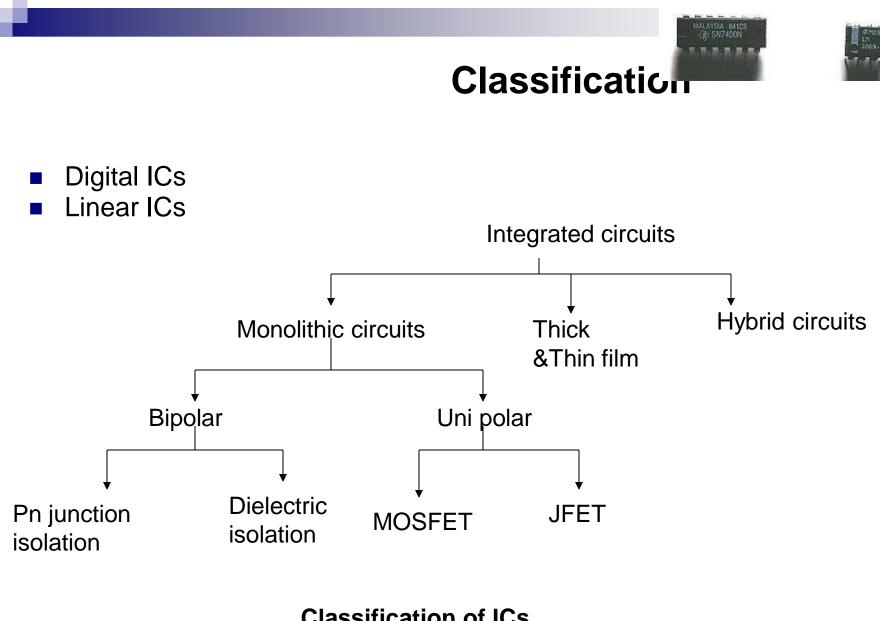- Small size
- Low cost
- Less weight
- Low supply voltages
- Low power consumption
- Highly reliable
- Matched devices
- Fast speed



Classification of ICs





Chip size and Complexity

- Invention of Transistor (Ge)
- **Development of Silicon**
- Silicon Planar Technology
- First ICs, SSI (3- 30gates/chip)
- MSI (30-300 gates/chip) - 1965-1970
- LSI (300-3000 gates/chip) -1970 - 1975
- VLSI (More than 3k gates/chip) - 1975
- ULSI (more than one million active devices are integrated on single chip)

- 1947
- 1955-1959
- 1959
- 1960

SSI	MSI	LSI	VLSI	ULSI
< 100 active devices	100-1000 active devices	1000- 100000 active devices	>100000 active devices	Over 1 million active devices
Integrated resistors, diodes & BJT's	BJT's and Enhanced MOSFETS	MOSFETS	8bit, 16bit Microproces sors	Pentium Microproces sors

Selection of IC Package

Туре	Criteria	
Metal can package	 Heat dissipation is important For high power applications like power amplifiers, voltage regulators etc. 	
DIP	 For experimental or bread boarding purposes as easy to mount If bending or soldering of the leads is not required Suitable for printed circuit boards as lead spacing is more 	
Flat pack	 More reliability is required Light in weight Suited for airborne applications 	

Factors affecting selection of IC package

- Relative cost
- Reliability
- Weight of the package
- Ease of fabrication
- Power to be dissipated
- Need of external heat sink





Temperature Ranges

- 1. Military temperature range $:-55^{\circ}$ C to $+125^{\circ}$ C (-55° C to $+85^{\circ}$ C)
- 2. Industrial temperature range : -20° C to +85° C (-40° C to +85° C)
- 3. Commercial temperature range: 0° C to +70° C (0° C to +75° C)

The operational amplifier (Op-Amp) is a multiterminal device which internally is quite complex.

Operational Amplifier

An "Operational amplifier" is a direct coupled high-gain amplifier usually consisting of one or more differential amplifiers and usually followed by a level translator and output stage.

The operational amplifier is a versatile device that can be used to amplify dc as well as ac input signals and was originally designed for computing such mathematical functions as addition, subtraction, multiplication and integration.


Basic Information of Op-Amp


Op-amps have five basic terminals, that is, two input terminals, one output terminal and two power supply terminals.

Packages



The metal can (TO) Package

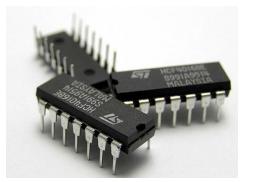

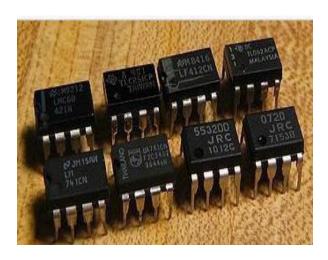



The Flat Package

The Dual-in-Line (DIP)

Package

Basic Information of an Op-amp contd...

Power supply connection:

The power supply voltage may range from about \pm 5V to \pm 22V.

The common terminal of the V⁺ and V⁻ sources is connected to a reference point or ground.

Manufacturer's Designation for Linear ICs

- Fairchild
- National Semiconductor
- Motorola
- RCA
- Texas Instruments
- Signetics
- Burr- Brown

- μΑ, μΑF
- LM,LH,LF,TBA
- MC,MFC
- CA,CD
- SN
- N/S,NE/SE
- BB

Fairchild's original µA741 is also manufactured by other manufactures as follows

- National Semiconductor LM741
- Motorola MC1741
- RCA CA3741
- Texas Instruments SN52741
- Signetics N5741

- 741Military grade op-amp
- 741C Commercial grade op-amp
- 741A Improved version of 741
- 741E Improved version of 741C
- 741S Military grade op-amp with higher slew rate
- **741SC** Commercial grade op-amp with higher slew rate

Differential Amplifier

$$V_{0} = A_{d} (V_{1} - V_{2})$$

$$A_{d} = 20 \log_{10} (A_{d}) \text{ in } dB$$

$$V_{c} = \underbrace{(V_{1} + V_{2})}_{2}$$

$$CMRR = \rho = | \begin{array}{c} 2 \\ |A_{d} \\ A_{c} \end{array}$$

Characteristics and performance parameters of Op-amp

- Input offset Voltage
- Input offset current
- Input bias current
- Differential input resistance
- Input capacitance
- Open loop voltage gain
- CMRR
- Output voltage swing

Characteristics and performance parameters of Opamp

- Output resistance
- Offset adjustment range
- Input Voltage range
- Power supply rejection ratio
- Power consumption
- Slew rate
- Gain Bandwidth product
- Equivalent input noise voltage and current

Characteristics and performance parameters of Opamp

- Average temperature coefficient of offset parameters
- Output offset voltage
- Supply current

1. Input Offset Voltage

The differential voltage that must be applied between the two input terminals of an op-amp, to make the output voltage zero.

It is denoted as V_{ios}

For op-amp 741C the input offset voltage is 6mV

2. Input offset current

The algebraic difference between the currents flowing into

the two input terminals of the op-amp

It is denoted as
$$I_{ios} = |I_{b1} - I_{b2}|$$

For op-amp 741C the input offset current is 200nA

3. Input bias current

The average value of the two currents flowing

into the op-amp input terminals

It is expressed mathematically as

$$\frac{I_{b1} + I_{b2}}{2}$$

For 741C the maximum value of I_b is 500nA

4. Differential Input Resistance

It is the equivalent resistance measured at either the

inverting or non-inverting input terminal with the other

input terminal grounded

It is denoted as R_i

For 741C it is of the order of $2M\Omega$

5. Input capacitance

It is the equivalent capacitance measured at either the inverting or non- inverting input terminal with the other input terminal grounded.

It is denoted as C_i

For 741C it is of the 1-4 pF

6. Open loop Voltage gain

It is the ratio of output voltage to the differential input voltage, when op-amp is in open loop configuration, without any feedback. It is also called as large signal

voltage gain

It is denoted as A_{OL}

$$A_{OL} = V_o / V_d$$

For 741C it is typically 200,000

7. CMRR

It is the ratio of differential voltage gain $A_d\,$ to common mode voltage gain $A_c\,$

$$CMRR = A_d / A_c$$

 A_d is open loop voltage gain A_{OL} and A_c = V_{OC} / V_c

For op-amp 741C CMRR is 90 dB

8. Output Voltage swing

The op-amp output voltage gets saturated at +V_{cc} and – V_{EE} and it cannot produce output voltage more than +V_{cc} and –V_{EE}. Practically voltages +V_{sat} and –V_{sat} are slightly less than +V_{cc} and –V_{EE}.

For op-amp 741C the saturation voltages are \pm 13V for supply voltages \pm 15V

9. Output Resistance

It is the equivalent resistance measured between the output

terminal of the op-amp and ground

It is denoted as R_o

For op-amp 741 it is 75Ω

10. Offset voltage adjustment range

The range for which input offset voltage can be adjusted using the potentiometer so as to reduce output to zero

For op-amp 741C it is <u>+</u> 15mV

11. Input Voltage range

It is the range of common mode voltages which can be applied for which op-amp functions properly and given offset specifications apply for the op-amp

For $\pm 15V$ supply voltages, the input voltage range is $\pm 13V$

12. Power supply rejection ratio

PSRR is defined as the ratio of the change in input offset voltage due to the change in supply voltage producing it, keeping the other power supply voltage constant. It is also called as power supply sensitivity (PSV)

 $PSRR = (\Delta v_{ios} / \Delta V_{cc}) | constant V_{EE} \qquad PSRR = (\Delta v_{ios} / \Delta V_{EE}) | constant V_{cc}$

The typical value of PSRR for op-amp 741C is 30μ V/V

13. Power Consumption

It is the amount of quiescent power to be consumed by op-

amp with zero input voltage, for its proper functioning

It is denoted as P_c

For 741C it is 85mW

14. Slew rate

It is defined as the maximum rate of change of output voltage with time. The slew rate is specified in V/µsec

Slew rate =
$$S = dV_o / dt |_{max}$$

It is specified by the op-amp in unity gain condition.

The slew rate is caused due to limited charging rate of the compensation capacitor and current limiting and saturation of the internal stages of op-amp, when a high frequency large amplitude signal is applied.

Slew rate

It is given by $dV_c/dt = I/C$

For large charging rate, the capacitor should be small or the current should be large.

$$S = I_{max} / C$$

For 741 IC the charging current is 15 μ A and the internal capacitor is 30 pF. S= 0.5V/ μ sec

Slew rate equation

$$\frac{dVo}{dt} = V_{m} \omega \cos \omega t$$

$$\frac{dVo}{S = slew rate} = \frac{\frac{dVo}{dt}}{dt} \max$$

 $S = V_m \omega = 2 \pi f V_m$

 $V_s = V_m sin\omega t$

 $V_o = V_m \sin \omega t$

 $S = 2 \pi f V_m V / sec$

For distortion free output, the

maximum allowable input

This is also called **full power bandwidth** of the

op-amp

frequency
$$f_m$$
 can be obtained as

$$f_m = \frac{S}{2 \Pi V_m}$$

15. Gain – Bandwidth product

It is the bandwidth of op-amp when voltage gain is unity (1). It is denoted as GB.

The GB is also called unity gain bandwidth (UGB) or closed loop bandwidth

It is about 1MHz for op-amp 741C

16. Equivalent Input Noise Voltage and Current

The noise is expressed as a power density

Thus equivalent noise voltage is expressed as V²/Hz while the equivalent noise current is expressed as A^2 /Hz

17. Average temperature coefficient of offset parameters

The average rate of change of input offset voltage per unit change in temperature is called average temperature coefficient of input offset voltage or input offset voltage drift

It is measured in μ V/°C. For 741 C it is 0.5 μ V/°C

The average rate of change of input offset current per unit change in temperature is called average temperature coefficient of input offset current or input offset current drift


It is measured in nA/°C or pA/°C . For 741 C it is 12 pA/°C

18. Output offset voltage (V_{oos})


The output offset voltage is the dc voltage present at the output terminals when both the input terminals are grounded.

It is denoted as V_{oos}


Factors affecting parameters of Op-amp

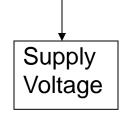

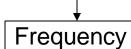- 1. Voltage gain
- 2. Output Voltage swing
- 3. Input voltage range
- 4. Power consumption
- 5. Input offset current



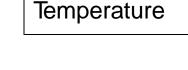- 1. Voltage gain
- 2. Input resistance
- 3. Output resistance
- 4. CMRR
- 5. Input noise voltage
- 6. Input noise current



- 1. Input offset current
- 2. Input offset voltage
- 3. Input bias current
- 4. Power consumption
- 5. Gain-Bandwidth product
- 6. Slew rate
- 7. Input resistance

Parameter consideration for various applications

For A.C. applications	For D.C. applications
Input resistance	Input resistance
Output resistance	Output resistance
Open loop voltage gain	Open loop voltage gain
Slew rate	Input offset voltage
Output voltage swing	Input offset current
Gain- bandwidth product	Input offset voltage and current drifts
Input noise voltage and current	
Input offset voltage and current drifts	

Absolute Maximum Ratings of Op-amp

Maximum power dissipation: This is the maximum power which can be dissipated, in the internal stages of the op-amp in the form of heat

Operating temperature range: As specified in the data sheet, op-amp can work satisfactorily, over the operating temperature range, as required for the given application

Absolute Maximum Ratings of Op-amp

Maximum supply voltage: This is the maximum d.c. supply voltage which can be applied to the op-amp

Maximum differential input voltage: This rating gives the maximum value of difference between the two input voltages, applied to the two input terminals of the opamp

Absolute Maximum Ratings of Op-amp

Maximum common mode input voltage: This is the maximum value of the input voltage which can be simultaneously applied to the two input terminals

Storage temperature range: This gives the temperature range over which the op-amp can be stored safely.

Op-amp characteristics dependent on the power supply voltages

- Absolute maximum power supply voltage
- Absolute maximum differential input voltages
- Absolute maximum common mode input voltage

Ideal Op-amp

1.An ideal op-amp draws no

current at both the input terminals

I.e. $I_1 = I_2 = 0$. Thus its input


impedance is infinite. Any source

- can drive it and there is no loading 2. The gain of an ideal op-amp is infinite, hence the on the driver stage differential input $V_d = V_1 - V_2$ is essentially zero for the finite output voltage V_0
- The output voltage V_o is independent of the current drawn from the output terminals. Thus its output impedance is zero and hence output can drive an infinite number of other circuits

The Ideal Operational Amplifier

A_{OL} Open loop voltage gain $= \infty$ R_i Input Impedance $= \infty$ R_{o} **Output Impedance** = 0BW Bandwidth $= \infty$ Zero offset ($V_0 = 0$ when $V_1 = V_2 = 0$) V_{ios} = 0**CMRR** ρ ∞ Slew rate S **=** ∞ No effect of temperature Power supply rejection ratio PSRR = 0

Ideal Voltage transfer curve

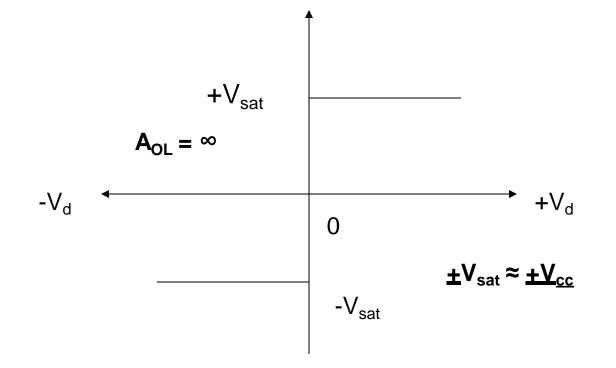

Practical voltage transfer curve

- 1. If V_d is greater than corresponding to b, the output attains + V_{sat}
- 2. If V_d is less than corresponding to a, the output attains $-V_{sat}$
- Thus range a-b is input range for which output varies linearily with the input. But A_{OL} is very high, practically
- this range is very small

Equivalent circuit of practical op-amp

- A_{OL} = Large signal open loop voltage gain
- V_d = Difference voltage $V_1 V_2$
- V_1 = Non-inverting input voltage with respect to ground
- V₂ = Inverting input voltage with respect to ground
- R_i = Input resistance of op-amp
- R_o = Output resistance of op-amp

Transient Response Rise time

When the output of the op-amp is suddenly changing like pulse type, then the rise time of the response depends on the cut-off frequency f_H of the op-amp. Such a rise time is called cut-off frequency limited rise time or transient response rise time (t_r)

$$t_r = \frac{0.35}{f_H}$$

Op-amp Characteristics

DC Characteristics

Input bias current Input offset current Input

offset voltage Thermal drift

AC Characteristics

Slew rate Frequency response

DC Characteristics Thermal Drift

The op-amp parameters input offset voltage V_{ios} and input offset current I_{ios} are not constants but vary with the factors

- 1. Temperature
- 2. Supply Voltage changes
- 3. Time

Thermal Voltage Drift

It is defined as the average rate of change of input offset voltage per unit change in temperature. It is also called as input offset voltage drift


Input offset voltage drift =
$$\frac{\Delta V_{ios}}{\Delta T}$$

 ΔV_{ios} = change in input offset voltage ΔT = Change in temperature



- not uniform over specified operating temperature range.
- The value of input offset voltage may increase or

decrease with the increasing temperature

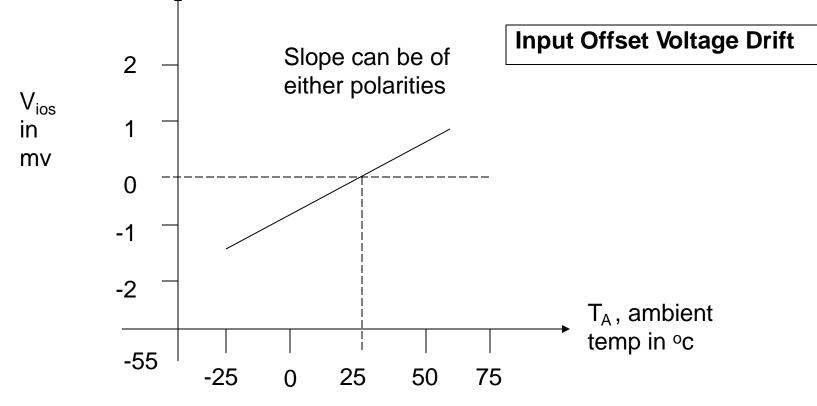


Input bias current drift

It is defined as the average rate of change of input bias

current per unit change in temperature

Thermal drift in input bias current =
$$\frac{\Delta I_b}{\Delta T}$$

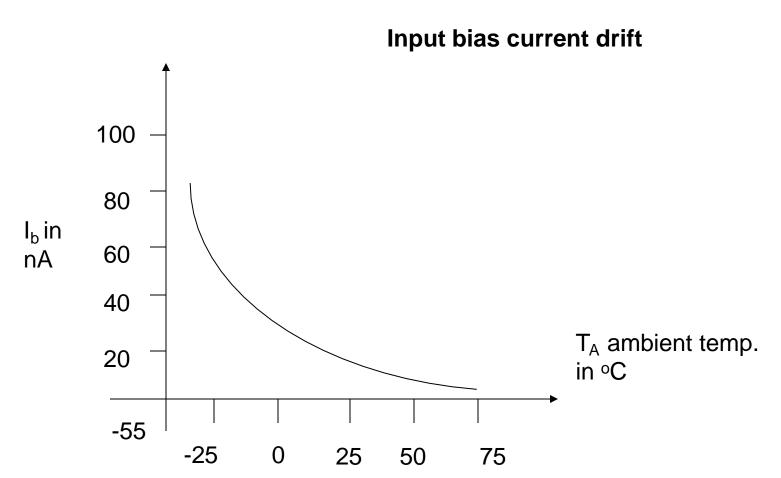It is measured in nA/°C or pA/°c. These parameters vary randomly with temperature. i.e. they may be positive in one temperature range and negative in another




Input Offset current drift

It is defined as the average rate of change of input offset current per unit change in temperature

Thermal drift in input offset current = $\frac{\Delta I_{ios}}{\Delta T}$

It is measured in nA/°C or pA/°c. These parameters vary randomly with temperature. i.e. they may be positive in one temperature range and negative in another

Input Offset current Drift

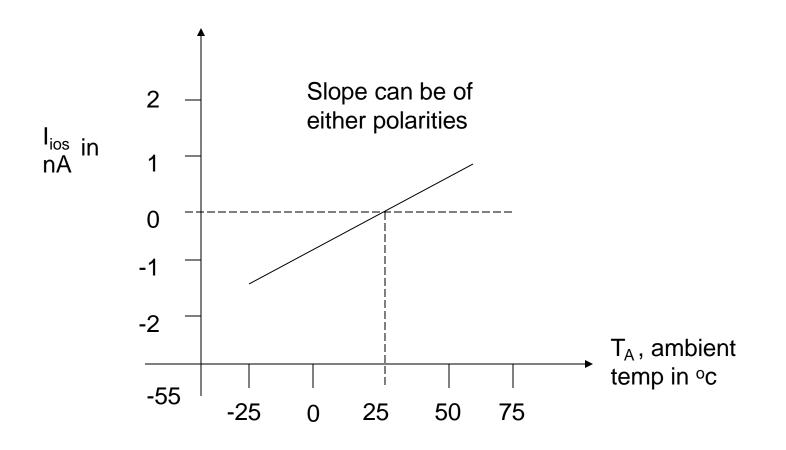

AC Characteristics

Frequency Response

Ideally, an op-amp should have an infinite bandwidth but practically opamp gain decreases at higher frequencies. Such a gain reduction with respect to frequency is called as roll off.

The plot showing the variations in magnitude and phase angle of the gain due to the change in frequency is called *frequency response* of the op-amp When the gain in decibels, phase angle in degrees are plotted against logarithmic scale of frequency, the plot is called **Bode Plot**

The manner in which the gain of the op-amp changes with variation in frequency is known as the *magnitude plot*.

The manner in which the phase shift changes with variation

in frequency is known as the *phase-angle plot*.

Obtaining the frequency response

To obtain the frequency response, consider the high frequency model of the op-amp with capacitor C at the output, taking into account the

capacitive effect present

$$A_{OL}(f) = \frac{A_{OL}}{1 + j2\Pi f R_o C}$$
$$A_{OL}(f) = \frac{A_{OL}}{1 + j(-f)}$$

Where


 $A_{OL}(f)$ = open loop voltage gain as a function of frequency

 A_{OL} = Gain of the op-amp at 0Hz F =

operating frequency


 $F_{o=}$ Break frequency or cutoff frequency of op-amp

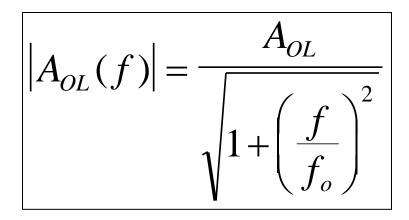For a given op-amp and selected value of C, the frequency f_o is constant. The above equation can be written in the polar form as



$$\angle A_{OL}(f) = \Phi(f) = -\tan^{-1}\left(\frac{f}{f_0}\right)$$

Frequency Response of an op-amp

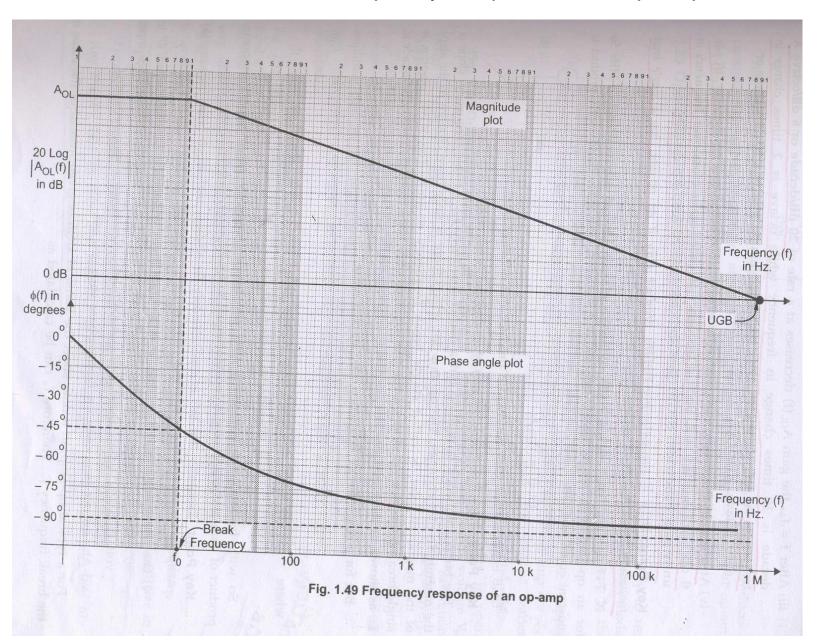

The following observations can be made from the frequency response of an op-amp

i) The open loop gain A_{OL} is almost constant from 0 Hz to the break frequency $f_{o\,.}$

ii) At f=f_o, the gain is 3dB down from its value at 0Hz. Hence the frequency f_o is also called as -3dB frequency. It is also know as corner frequency iii) After f=f_o, the gain A_{OL} (f) decreases at a rate of 20 dB/decade or 6dB/octave. As the gain decreases, slope of the magnitude plot is - 20dB/decade or -6dB/octave, after f=f_o.

iv)At a certain frequency, the gainreduces to 0dB. This means $20\log|A_{OL}|$ is0dB i.e. $|A_{OL}| = 1$. Such a frequency is called gain cross-over frequency orunity gain bandwidth (UGB). It is also called closed loop bandwidth.

UGB is the gain bandwidth product only if an op-amp has a single breakover frequency, before A_{OL} (f) dB is zero.

For an op-amp with single break frequency f_o , after f_o the gain bandwidth product is constant equal to UGB

UGB is also called gain bandwidth product and denoted as f_t Thus f_t is the product of gain of op-amp and bandwidth. The break frequency is nothing but a corner frequency f_o . At this

frequency, slope of the magnitude plot changes. The op-amp for which there is only once change in the slope of the magnitude plot, is called single break frequency op-amp. For a single break frequency we can also write

 $UGB = A_f f_f$

 A_f = closed loop voltage gain F_f =

bandwidth with feedback

v) The phase angle of an op-amp with single break frequency varies between 0° to 90°. The maximum possible phase shift is -90°, i.e. output voltage lags input voltage by 90°when phase shift is maximum

vi) At a corner frequency $f=f_o$, the phase shift is -45^{0.} $F_o = UGB / A_{OL}$

requency f in Hz	A _{OL} (f) in dB = 20 log $\frac{A_{OL}}{\sqrt{1 + \left(\frac{f}{f_o}\right)^2}}$ in dB	$\phi (\mathbf{f}) = -\tan^{-1}\left(\frac{\mathbf{f}}{\mathbf{f}_0}\right)$
		in degrees
0	106.02 dB	0°
5	103.01 dB	– 45°
10	99.03 dB	
100	79.98 dB	- 63.43°
1000		– 87.13°
100	60.00 dB	- 89.71°
100 × 10 ³	20.00 dB	- 89.99°
1×10 ⁶	0 dB	- 89.999°

The modes of using an op-amp

- Open Loop : (The output assumes one of the two possible output states, that is +V_{sat} or V_{sat} and the amplifier acts as a switch only).
- Closed Loop: (The utility of an op-amp can be greatly increased by providing negative feed back. The output in this case is not driven into saturation and the circuit behaves in a linear manner).

Open loop configuration of op-amp

- The voltage transfer curve indicates the inability of opamp to work as a linear small signal amplifier in the open loop mode
- Such an open loop behaviour of the op-amp finds some rare applications like voltage comparator, zero crossing detector etc.

Open loop op-amp configurations

- The configuration in which output depends on input, but output has no effect on the input is called open loop configuration.
- No feed back from output to input is used in such configuration.
- The opamp works as high gain amplifier
- The op-amp can be used in three modes in open loop configuration they are
- 1. Differential amplifier
- 2. Inverting amplifier
- 3. Non inverting amplifier

Differential Amplifier

The amplifier which amplifies the difference between the two input voltages is called differential amplifier.

$$V_{o} = A_{OL}V_{d} = A_{OL}(V_{1} - V_{2}) = A_{OL}(V_{in1} - V_{in2})$$

Key point: For very small V_d , output gets driven into saturation due to high A_{OL} , hence this application is applicable for very small range of differential input voltage.

Inverting Amplifier

The amplifier in which the output is inverted i.e. having 180° phase shift with respect to the input is called an inverting amplifier

$$V_o = -A_{OL}V_{in2}$$

Keypoint: The negative sign indicates that there is phase shift of 180° between input and output i.e. output is inverted with respect to input.

Non-inverting Amplifier


The amplifier in which the output is amplified without any phase shift in between input and output is called non inverting amplifier

$$V_o = A_{OL} V_{in1}$$

Keypoint: The positive output shows that input and output are in phase and input is amplified A_{OL} times to get the output.

Why op-amp is generally not used in open loop mode?

As open loop gain of op-amp is very large, very small input voltage drives the op-amp voltage to the saturation level. Thus in open loop configuration, the output is at its positive saturation voltage $(+V_{sat})$ or negative saturation voltage ($-V_{sat}$) depending on which input V₁ or V₂ is more than the other. For a.c. input voltages, output may switch between positive and negative saturation voltages

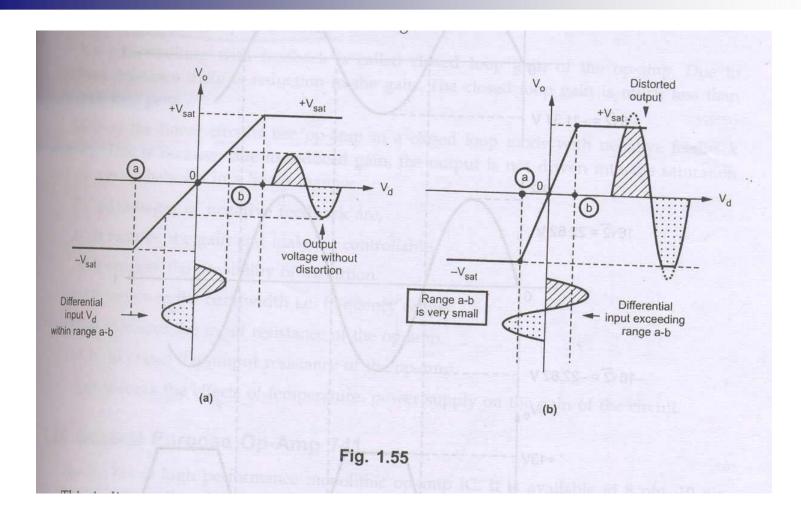

This indicates the inability of op-amp to work as a linear small signal amplifier in the open loop mode. Hence the op-amp in open loop configuration is not used for the linear applications


General purpose op-amp 741

The IC 741 is high performance monolithic op-amp IC. It is available in 8pin, 10pin or 14pin configuration. It can operate over a temperature of -55° C to 125° C.

Features:


- i) No frequency compensation required
- ii) Short circuit protection provided
- iii) Offset Voltage null capability
- iv) Large common mode and differential voltage range
- v) No latch up

Internal schematic of 741 op-amp

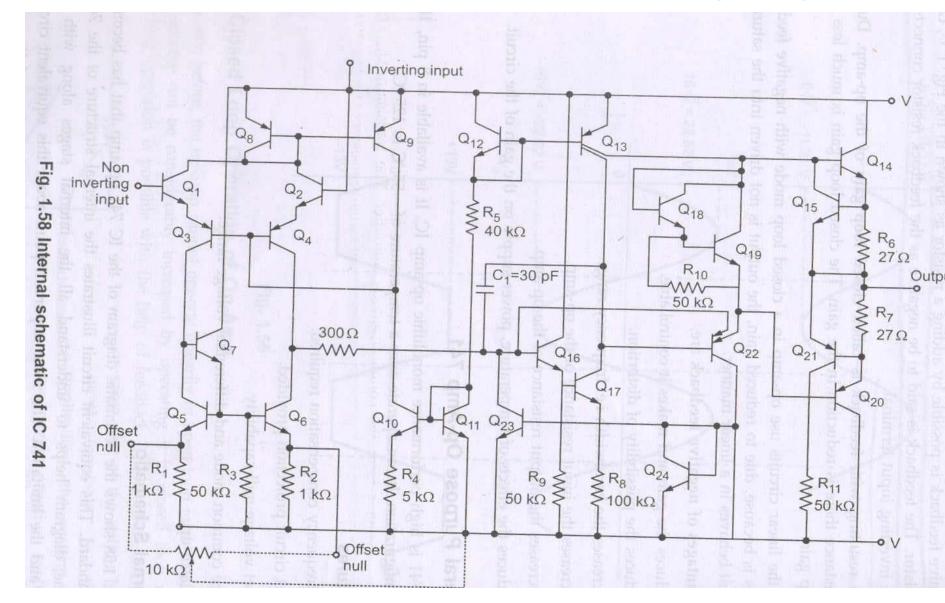

The 8pin DIP package of IC 741

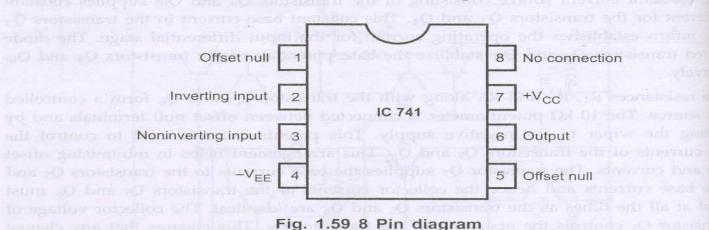The 8 pin DIP package of IC 741 is shown in the Fig. 1.59.



1.26.3 Ideal Vs Practical Characteristics of IC 741 Op-Amp

The Table 1.7 lists the ideal op-amp characteristics and the typical characteristics 741 IC, a popular general purpose op-amp IC.

Sr. No	Parameter	Symbol	Ideal	Typical for 741 IC
1	Open loop voltage gain	A _{OL}	∞	2×10^{5}
2	Output impedance	Zout	0	75 Ω
3	Input impedance	Zin	00	2 MΩ
4	Input offset current	I _{ios}	0 dela	20 nA
5	Input offset voltage	Vios	0	1 mV
6	Bandwidth	B.W *	00	1 MHz
7	CMRR	ρ	ant contraction	90 dB
8	Slew rate	S	œ	0.5 V/µsec
9	Input bias current	Ib	0	80 nA
10	PSRR	PSRR	0	30 μV/V

Realistic simplifying assumptions

 Zero input current: The current drawn by either of the input terminals (inverting and non-inverting) is zero

Virtual ground :This means the differential input voltage
 V_d between the non-inverting and inverting terminals is
 essentially zero. (The voltage at the non inverting input
 terminal of an op-amp can be realistically assumed to be
 equal to the voltage at the inverting input terminal

Closed loop operation of op-amp

The utility of the op-amp can be increased considerably by operating in closed loop mode. The closed loop operation is possible with the help of feedback. The feedback allows to feed some part of the output back to the input terminals. In the linear applications, the opamp is always used with negative feedback. The negative feedback helps in controlling gain, which otherwise drives the op-amp out of its linear range, even for a small noise voltage at the input terminals

Ideal Inverting Amplifier

- 1. The output is inverted with respect to input, which is indicated by minus sign.
- 2. The voltage gain is independent of open loop gain of the op-amp, which is assumed to be large.
- 3. The voltage gain depends on the ratio of the two resistances. Hence selecting R_f and R_1 , the required value of gain can be easily obtained.
- 4. If $R_f > R_{1,}$, the gain is greater than 1 If $R_f < R_{1,}$, the gain is less than 1
- If $R_{f} = R_1$, the gain is unity

Thus the output voltage can be greater than, less than or equal to the input voltage in magnitude

- 5. If the ratio of R_f and R_1 is K which is other than one, the circuit is called scale changer while for $R_f/R_1 = 1$ it is called phase inverter.
- 6. The closed loop gain is denoted as A_{VF} or A_{CL} i.e. gain with feedback

Ideal Non-inverting Amplifier

- 1. The voltage gain is always greater than one
- ^{2.} The voltage gain is positive indicating that for a.c. input, the output and input are in phase while for d.c. input, the output polarity is same as that of input
- ^{3.} The voltage gain is independent of open loop gain of op-amp, but depends only on the two resistance values
- ^{4.} The desired voltage gain can be obtained by selecting proper values of R_f and R_1

Comparison of the ideal inverting and noninverting op-amp

Ideal Inverting amplifier	Ideal non-inverting amplifier		
1. Voltage gain=-R _f /R ₁	1. Voltage gain=1+R _f /R ₁		
2. The output is inverted with respect to input	2. No phase shift between input and output		
 The voltage gain can be adjusted as greater than, equal to or less than one 	3. The voltage gain is always greater than one		
4. The input impedance is R_1	4. The input impedance is very large		

Practical Inverting Amplifier

Closed Loop Voltage gain =

$$A_{CL} = -\frac{A_{OL}R_f}{R_1 + R_f + R_1A_{OL}}$$

Practical Non-Inverting Amplifier


Closed Loop Voltage gain =

$$A_{CL} = \frac{A_{OL}(R + R)}{\frac{OL}{R_1 + R_f} + R_1 A_{OL}}$$

Instrumentation Amplifier

In a number of industrial and consumer applications, the measurement of physical quantities is usually done with the help of transducers. The output of transducer has to be amplified So that it can drive the indicator or display system. This function is performed by an instrumentation amplifier


Instrumentation Amplifier

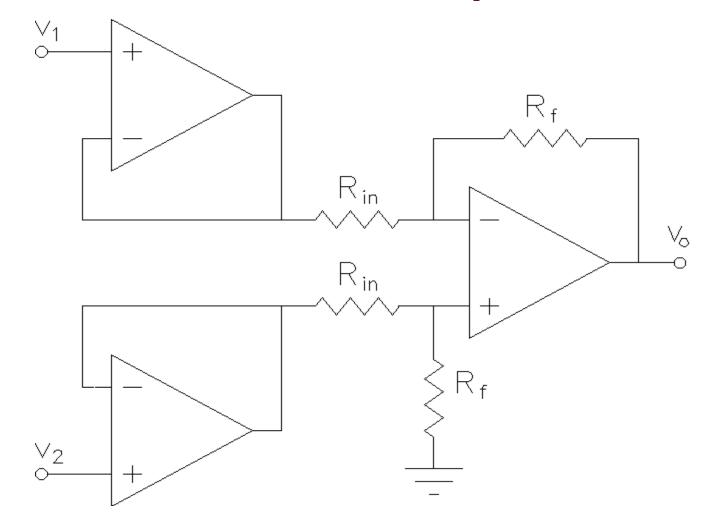


Features of instrumentation amplifier

- 1. high gain accuracy
- 2. high CMRR
- 3. high gain stability with low temperature coefficient
- 4. low dc offset
- 5. low output impedance


AC AMPLIFIER

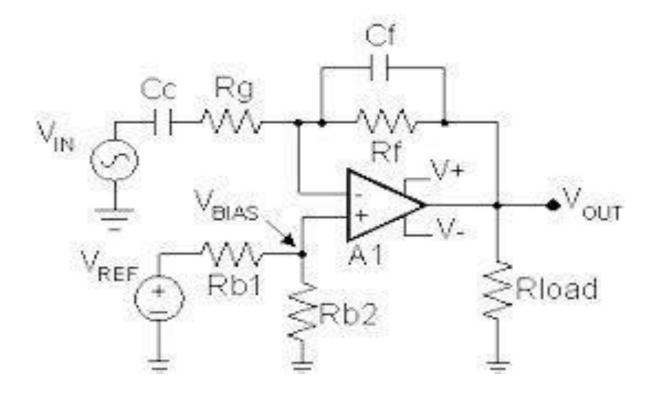



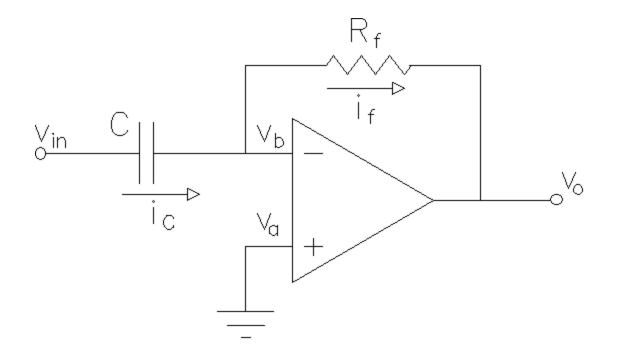




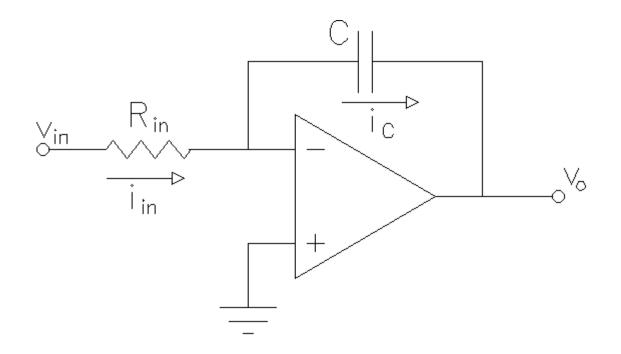

Differential amplifier

This circuit amplifies only the difference between the two inputs. In this circuit there are two resistors labeled R $_{\rm IN}$ Which means that their values are equal. The differential amplifier amplifies the difference of two inputs while the differentiator amplifies the slope of an input


Summer

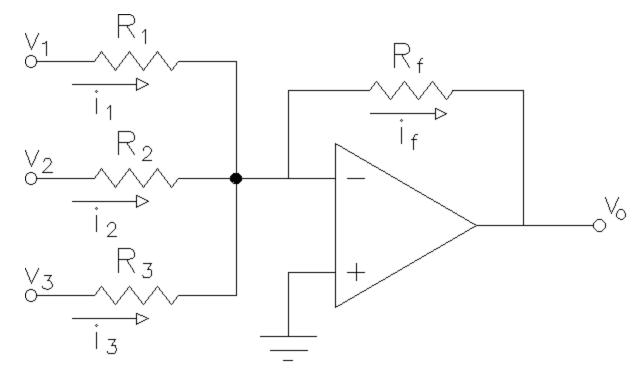

Comparator

A comparator is a circuit which compares a signal voltage applied at one input of an op- amp with a known reference voltage at the other input. It is an open loop op - amp with output + Vsat


Comparator

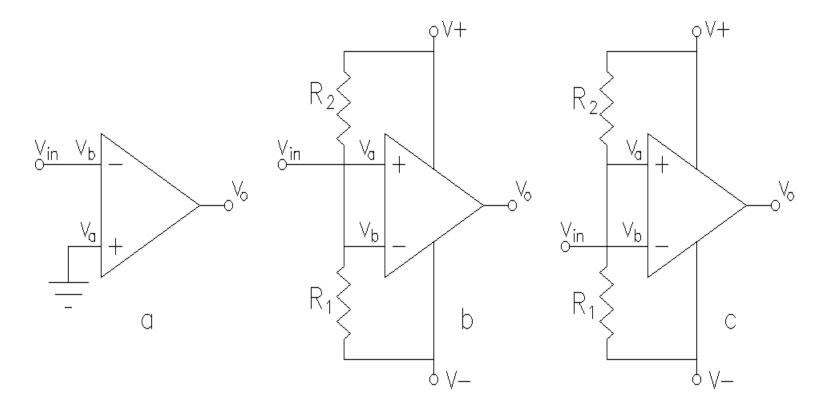

Applications of comparator

- 1. Zero crossing detector
- 2. Window detector
- 3. Time marker generator
- 4. Phase detector

Schmitt trigger

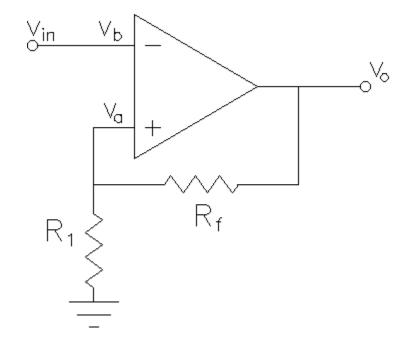

INTRODUCTION TO VOLTAGE REGULATORS


A voltage regulator is designed to automatically maintain a constant voltage level. A voltage regulator may be a simple "feed-forward" design or may include negative feedback control loops. It may use an electromechanical mechanism, or electronic components.

IC Voltage Regulators

There are basically two kinds of IC voltage regulators:
 Multipin type, e.g. LM723C
 3-pin type, e.g. 78/79XX

- Multipin regulators are less popular but they provide the greatest flexibility and produce the highest quality voltage regulation
- 3-pin types make regulator circuit design simple

Multipin IC Voltage Regulator

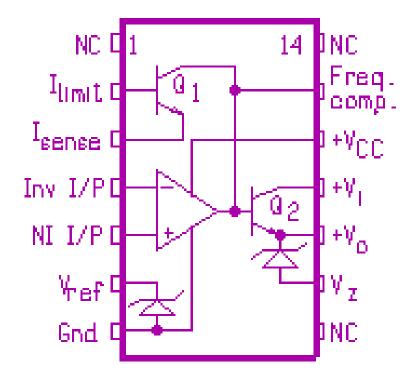


- The LM723 has an equivalent circuit that contains most of the parts of the op-amp voltage regulator discussed earlier.
- It has an internal voltage reference, error amplifier, pass transistor, and current limiter all in one IC package.
 LM 723C Schematic

LM723 Voltage Regulator

- Can be either 14-pin DIP or 10-pin TO-100 can
- May be used for either +ve or -ve, variable or fixed regulated voltage output
- Using the internal reference (7.15 V), it can operate as a high-voltage regulator with output from 7.15 V to about 37 V, or as a low-voltage regulator from 2 V to 7.15 V
- Max. output current with heat sink is 150 mA
- Dropout voltage is 3 V (i.e. $V_{CC} > V_{o(max)} + 3$)

LM723 in High-Voltage Configuration

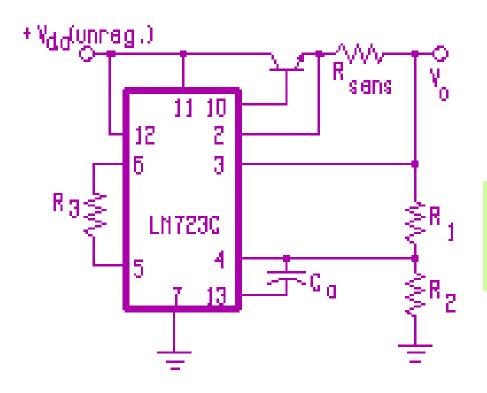



External pass transistor and current sensing added.

Design equations: V (R + R) $V_o = \frac{ref \ 1 \ 2}{R_2}$ $R_3 = \frac{R_1 R_2}{R_1 + R_2}$ $R_{sens} = \frac{0.7}{I_{max}}$

Choose $R_1 + R_2 = 10$ k Ω , and $C_c = 100$ pF. To make V_o variable, replace R_1 with a pot.

LM723 in Low-Voltage Configuration

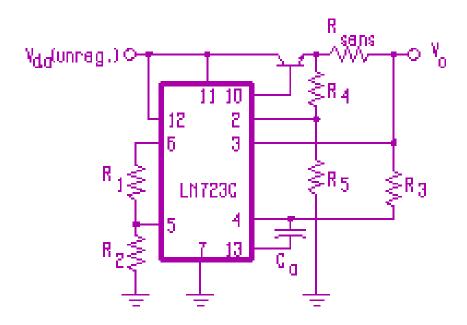

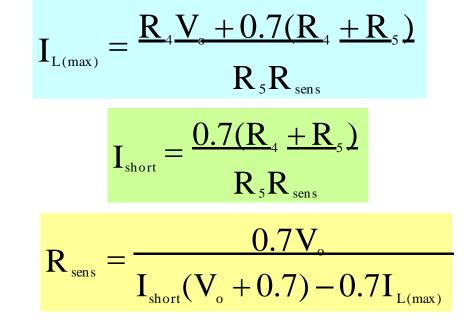

With external pass transistor and foldback current limiting

$$\mathbf{V}_{o} = \frac{\mathbf{R}_{2}\mathbf{V}_{ref}}{\mathbf{R}_{1} + \mathbf{R}_{2}}$$


Under foldback condition:

$$V_{o}' = \frac{0.7R_{L}(R_{4} + R_{5})}{R_{5}R_{sens} - R_{4}R_{L}}$$

Three-Terminal Fixed Voltage Regulators


- Less flexible, but simple to use
- Come in standard TO-3 (20 W) or TO-220 (15 W) transistor packages
- 78/79XX series regulators are commonly available with
- 5, 6, 8, 12, 15, 18, or 24 V output
- Max. output current with heat sink is 1 A
- Built-in thermal shutdown protection
- 3-V dropout voltage; max. input of 37 V
- Regulators with lower dropout, higher in/output, and better regulation are available.

Basic Circuits With 78/79XX Regulators

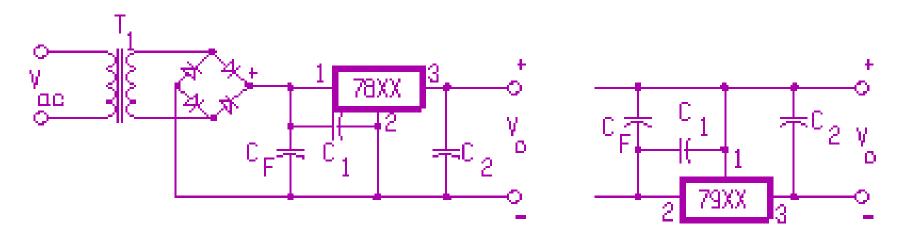


- Both the 78XX and 79XX regulators can be used to provide +ve or -ve output voltages
- C₁ and C₂ are generally optional. C₁ is used to cancel any inductance present, and C₂ improves the transient response. If used, they should preferably be either 1 μF tantalum type or 0.1 μF mica type capacitors.

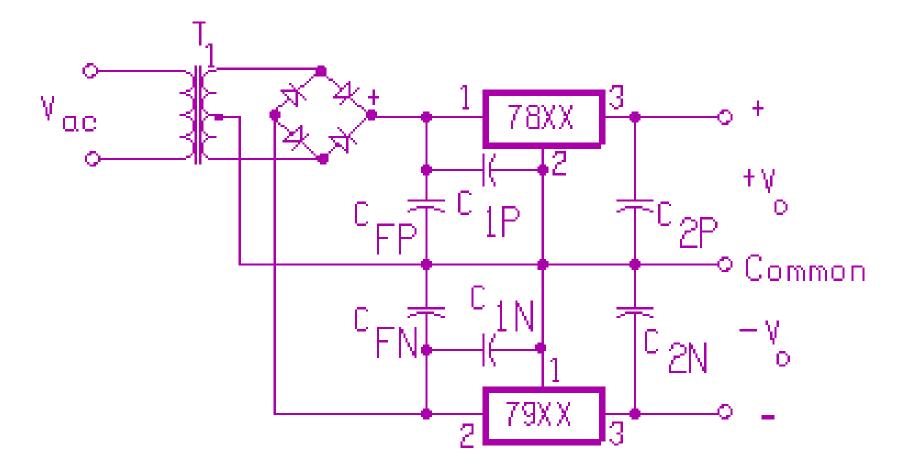Dual-Polarity Output with 78/79XX Regulators




78XX Regulator with Pass Transistor

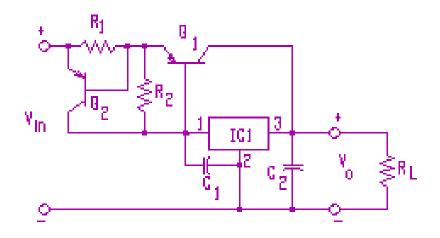

$$R_1 = \frac{0.7}{I_{\text{max}}}$$
 $R_2 = \frac{0.7}{I_{R2}}$

- Q_1 starts to conduct when $V_{R2} = 0.7 V.$
- R2 is typically chosen so that max. I_{R2} is 0.1 A.
- Power dissipation of Q_1 is $P = (V_i - V_o)I_L$.
- Q_2 is for current limiting protection. It conducts when $V_{R1} = 0.7$ V.
- Q₂ must be able to pass max. 1 A; but note that max. V_{CE2} is only 1.4 V.

78XX Floating Regulator

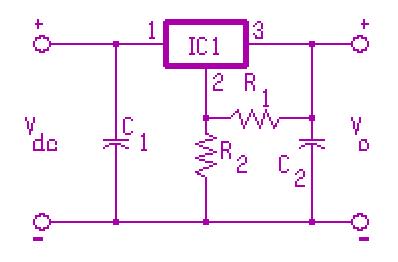


$$V_o = V_{reg} + \left(\frac{V_{reg}}{R_1} + I_Q\right) R_2$$

- It is used to obtain an output > the V_{reg} value up to a max.of 37 V.
- R_1 is chosen so that $R_1 \stackrel{>}{\rightarrow} 0.1 V_{reg}/I_Q$, where I is the

3-Terminal Variable Regulator

- The floating regulator could be made into a variable regulator by replacing R₂ with a pot. However, there are several disadvantages:
 - \Box Minimum output voltage is V_{reg} instead of 0 V.
 - \Box I_Q is relatively large and varies from chip to chip.
 - \Box Power dissipation in R₂ can in some cases be quite large resulting in bulky and expensive equipment.
- A variety of 3-terminal variable regulators are available,
 e.g. LM317 (for +ve output) or LM 337 (for -ve output).

Basic LM317 Variable Regulator Circuits

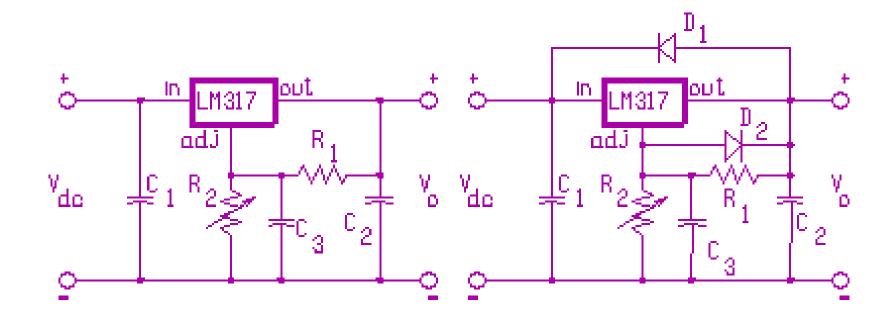

(a) Circuit with capacitors to improve performance (b) Circuit with protective diodes

Notes on Basic LM317 Circuits

- The function of C₁ and C₂ is similar to those used in the 78/79XX fixed regulators.
- C₃ is used to improve ripple rejection.
- Protective diodes in circuit (b) are required for highcurrent/high-voltage applications.


$$V_o = V_{ref} + \left(\frac{V_{ref}}{R_1} + I_{adj}\right)R_2$$


$$R_2 = \frac{R (V - V)}{V_{ref} + I_{adj}R_1}$$

where $V_{ref} = 1.25$ V, and I_{adj} is the current flowing into the adj. terminal (typically 50 μ A).

 $R_1 = V_{ref} / I_{L(min)}$, where $I_{L(min)} i_S$ typically 10 mA.

LM317 Regulator Circuits

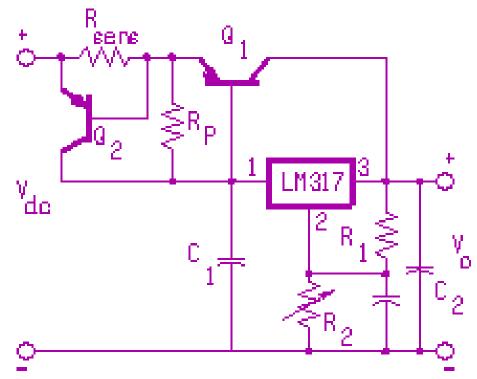

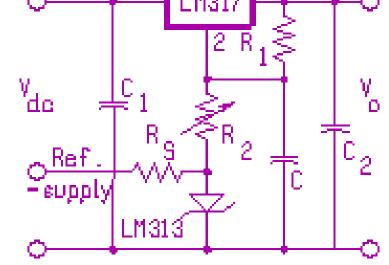

Circuit with pass transistor and current limiting Circuit to give 0V min. output voltage

UNIT –II

Opamp -555IC-565 applications

Filter

Filter is a frequency selective circuit that passes signal of specified Band of frequencies and attenuates the signals of frequencies outside the band

Type of Filter

- **1.** Passive filters
- 2. Active filters

Passive filters

Passive filters works well for high frequencies. But at audio frequencies, the inductors become problematic, as they become large, heavy and expensive.For low frequency applications, more number of turns of wire must be used which in turn adds to the series resistance degrading inductor's performance ie, low Q, resulting in high power dissipation

Active filters

Active filters used op- amp as the active element and resistors and capacitors as passive elements. By enclosing a capacitor in the feed back loop , inductor less active filters can be obtained

some commonly used active filters

- 1. Low pass filter
- 2. High pass filter
- 3. Band pass filter
- 4. Band reject filter
- 5. All pass filter

Active Filters

Active filters use op-amp(s) and RC components.

- Advantages over passive filters:
 - □ op-amp(s) provide gain and overcome circuit losses
 - □ increase input impedance to minimize circuit loading
 - higher output power

□ sharp cutoff characteristics can be produced simply and efficiently without bulky inductors

 Single-chip universal filters (e.g. switched-capacitor ones) are available that can be configured for any type of filter or response.

Review of Filter Types & Responses


- 4 major types of filters: low-pass, high-pass, band pass, and band-reject or band-stop
- 0 dB attenuation in the passband (usually)
- 3 dB attenuation at the *critical* or *cutoff frequency*, f_c (for Butterworth filter)
- Roll-off at 20 dB/dec (or 6 dB/oct) per *pole* outside the passband (# of poles = # of reactive elements). Attenuation at any frequency f is:

atten.(dB) at
$$f = \log\left(\frac{f}{f_c}\right) x$$
 atten.(dB) at f_{dec}


Review of Filters (cont'd)

- Bandwidth of a filter: BW = f_{cu} f_{cl}
- Phase shift: 45°/pole at f_c; 90°/pole at >> f_c
- 4 types of filter responses are commonly used:
 - Butterworth maximally flat in passband; highly nonlinear phase response with frequecny
 - □ Bessel gentle roll-off; linear phase shift with freq.
 - Chebyshev steep initial roll-off with ripples in passband
 - Cauer (or elliptic) steepest roll-off of the four types but has ripples in the passband and in the stopband

Frequency Response of Filters

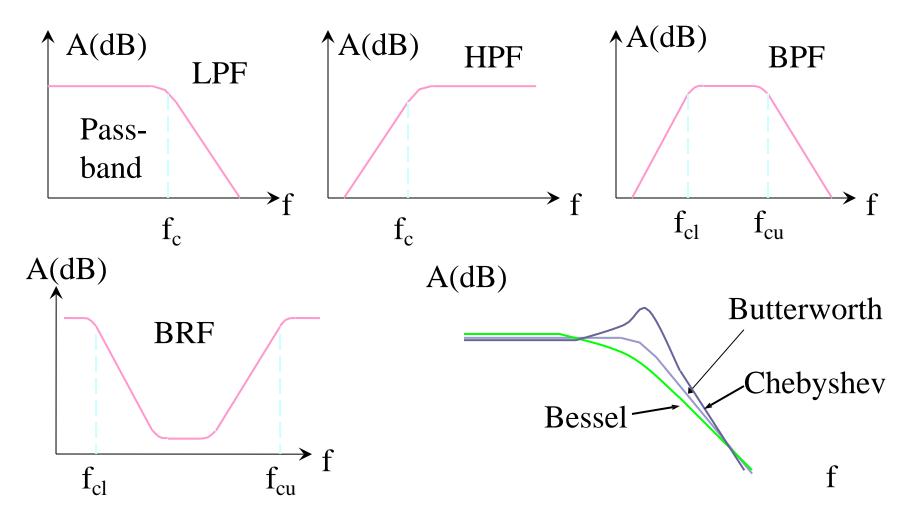

Unity-Gain Low-Pass Filter Circuits

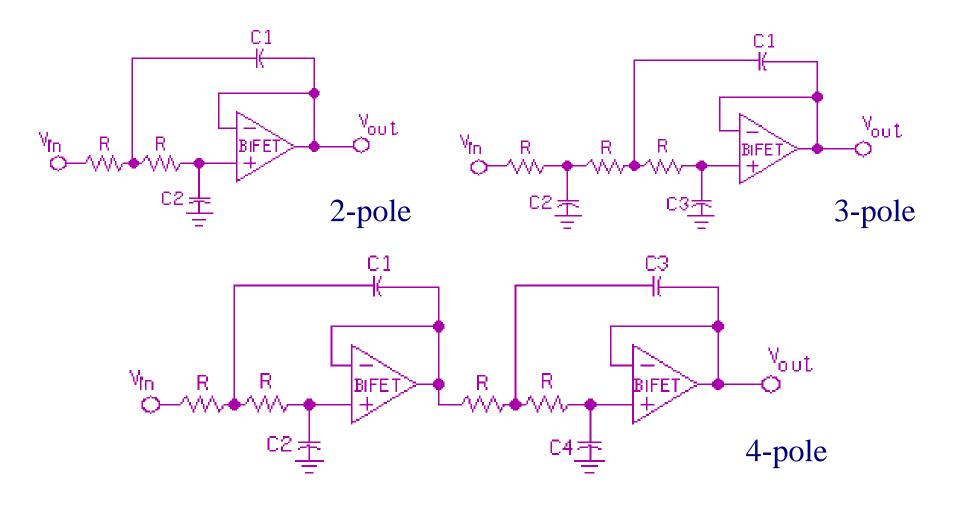

Design Procedure for Unity-Gain LPF

- * Determine/select number of poles required.
- In Calculate the frequency scaling constant, $K_f = 2\pi f$
- Divide normalized C values (from table) by K_f to obtain frequency-scaled C values.
- Select a desired value for one of the frequency-scaled C values and calculate the impedance scaling factor:

$$K_x = \frac{frequency - scaled C value}{desired C value}$$

 \oplus Divide all frequency-scaled C values by K_x \oplus Set R = K_x Ω

An Example

Design a unity-gain LP Butterworth filter with a critical frequency of 5 kHz and an attenuation of at least 38 dB at 15 kHz.


- The attenuation at 15 kHz is 38 dB
- \otimes the attenuation at 1 decade (50 kHz) = 79.64 dB.

We require a filter with a roll-off of f at least 4 poles. $K_f = 31,416 \text{ rad/s.}$ Let's pick $C_1 = 0.01 \ \mu\text{F}$ (or 10 nF). Then $C_2 = 8.54 \ n\text{F}$, $C_3 = 24.15 \ n\text{F}$, and $C_4 = 3.53 \ n\text{F}$. Pick standard values of 8.2 nF, 22 nF, and 3.3 nF. $K_x =$

3,444

Make all R = 3.6 k Ω (standard value)

Unity-Gain High-Pass Filter Circuits

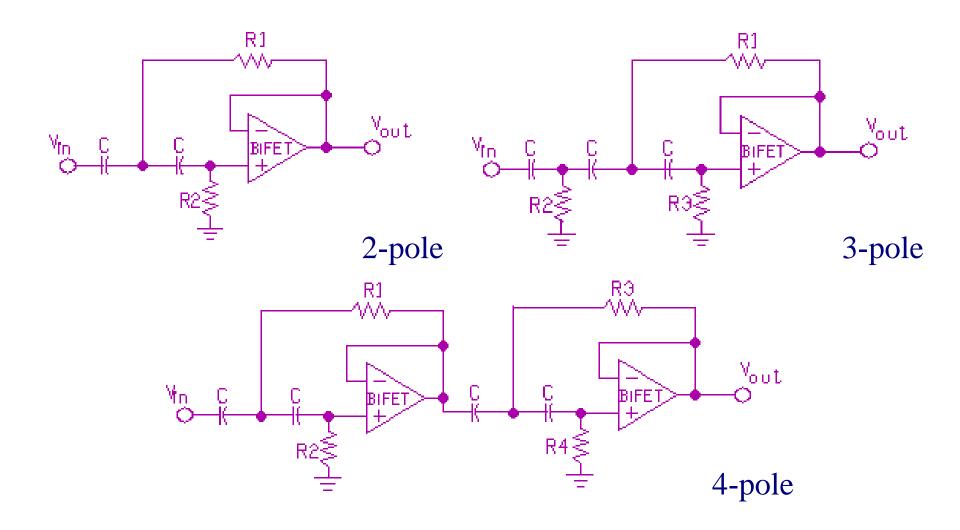


Design Procedure for Unity-Gain HPF

- The same procedure as for LP filters is used except for step #3, the normalized C value of 1 F is divided by K_f. Then pick a desired value for C, such as 0.001 μF to 0.1 μF, to calculate K_x. (Note that all capacitors have the same value).
- For step #6, multiply all normalized R values (from table) by K_x.

E.g. Design a unity-gain Butterworth HPF with a critical frequency of 1 kHz, and a roll-off of 55 dB/dec. (Ans.: C = 0.01 μ F, R₁ = 4.49 k Ω , R₂ = 11.43 k Ω , R₃ = 78.64 k Ω .; pick standard values of 4.3 k Ω , 11 k Ω , and 75 k Ω).

Equal-Component Filter Design

٧_{In}

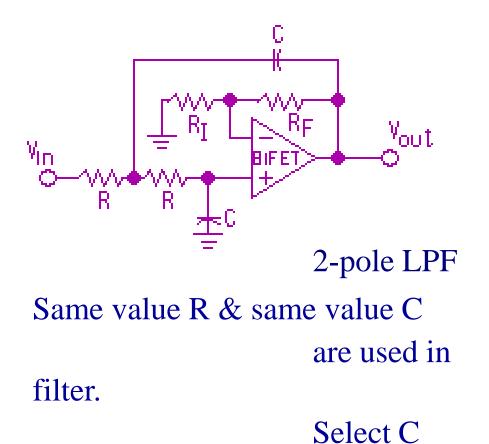

(e.g. 0.01 μ F), then:

 $A_{v} \text{ for } \# \text{ of poles is given in} \\ a \text{ table and} \\ \text{is the same for} \\ A_{F} = \frac{R_{F}}{R_{I}} + 1 P \text{ and HP} \\ \text{filter } \frac{A_{F}}{R_{I}} = \frac{R_{F}}{R_{I}} + 1 P \text{ and HP} \\ \text{filter } \frac{R_{F}}{R_{I}} = \frac{R_{F}}{R_{I}} + 1 P \text{ and HP} \\ \text{filter } \frac{R_{F}}{R_{I}} = \frac{R_{F}}{R_{I}} + 1 P \text{ and HP} \\ \text{filter } \frac{R_{F}}{R_{I}} = \frac{R_{F}}{R_{I}} + 1 P \text{ and HP} \\ \text{filter } \frac{R_{F}}{R_{I}} = \frac{R_{F}}{R_{I}} + 1 P \text{ and HP} \\ \text{filter } \frac{R_{F}}{R_{I}} = \frac{R_{F}}{R_{I}} + 1 P \text{ and HP} \\ \text{filter } \frac{R_{F}}{R_{I}} = \frac{R_{F}}{R_{I}} + 1 P \text{ and HP} \\ \text{filter } \frac{R_{F}}{R_{I}} = \frac{R_{F}}{R_{I}} + 1 P \text{ and HP} \\ \text{filter } \frac{R_{F}}{R_{I}} = \frac{R_{F}}{R_{I}} + 1 P \text{ and HP} \\ \text{filter } \frac{R_{F}}{R_{I}} = \frac{R_{F}}{R_{I}} + 1 P \text{ and HP} \\ \text{filter } \frac{R_{F}}{R_{I}} = \frac{R_{F}}{R_{I}} + 1 P \text{ and HP} \\ \text{filter } \frac{R_{F}}{R_{I}} = \frac{R_{F}}{R_{I}} + 1 P \text{ and HP} \\ \text{filter } \frac{R_{F}}{R_{I}} = \frac{R_{F}}{R_{I}} + 1 P \text{ and HP} \\ \text{filter } \frac{R_{F}}{R_{I}} = \frac{R_{F}}{R_{I}} + 1 P \text{ and HP} \\ \text{filter } \frac{R_{F}}{R_{I}} = \frac{R_{F}}{R_{I}} + 1 P \text{ and HP} \\ \text{filter } \frac{R_{F}}{R_{I}} = \frac{R_{F}}{R_{I}} + 1 P \text{ and HP} \\ \text{filter } \frac{R_{F}}{R_{I}} = \frac{R_{F}}{R_{I}} + 1 P \text{ and HP} \\ \text{filter } \frac{R_{F}}{R_{I}} = \frac{R_{F}}{R_{I}} + 1 P \text{ and HP} \\ \text{filter } \frac{R_{F}}{R_{I}} = \frac{R_{F}}{R_{I}} + 1 P \text{ and HP} \\ \text{filter } \frac{R_{F}}{R_{I}} = \frac{R_{F}}{R_{I}} + 1 P \text{ and HP} \\ \text{filter } \frac{R_{F}}{R_{I}} = \frac{R_{F}}{R_{I}} + 1 P \text{ and HP} \\ \text{filter } \frac{R_{F}}{R_{I}} = \frac{R_{F}}{R_{I}} + 1 P \text{ and HP} \\ \frac{R_{F}}{R_{I}} = \frac{R_{F}}{R_{I}} + 1 P \text{ and HP} \\ \frac{R_{F}}{R_{I}} = \frac{R_{F}}{R_{I}} + 1 P \text{ and HP} \\ \frac{R_{F}}{R_{I}} = \frac{R_{F}}{R_{I}} + 1 P \text{ and HP} \\ \frac{R_{F}}{R_{I}} = \frac{R_{F}}{R_{I}} + 1 P \text{ and HP} \\ \frac{R_{F}}{R_{I}} = \frac{R_{F}}{R_{I}} + 1 P \text{ and HP} \\ \frac{R_{F}}{R_{I}} = \frac{R_{F}}{R_{I}} + 1 P \text{ and HP} \\ \frac{R_{F}}{R_{I}} = \frac{R_{F}}{R_{I}} + 1 P \text{ and HP} \\ \frac{R_{F}}{R_{I}} = \frac{R_{F}}{R_{I}} + 1 P \text{ and HP} \\ \frac{R_{F}}{R_{I}} = \frac{R_{F}}{R_{I}} + 1 P \text{ and HP} \\ \frac{R_{F}}{R_{I}} = \frac{R_{F}}{R_{I}}$

C


Y_{out}

Example

Design an equal-component LPF with a critical frequency of 3 kHz and a roll-off of 20 dB/oct.

Select standard values: 5.1 k Ω , 1.5 k Ω , and 12 k Ω .

Bandpass and Band-Rejection Filter

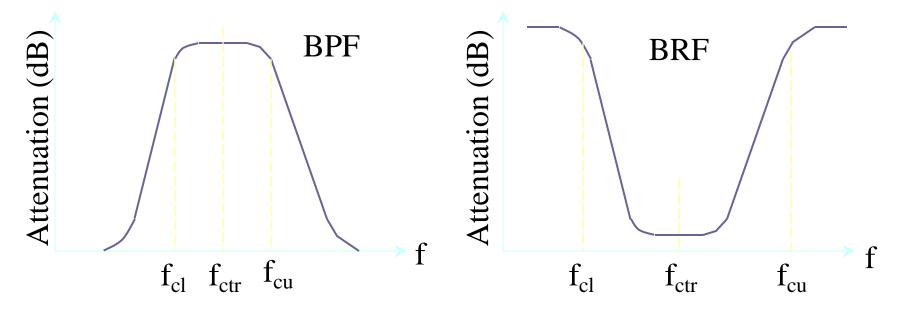

<u>J</u> ctr

BW

The quality factor, Q, of a filter is given by:

where $BW = f_{cu} - f_{cl}$ and

$$f_{ctr} = \sqrt{f_{cu} f_{cl}}$$


More On Bandpass Filter

If BW and f_{centre} are given, then:
A broadband BPF can be obtained by combining a LPF and
a HPF:

$$f_{cl} = \sqrt{\frac{BW^2}{4} + f_{ctr}^2} - \frac{BW}{2}$$
; $f_{cu} = \sqrt{\frac{BW^2}{4} + f_{ctr}^2} + \frac{BW}{2}$


> 1.

The Q of this filter is usually

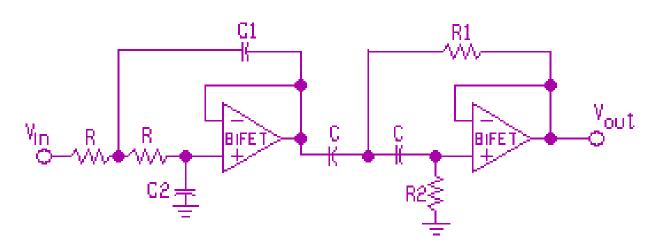


Broadband Band-Reject Filter

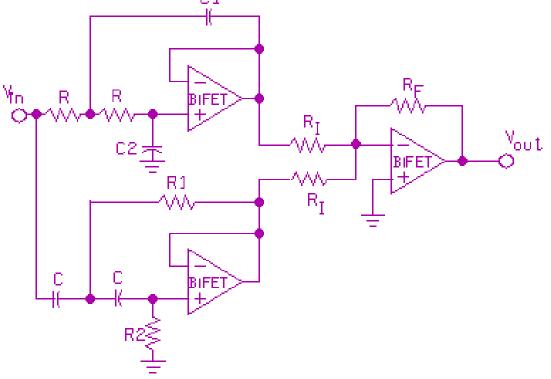A LPF and a HPF can also be combined to give a broadband BRF: \Box_{μ}^{1}




2-pole band-reject filter

Narrow-band Bandpass Filter

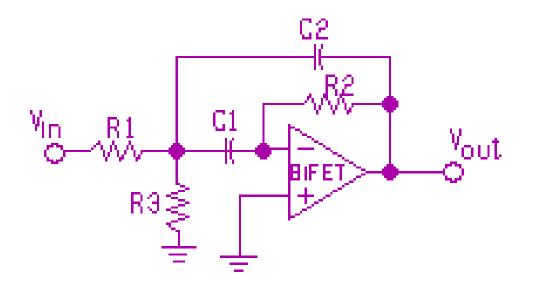

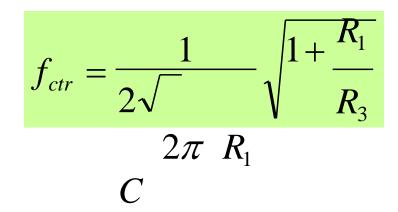
$$BW = \frac{f_{ctr}}{Q} = \frac{1}{1}$$
$$C1 = C2 = C^{2\pi} R_1$$
$$R_2 = 2 \Re_1$$
$$R_3 = \frac{R_1}{2Q^2 - 1}$$



 R_3 can be adjusted or trimmedto change f ctrthe BW.Q < 1.


Narrow-band Band-Reject Filter

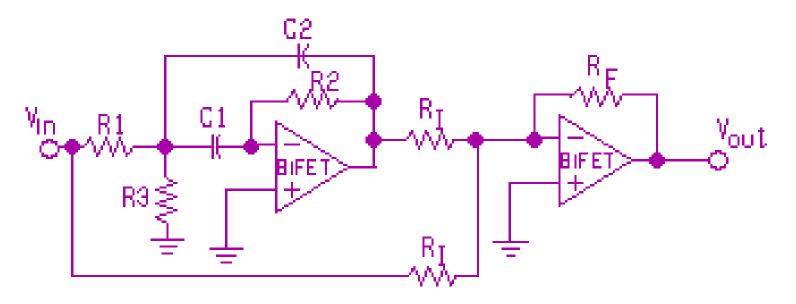Easily obtained by combining the inverting output of a narrow-band BRF and the original signal:




The equations for R1, R2, R3, C1, and C2 are the same as before. $R_I = R_F$ for unity gain and is often chosen to be >> R1.

TRIANGULAR WAVE GENERATOR

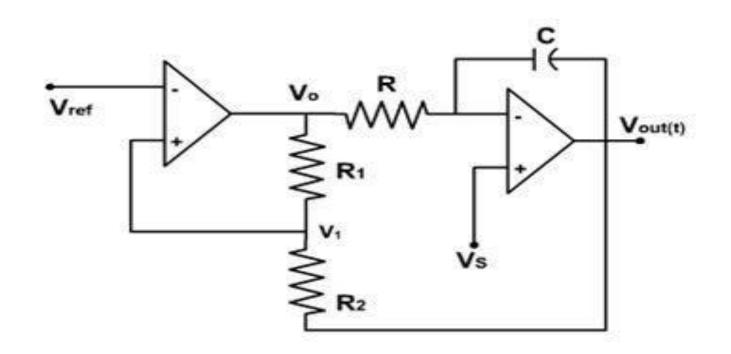

555 IC

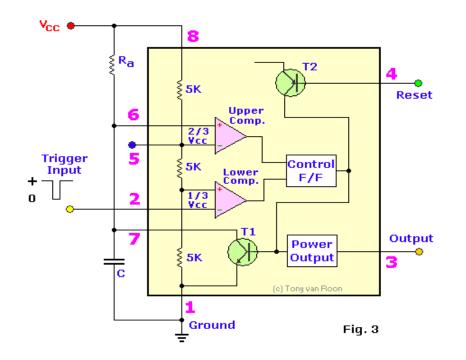The 555 timer is an integrated circuit specifically designed to perform signal generation and timing functions.



Features of 555 Timer Basic blocks


- 1. It has two basic operating modes: monostable and astable
- It is available in three packages. 8 pin metal can , 8 pin dip, 14 pin dip.
- 3. It has very high temperature stability

Applications of 555 Timer

- 1. astable multivibrator
- 2. monostable multivibrator
- 3. Missing pulse detector
- 4. Linear ramp generator
- 5. Frequency divider
- 6. Pulse width modulation
- 7. FSK generator
- 8. Pulse position modulator
- 9. Schmitt trigger

Astable multivibrator

.

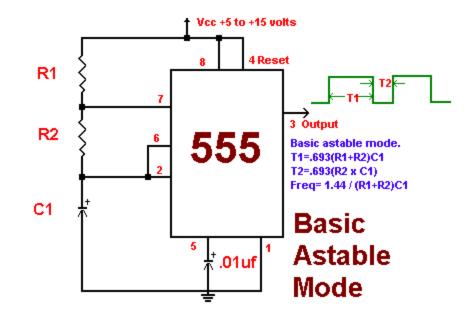


Astable multivibrator

When the voltage on the capacitor reaches (2/3)Vcc, a switch is closed at pin 7 and the capacitor is discharged to (1/3)Vcc, at which time the switch is opened and the cycle starts over

Monostable multivibrator

.

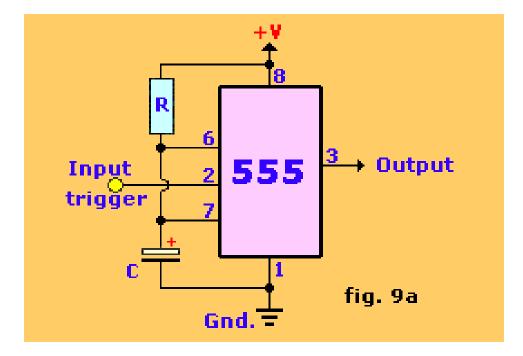

Voltage controlled oscillator

A voltage controlled oscillator is an oscillator circuit in which the frequency of oscillations can be controlled by an externally applied voltage

The features of 566 VCO

- 1. Wide supply voltage range(10- 24V)
- 2. Very linear modulation characteristics
- 3. High temperature stability



DATA CONVERTETRS

Classification of ADCs

- 1. Direct type ADC.
- 2. Integrating type ADC

Direct type ADCs

- 1. Flash (comparator) type converter
- 2. Counter type converter
- 3. Tracking or servo converter.
- 4. Successive approximation type converter

Integrating type converters

An ADC converter that perform conversion in an indirect manner by first changing the analog I/P signal to a linear function of time or frequency and then to a digital code is known as integrating type A/D converter


Digital Logic families

Overview

- Integration, Moore's law
- Early families (DL, RTL)
- TTL
- Evolution of TTL family
- ECL
- CMOS family and its evolution
- Overview


Integration Levels

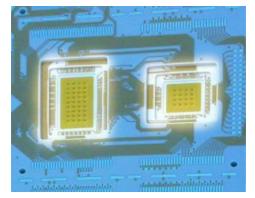- Gate/transistor ratio is roughly 1/10
 - SSI < 12 gates/chip
 - MSI < 100 gates/chip
 - LSI ...1K gates/chip
 - VLSI ...10K gates/chip
 - ULSI ...100K gates/chip
 - GSI ...1Meg gates/chip




Moore's law

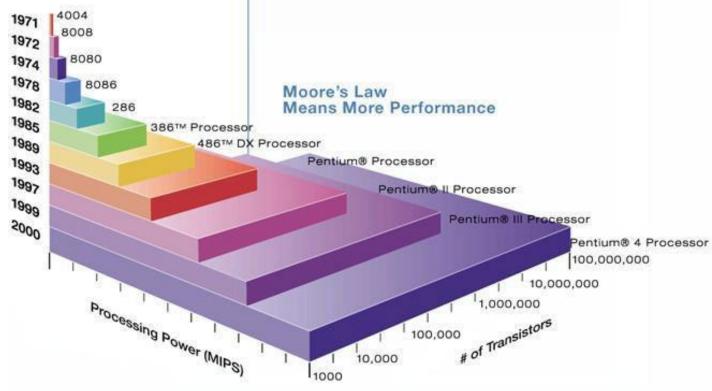
 A prediction made by Moore (a co-founder of Intel) in 1965: "... a number of transistors to double every 2 years."



In the beginning...

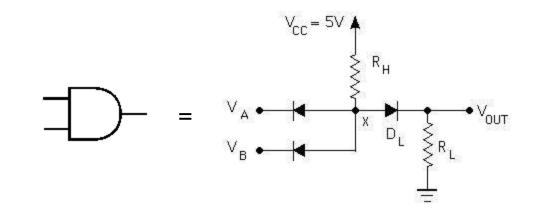Diode Logic (DL) simplest; does not scale NOT not possible (need an active e_Rl_ee_sm_{is}e_tn_ot_r)₋ Transistor Logic (RTL) replace diode switch with a transistor switch can be cascaded large power draw




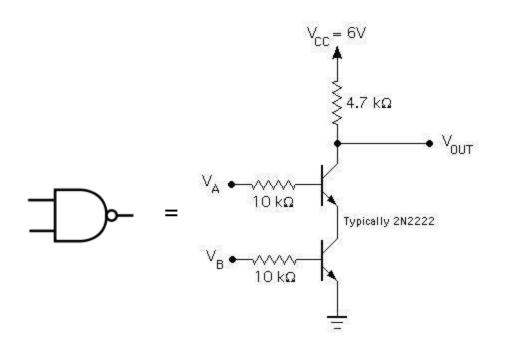



Diode-Transistor Logic (DTL)
•essentially diode logic with transistor amplification
•reduced power consumption

•faster than RTL

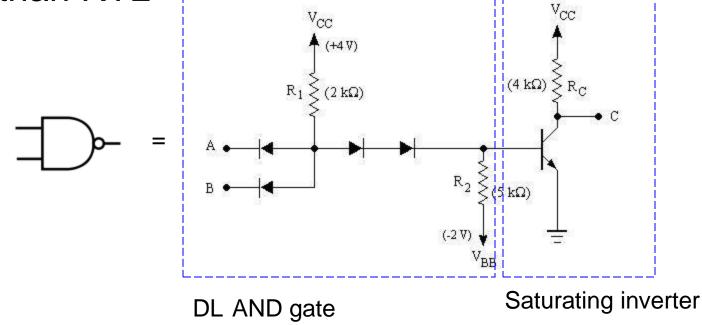


Logic families: V levels

 $V_{OH}(min)$ – The minimum voltage level at an output in the logical "1" state under defined load conditions

 $V_{OL}(max)$ – The maximum voltage level at an output in the logical "0" state under defined load conditions

 $V_{IH}(min)$ – The minimum voltage required at an input to be recognized as "1" logical state

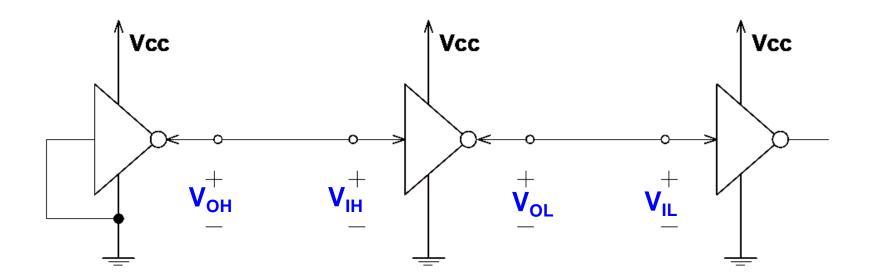 $V_{IL}(max)$ – The maximum voltage required at an input that still will be recognized as "0" logical state




Logic families: I requirements

 I_{OH} – Current flowing into an output in the logical "1" state under specified load conditions


 I_{OL} – Current flowing into an output in the logical "0" state under specified load conditions

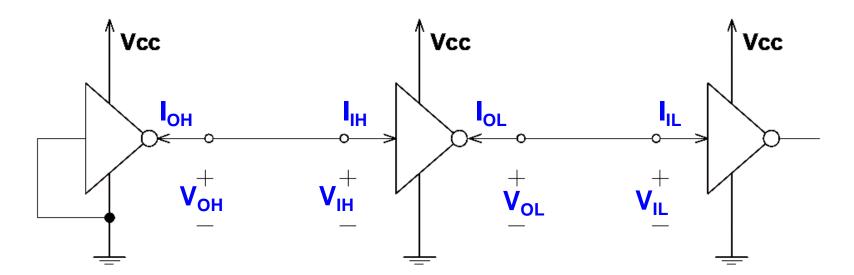 I_{IH} – Current flowing into an input when a specified HI level is applied to that input I_{IL} – Current flowing into an input when a specified LO level is applied to that input




Logic families: fanout

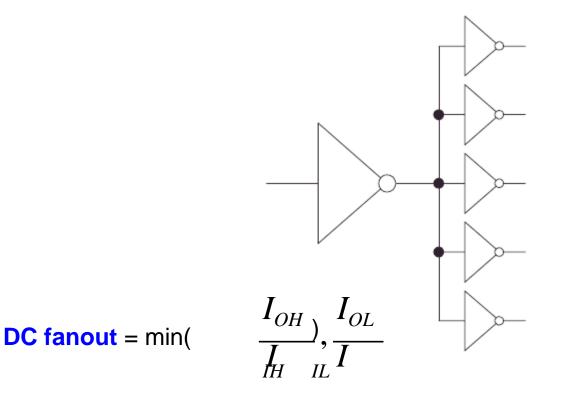Fanout: the maximum number of logic inputs (of the same logic family) that an output can drive reliably




Logic families: propagation delay

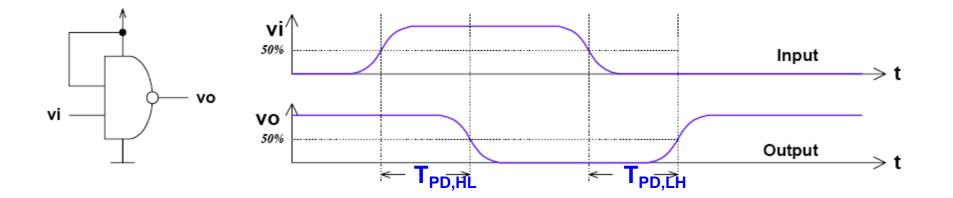

 $T_{PD,HL}$ – input-to-output propagation delay from HI to LO output $T_{PD,LH}$ – inputto-output propagation delay from LO to HI output

Speed-power product: $T_{PD} \times P_{avg}$

Logic families: noise margin

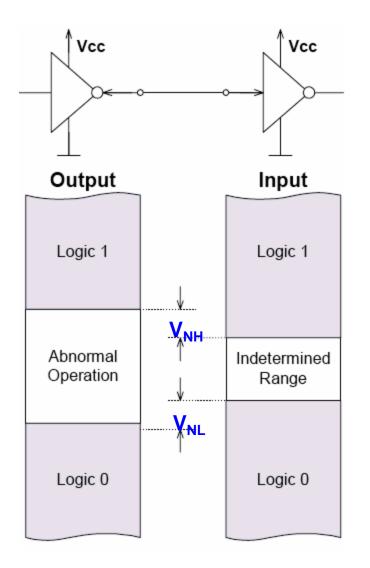

HI state noise margin: $V_{NH} = V_{OH}(min) - V_{IH}(min)$

LO state noise margin: $V_{NL} = V_{IL}(max) - V_{OL}(max)$


Noise margin: $V_N = min(V_{NH}, V_{NL})$

TTL

- Bipolar Transistor-Transistor Logic (TTL) • first introduced by in 1964 (Texas Instruments)
- •TTL has shaped digital technology in many ways
- Standard TTL family (e.g. 7400) is obsolet
- •Newer TTL families still used (e.g. 74ALS00)

Distinct features

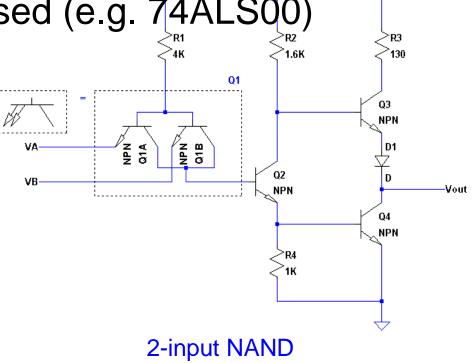
- Multi-emitter transistors
- Totem-pole transistor
 arrangement
- Open LTspice example: TTL NAND...




TTL evolution

Schottky series (74LS00) TTL

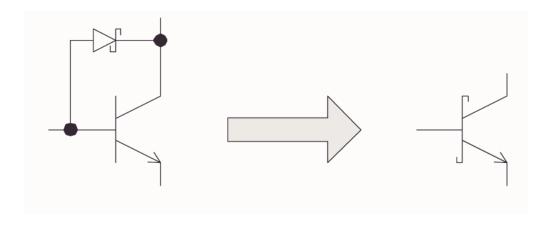- •A major slowdown factor in BJTs is due to transistors going in/out of saturation
- •Shottky diode has a lower forward bias (0.25V)
- •When BC junction would become forward biased,
- the Schottky diode bypasses the current
- preventing the transistor from going into saturation



TTL family evolution

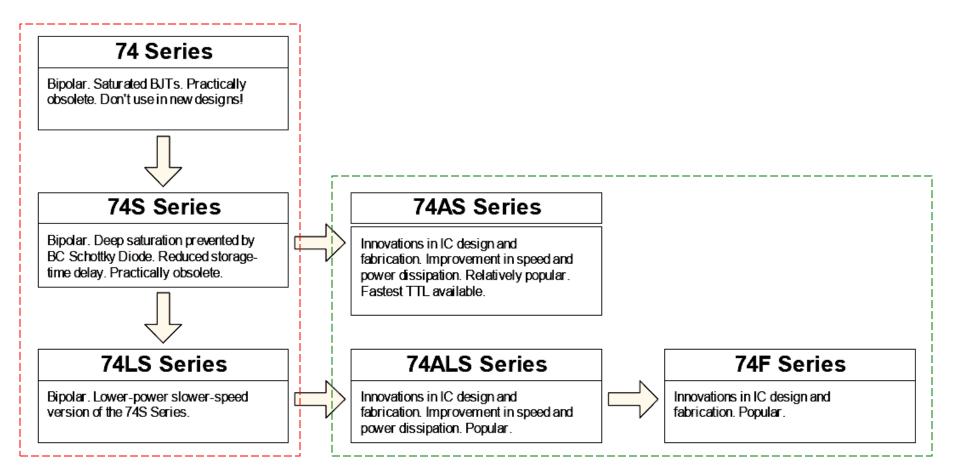

Legacy: don't use in new designs

Widely used today

ECL

Emitter-Coupled Logic (ECL)


- •<u>PROS</u>: Fastest logic family available (~1ns)
- •<u>CONS</u>: low noise margin and high power dissipation
- •Operated in emitter coupled geometry (recall differential amplifier or emitter-follower), transistors are biased and operate near their Q-point (never near saturation!)
- Logic levels. "0": -1.7V. "1": -0.8V
- Such strange logic levels require extra effort when interfacing to TTL/CMOS logic families.
 Open LTspice example: ECL inverter...

CMOS

Complimentary MOS (CMOS)

- Other variants: NMOS, PMOS (obsolete)
- Very low static power consumption
- Scaling capabilities (large integration all MOS)
- Full swing: rail-to-rail output
- Things to watch out for:
 - don't leave inputs floating (in TTL these will float
 - to HI, in CMOS you get undefined behaviour)
 - susceptible to electrostatic damage (finger of death)

Life-cycle

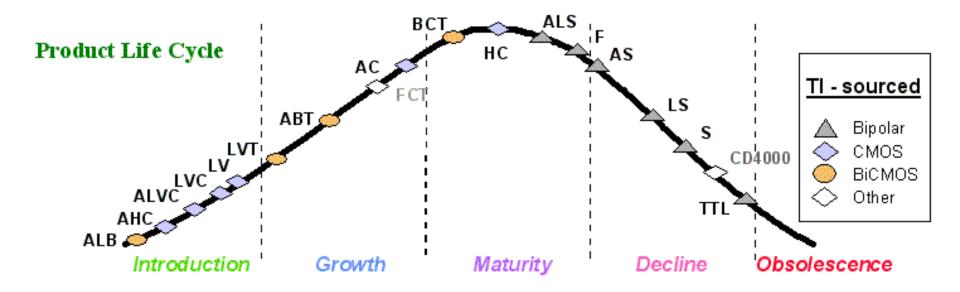

Combinational Circuits

Outline

Boolean Algebra
Decoder
Encoder
MUX

History: Computer and the Rationalist

- Modern research issues in AI are formed and evolve through a combination of historical, social and cultural pressures.
- The rationalist tradition had an early proponent in Plato, and was continued on through the writings of Pascal, Descates, and Liebniz
- For the rationalist, the external world is reconstructed through the clear and distinct ideas of a mathematics

History: Development of Formal Logic

- The goal of creating a formal language for thought also appears in the work of <u>George</u> <u>Boole</u>, another 19th century mathematician whose work must be included in the roots of AI
- The importance of Boole's accomplishment is in the extraordinary power and simplicity of the system he devised: Three Operations


Three Operations

three basic Boolean operations can be defined arithmetically as follows.

□ *x¬y=xy* □ *x*⊎*y=x* + *y* − *xy* □¬*x*=1 − *x*

Figure 1. Truth tables

x	у	x∧y	x∨y
0	0	0	0
1	0	0	1
0	1	0	1
1	1	1	1

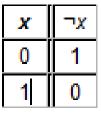

Boolean function and logic diagram

 Boolean algebra: Deals with binary variables and logic operations operating on those variables.

 Logic diagram: Composed of graphic symbols for logic gates. A simple circuit sketch that represents inputs and outputs of Boolean functions.

Basic Identities of Boolean Algebra

 $(1) \qquad x + 0 = x$ $(2) \qquad x \cdot 0 = 0$ (3) x + 1 = 1 $x \cdot 1 = 1$ (4) (5) x + x = x(6) $x \cdot x = x$ (7) x + x' = x(8) $x \cdot x' = 0$ (9) x + y = y + x(10)xy = yx(11) x + (y + z) = (x + y) + z(12)x (yz) = (xy) z(13)x(y+z) = xy + xz(14) x + yz = (x + y)(x + z)(15) (x + y)' = x'y'(16) (xy)' = x' + y'(17) (x')' = x

Gates

Refer to the hardware to implement Boolean operators.

The most basic gates are

Name	Graphic symbol	Algebraic function	Truth table	
Inverter	а — О — х	x = A'	A x 0 1 1 0	_
AND	А- в	x = AB	A B x 0 0 0 0 1 0 1 0 0 1 1 1	True if both are true.
OR	A B X	x = A + B	A B x 0 0 0 0 1 1 1 0 1 1 1 1	True if either one is true.

Boolean function and truth table

•	Other common gates include:						
	Name	Graphic symbol	Algebraic function	Truth table			
_		гушра	Tunction	Capie			
	Exclusive-OR (XOR)	A B B X	x = A ⊕ B = A'B + AB'	<u>A B x</u> 0 0 0 0 1 1 1 0 1 1 1 0	Parity check: True if only one is true.		
	NAND	А- ВО- х	x = (AB)'	<u>A B x</u> 0 0 1 0 1 1 1 0 1 1 1 0	Inversion of AND.		
	NOR		x = A + B	A B x 0 0 1 0 1 0 1 0 0 1 1 0	Inversion of OR.		

Outline

Boolean Algebra
Decoder
Encoder
MUX

Decoder

□ Accepts a value and decodes it

Output corresponds to value of n inputs


□ Consists of:

- Inputs (n)
- Outputs (2^n , numbered from $0 \rightarrow 2^n$ 1)
- Selectors / Enable (active high or active low)

The truth table of 2-to-4 Decoder

<i>S</i> ₁	<i>S</i> ₀	Ε	00	01	02	03
Х	S ₀ X 0 1 0 1	0	0	0	0	0
0	0	1	1	0	0	0
0	1	1	0	1	0	0
1	0	1	0	0	1	0
1	1	1	0	0	0	1


2-to-4 Decoder

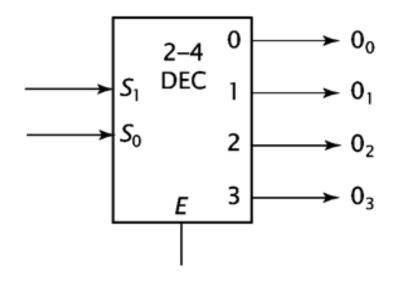

<i>S</i> ₁	<i>S</i> ₀	Ε	00	01	02	03
х	х	0	0	0	0	0
0	<i>S</i> ₀ X 1 0 1	1	1	0	0	0
0	1	1	0	1	0	0
1	0	1	0	0	1	0
1	1	1	0	0	0	1

(b)


2-to-4 Decoder

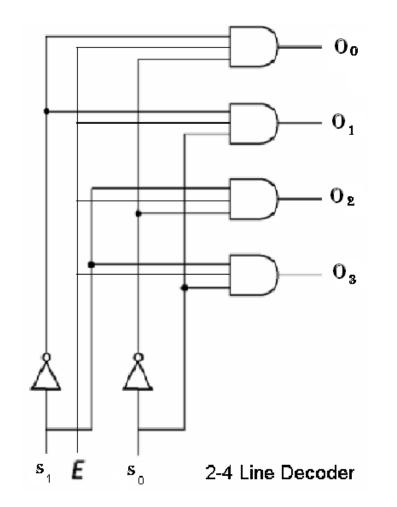


The truth table of 3-to-8 Decoder

A2	A1	A0	D0	D1	D2	D3	D4	D5	D6	D7
0	0	0	1							
0	0	1		1						
0	1	0			1					
0	1	1				1				
1	0	0					1			
1	0	1						1		
1	1	0							1	
1	1	1								1

3-to-8 Decoder

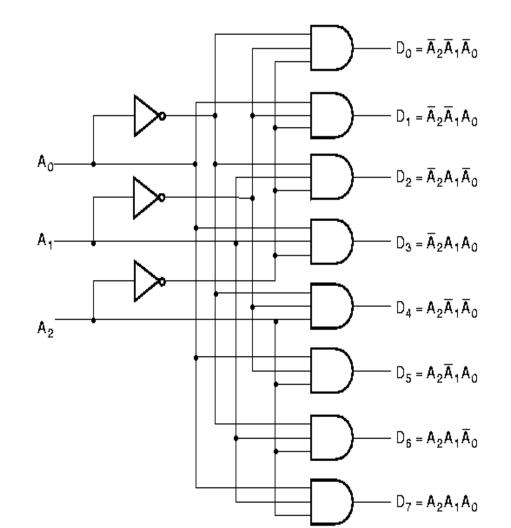

3-to-8 Decoder with Enable

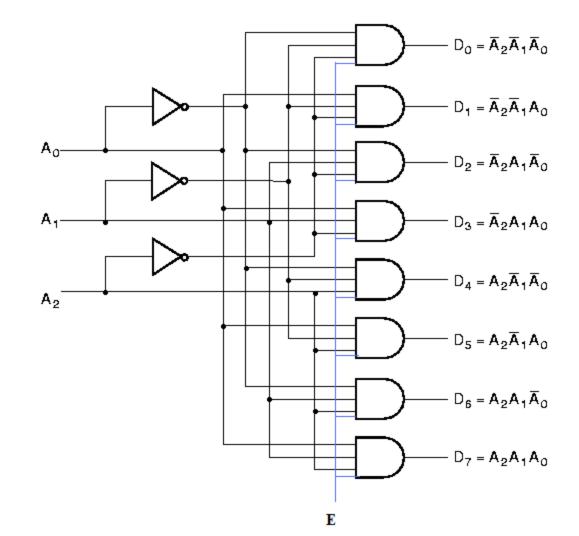

Decoder Expansion


Decoder expansion

Combine two or more small decoders with enable inputs to form a larger decoder


3-to-8-line decoder constructed from two 2-to- 4line decoders

- The MSB is connected to the enable inputs
- if A₂=0, upper is enabled; if A₂=1, lower is enabled.

Decoder Expansion

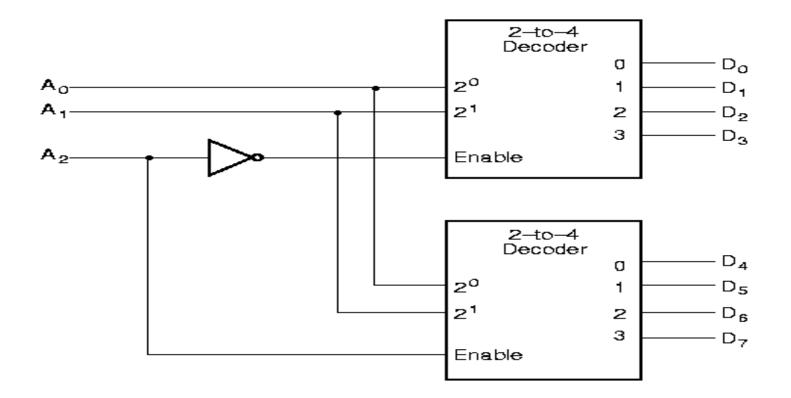

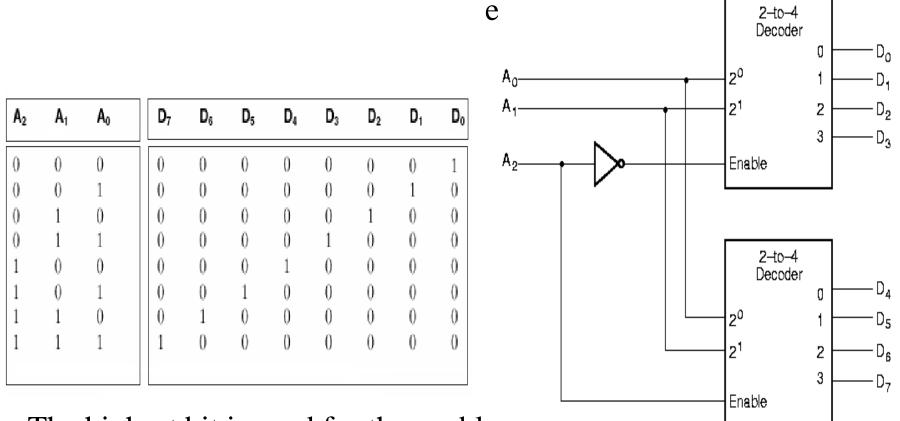Combining two 2-4 decoders to form one 3-8 decoder using enable switch



The highest bit is used for the enabl

How about 4-16 decoder

Use how many 3-8 decoder?Use how many 2-4 decoder?


Outline

- Boolean AlgebraDecoderEncoder
- Mux




Perform the inverse operation of a decoder 2ⁿ (or less) input lines and n output lines

Encoders

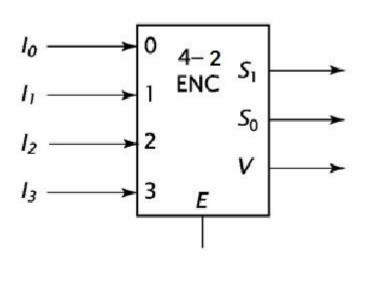

I ₀	<i>I</i> ₁	l ₂	<i>I</i> 3	Ε	<i>S</i> 1	S 0	V
х	х	х	x	0	z	Ζ	Ζ
0	0	0	0	1	0	0	0
1	0	0	0	1	0	0	1
0	1	0	0	1	0	1	1
0	0	1	0	1	1	0	1
0	0	0	1	1	1	1	1

Encoders with OR gates

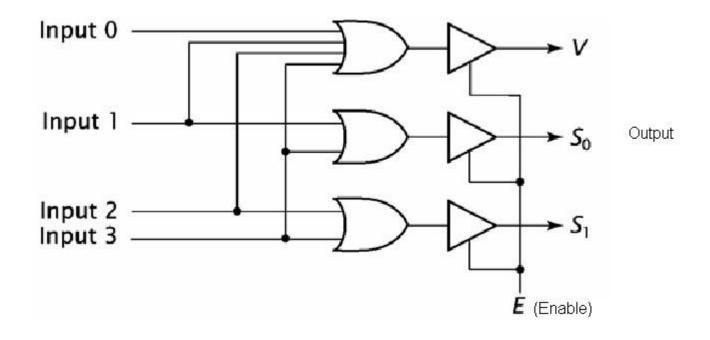

Encoders

Perform the inverse operation of a decoder
 2ⁿ (or less) input lines and n output lines

D ₇	D_6	D_5	D ₄	D ₃	D ₂	D ₁	Do	A ₂	A 1	A ₀
0	0	0	0	٥	0	0	1	0	0	٥
0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	1	0	0	0	1	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	0
0	0	1	0	0	0	0	0	1	0	1
0	1	0	0	0	0	0	0	1	1	0
1	0	0	0	0	0	0	0	1	1	1

Priority Encoder

Accepts multiple values and encodes them


- Works when more than one input is active
- □ Consists of:
 - Inputs (2ⁿ)
 - Outputs

□ when more than one output is active, sets output to correspond to highest input

- V (indicates whether any of the inputs are active)
- Selectors / Enable (active high or active low)

D3	D2	D1	D0	A1	A0	V
0	0	0	0	Х	Х	0
0	0	0	1	0	0	1
0	0	1	0	0	1	1
0	0	1	1	0	1	1
0	1	0	0	1	0	1
0	1	0	1	1	0	1
0	1	1	0	1	0	1
0	1	1	1	1	0	1
1	0	0	0	1	1	1
1	0	0	1	1	1	1
1	0	1	0	1	1	1
1	0	1	1	1	1	1
1	1	0	0	1	1	1
1	1	0	1	1	1	1
1	1	1	0	1	1	1
1	1	1	1	1	1	1

Priority Encoder

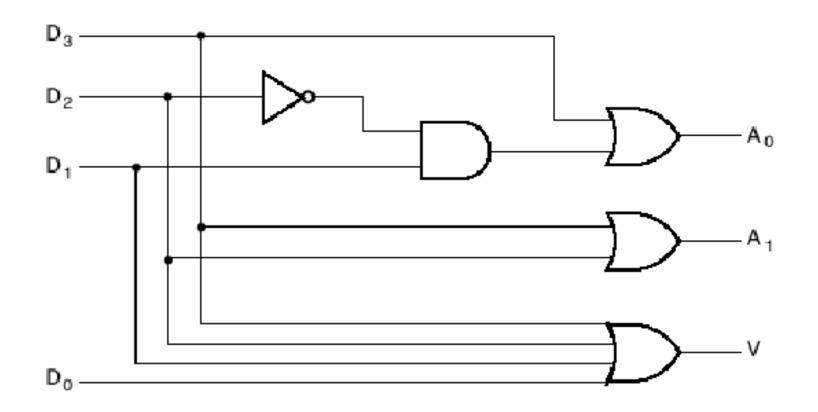

Outline


- Boolean AlgebraDecoderEncoder
- Mux

Multiplexer (MUX)


A multiplexer can use addressing bits to select one of several input bits to be the output.

A selector chooses a single data input and passes it to the MUX output
It has one output selected at a time.

Function table with enable

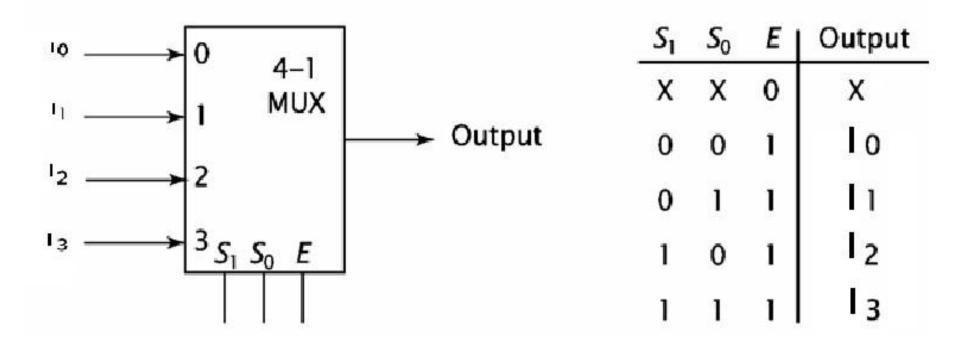

4 to 1 line multiplexer

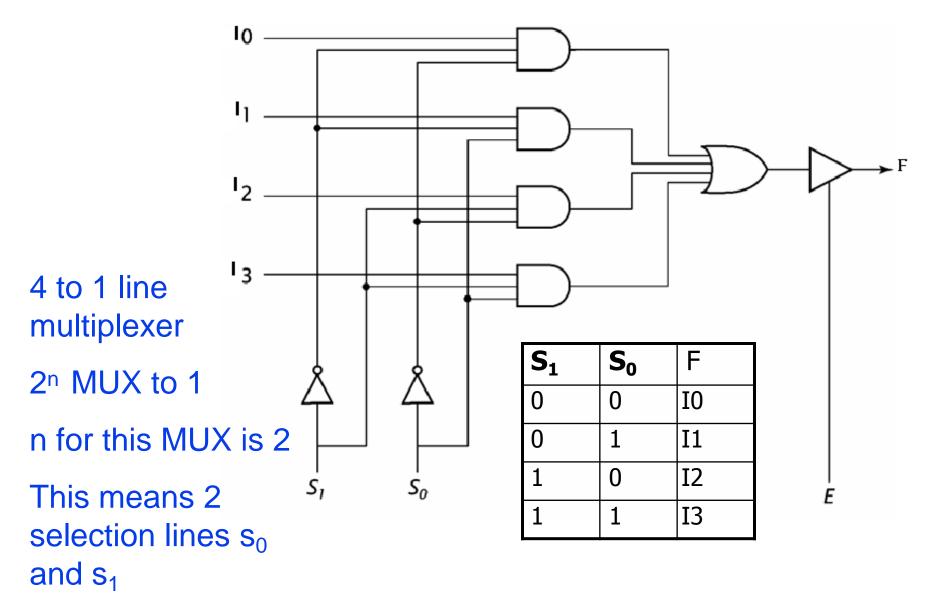

Multiplexer (MUX)

□ Consists of:

- Inputs (multiple) = 2ⁿ
- Output (single)
- Selectors (# depends on # of inputs) = n
- Enable (active high or active low)


Multiplexers versus decoders

•A <u>Multiplexer</u> uses *n* binary select bits to choose from a maximum of 2^n unique input lines.

•Decoders have 2^n number of output lines while multiplexers have only <u>one output line</u>.


•The output of the multiplexer is the data input whose index is specified by the *n* bit code.

Multiplexer Versus Decoder

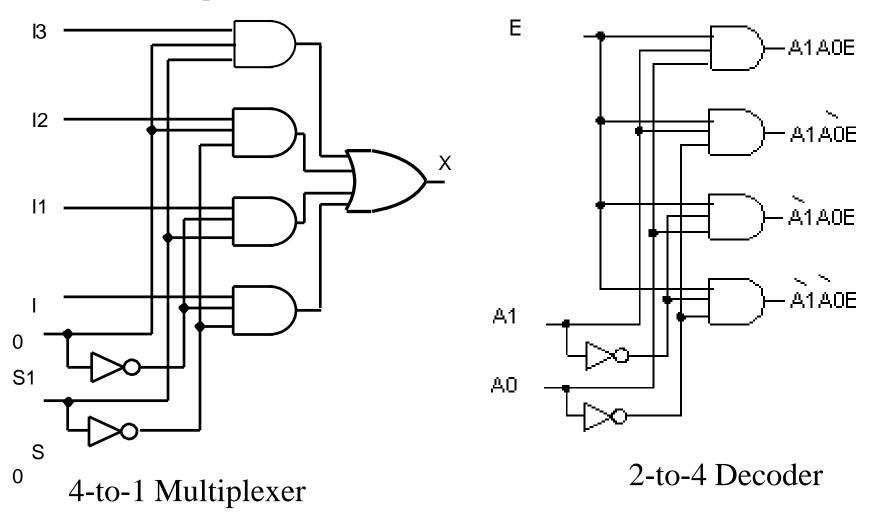


Note that the multiplexer has an extra OR gate. A1 and A0 are the two inputs in decoder. There are four inputs plus two selecs in multiplexer.

Cascading multiplexers

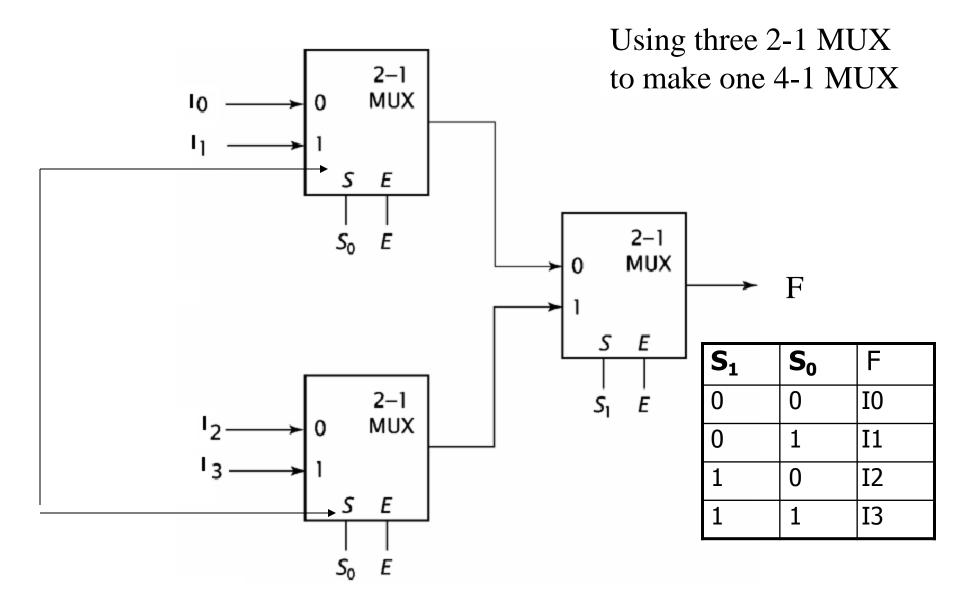


Example: Construct an 8-to-1 multiplexer using 2-to-1 multiplexers.

S ₂	S ₁	S ₀	F
0	0	0	I ₀
0	0	1	I ₁
0	1	0	I ₂
0	1	1	I ₃
1	0	0	I ₄
1	0	1	I ₅
1	1	0	I ₆
1	1	1	I ₇

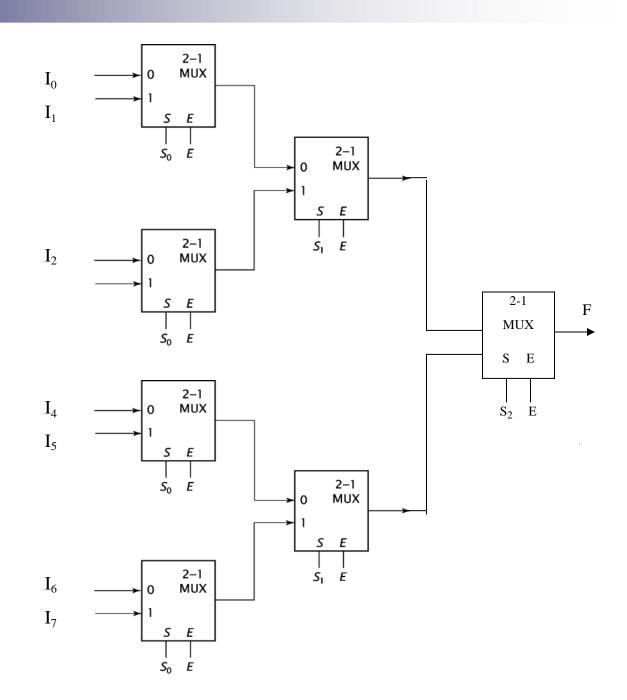


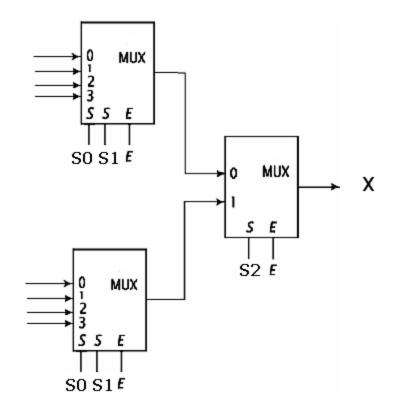Example : Construct 8-to-1 multiplexer using one 2-to-1 multiplexer and two 4-to-1 multiplexers



S ₂	S ₁	S ₀	Х
0	0	0	I ₀
0	0	1	I ₁
0	1	0	I ₂
0	1	1	I ₃
1	0	0	I ₄
1	0	1	I ₅
1	1	0	I ₆
1	1	1	I ₇

Quadruple 2-to-1 Line Multiplexer

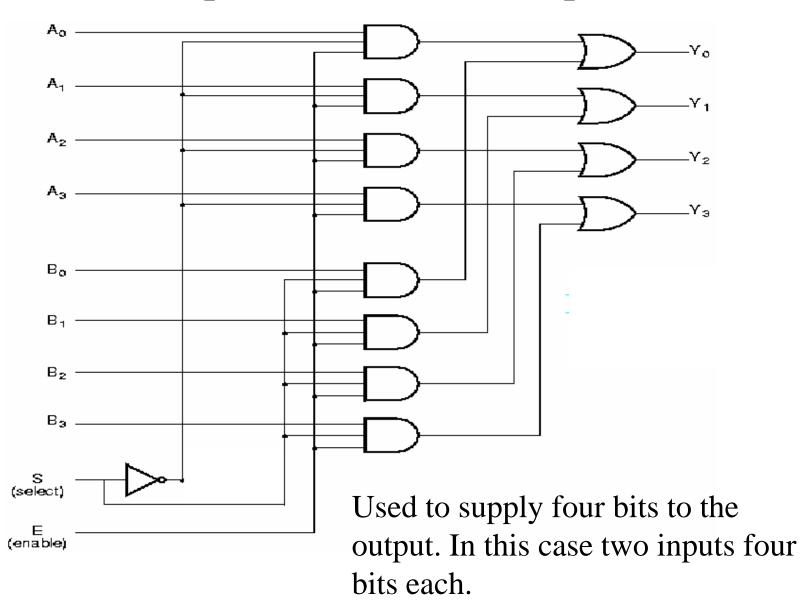

Quadruple 2-to-1 Line Multiplexer

E	S	Υ
(Enable)	(Select)	(Output)
0	X	All 0's
1	0	A
1	1	В




Combinational Logic

Combinational Logic:
 Output depends only on current input
 Has no memory

Sequential Logic

- Sequential Logic:
- Output depends not only on current input but also on past input values, e.g., design a counter
- □Need some type of memory to remember the past input values

Sequential Circuits

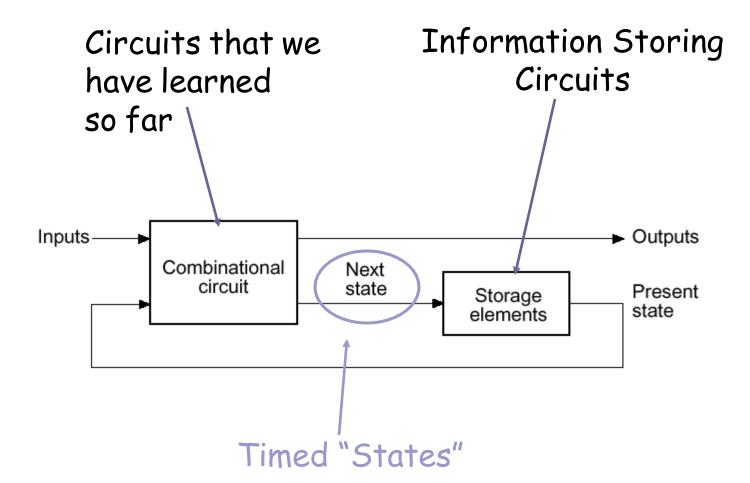

Sequential Logic: Concept

- Sequential Logic circuits remember past inputs and past circuit state.
- Outputs from the system are "fed back" as new inputs
- □With gate delay and wire delay
- The storage elements are circuits that are capable of storing binary information: memory.


Synchronous vs. Asynchronous

There are two types of sequential circuits:


Synchronous sequential circuit: circuit output changes only at some discrete instants of time. This type of circuits achieves synchronization by using a timing signal called the *clock*.

Asynchronous sequential circuit: circuit output can change at **any** time (clockless).


Clock Period

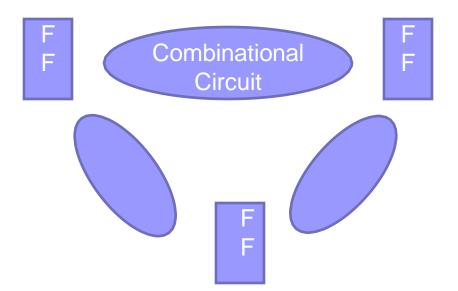

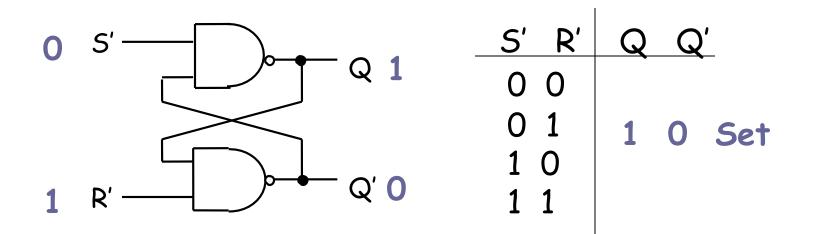
Smallest clock period = largest combinational circuit delay between any two directly connected FF, subjected to impact of FF setup time.



ХУ	NAND
00	1
01	1
10	1
11	0

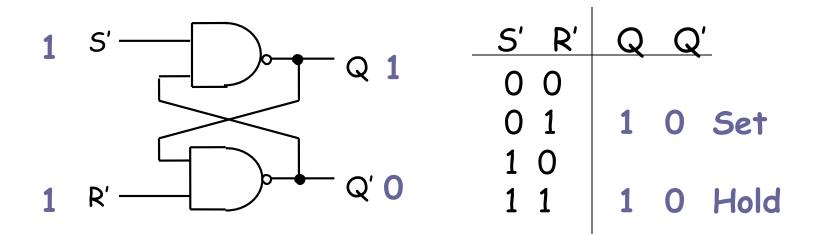


ХУ	NAND
00	1
01	1
10	1
11	0

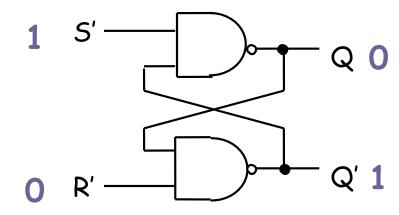

S' R'	Q	Q)'
00	-		
01	1	0	Set
1 0	0	1	Reset
1 1	1	0	Hold


T

ХУ	NAND
00	1
01	1
10	1
11	0

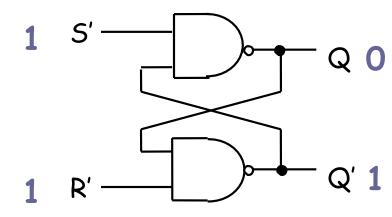

S' R'	Q	Q	<u>/</u>
00	-		
01	1	0	Set
1 0	0	1	Reset
1 1	1	0	Hold
	0	1	Hold

ХУ	NAND
00	1
01	1
10	1
11	0

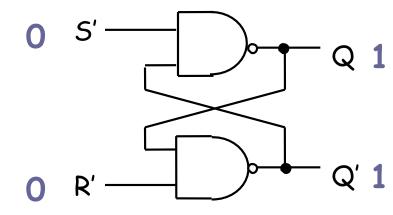


S' R'	<u>Q Q'</u>	
00	1 1 Disallowe	d
01	1 0 Set	
1 0	0 1 Reset	
1 1	1 O Hold	
	0 1 Hold	


ХУ	NAND
00	1
01	1
10	1
11	0

D Latch

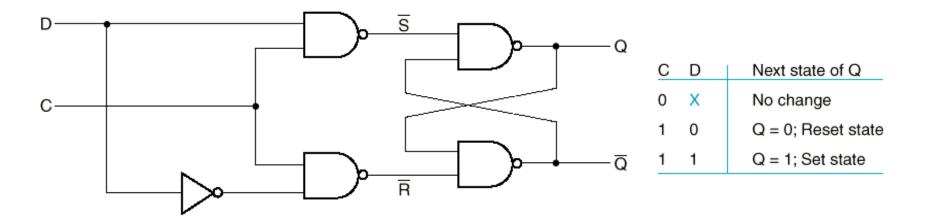One way to eliminate the undesirable indeterminate state in the RS flip flop is to ensure that inputs S and R are never 1 simultaneously. This is done in the D latch:



D Latch with Transmission Gates

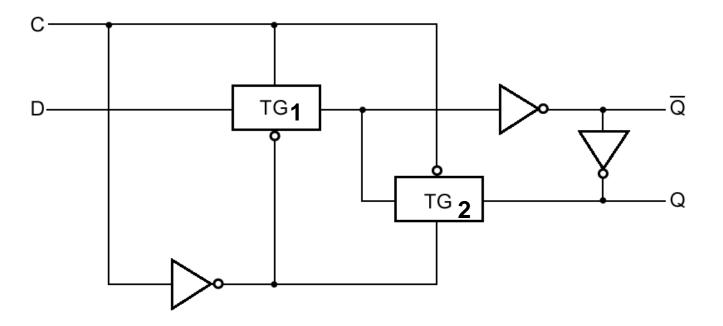


■ C=1 → TG1 closes and TG2 opens → Q'=D' and Q=D ■ C=0 → TG1 opens and TG22 closes → Hold Q and Q'

Flip-Flops

- Latches are "transparent" (= any change on the inputs is seen at the outputs immediately when C=1).
- This causes synchronization problems.
- Solution: use latches to create flip-flops that can respond (update) only on specific times (instead of any time).
- Types: RS flip-flop and D flip-flop


D Flip-Flop

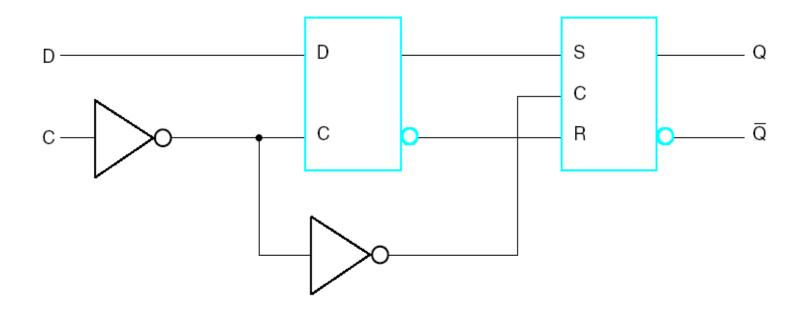

Characteristic Tables

- Defines the <u>logical</u> properties of a flip-flop (such as a truth table does for a logic gate).
- Q(t) present state at time t
- Q(t+1) next state at time t+1

D Flip-Flop Timing Parameters

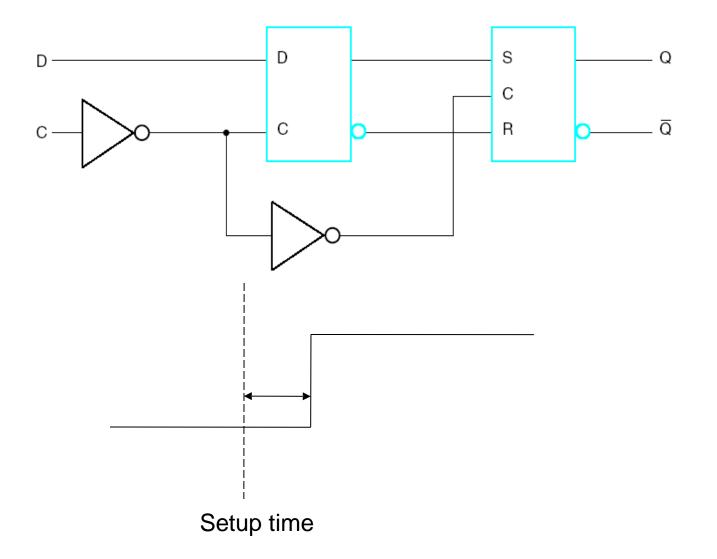


Sequential Circuit Analysis

- Analysis: Consists of obtaining a <u>suitable</u> description that demonstrates the <u>time sequence</u> of inputs, outputs, and states.
- Logic diagram: Boolean gates, flip-flops (of any kind), and appropriate interconnections.
- The logic diagram is derived from any of the following:
 - □ Boolean Equations (FF-Inputs, Outputs)
 - □ State Table
 - State Diagram

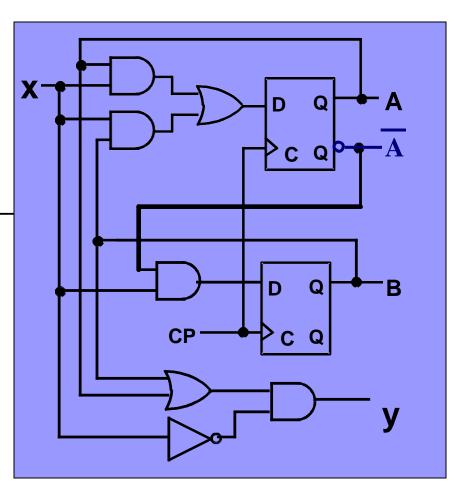Example


- <u>Input</u>: x(t)
- Output: y(t)
- State: (A(t), B(t))
- What is the Output
- What is the <u>Next State</u> <u>Function</u>?



Example (continued)

 Boolean equations for the functions:
 A(t+1) = A(t)x(t)
 B(t+1) = A'(t)x(t)

 $\Box y(t) = x'(t)(B(t) + A(t))$

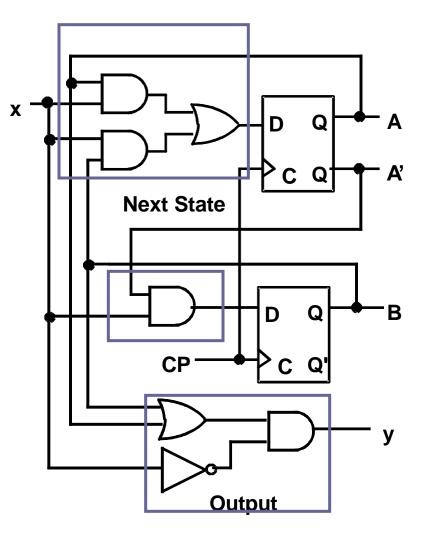

State Table Characteristics

State table – a multiple variable table with the following four sections:


- Present State the values of the state variables for each allowed state.
- □ *Input* the input combinations allowed.
- Next-state the value of the state at time (t+1) based on the present state and the input.
- Output the value of the output as a function of the present state and (sometimes) the input.
- From the viewpoint of a truth table:
 - □ the inputs are Input, Present State
 - □ and the outputs are Output, Next State

State Diagrams


- The sequential circuit function can be represented in graphical form as a <u>state diagram</u> with the following components:
 - □ A <u>circle</u> with the state name in it for each state
 - A <u>directed arc</u> from the <u>Present State</u> to the <u>Next State</u> for each <u>state transition</u>
 - A label on each <u>directed arc</u> with the <u>Input</u> values which causes the <u>state transition</u>, and
 - □ A label:
 - On each <u>circle</u> with the <u>output</u> value produced, or
 - On each <u>directed arc</u> with the <u>output</u> value produced.

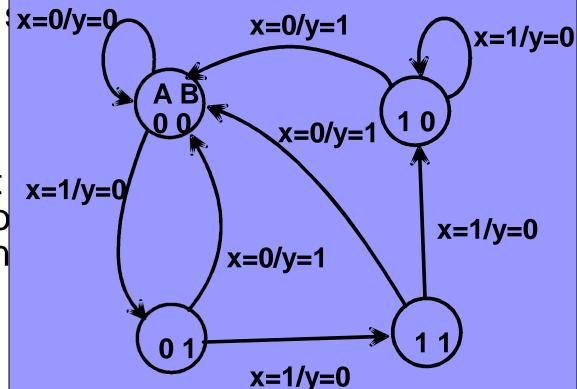Example: State Diagram

- Diagram gets confusing for large circuits
- For small circuit, usually easier to understand than the state table



MEMORY

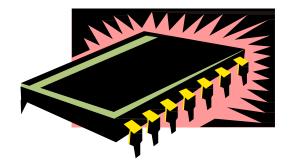


Memory

- Sequential circuits all depend upon the presence of memory.
 - □ A flip-flop can store one bit of information.
 - □ A register can store a single "word," typically 32 or 64 bits.
- Memory allows us to store even larger amounts of data.
 - □ Read Only Memory (ROM)
 - Random Access Memory (RAM)
 - Static RAM (SRAM)
 - Dynamic RAM (DRAM)

Picture of Memory

You can think of memory as being one big array of data.

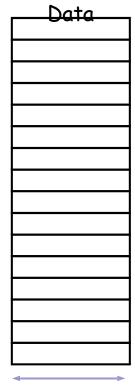- $\hfill\square$ The address serves as an array index.
- □ Each address refers to one word of data.
- You can read or modify the data at any given memory address, just like you can read or modify the contents of an array at any given index.



Word



Memory Signal Types

- Memory signals fall into three groups
 - Address bus selects one of memory locations
 - Data bus
 - Read: the selected location's stored data is put on the data bus
 - Write (RAM): The data on the data bus is stored into the selected location
 - Control signals specifies what the memory is to do
 - Control signals are usually active low
 - Most common signals are:
 - □ CS: Chip Select; must be active to do anything
 - □ OE: Output Enable; active to read data
 - □ WR: Write; active to write data

Memory Address, Location and size

- □ All bits in location are read/written together
- □ Cannot manipulate single bits in a location
- For k address signals, there are 2^k locations in memory device
- Each location contains an n bit word
- Memory size is specified as
 - □ #loc x bits per location
 - 2²⁴ x 16 RAM 2²⁴ = 16M words, each 16 bits long
 - 24 address lines, 16 data lines

□ #bits

• The total storage capacity is 2²⁴ x 16 = 2²⁸ bits

Size matters!


- Memory sizes are usually specified in numbers of bytes (1 byte= 8 bits).
- The 2²⁸-bit memory on the previous page translates into:

 2^{28} bits / 8 bits per byte = 2^{25} bytes

With the abbreviations below, this is equivalent to 32 megabytes.

	Prefix	Base 2	Base 10
К	Kilo	2 ¹⁰ = 1,024	10 ³ = 1,000
Μ	Mega	2 ²⁰ = 1,048,576	10 ⁶ = 1,000,000
G	Giga	2 ³⁰ = 1,073,741,824	10 ⁹ = 1,000,000,000

Read-only memory (ROM)

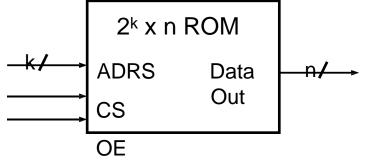

- Non-volatile
 - If un-powered, its content retains
- Read-only
 - normal operation cannot change contents
- k-bit ADRS specifies the address or location to read from
- A Chip Select, CS, enables or disables the RAM
- An Output Enable, OE, turns on or off tri-state output buffers
- Data Out will be the n-bit value stored at ADRS

ROM PROGRAMMING


□ Programmed ROM (PROM): contents loaded at the factory

- hardwired can't be changed
- embedded mass-produced systems
- □ OTP (One Time Programmable): Programmed by user
- □ UVPROM: reusable, erased by UV light
- EEPROM: Electrically erasable; clears entire blocks with single operation


ROM Usage

- ROMs are useful for holding data that never changes.
 - Arithmetic circuits might use tables to speed up computations of logarithms or divisions.
 - □ Many computers use a ROM to store important programs that should not be modified, such as the system BIOS.
 - □ Application programs of embedded systems, PDAs, game machines, cell phones, vending machines, etc., are stored in ROMs


ROM Structure

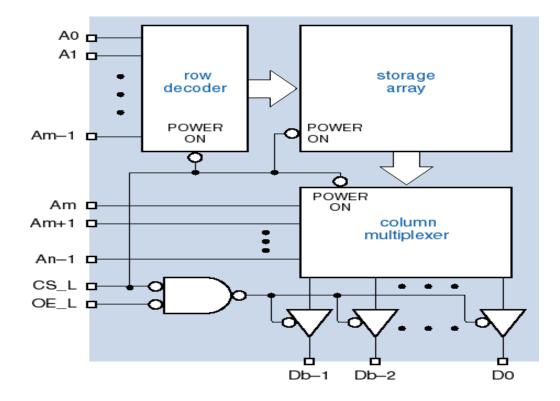




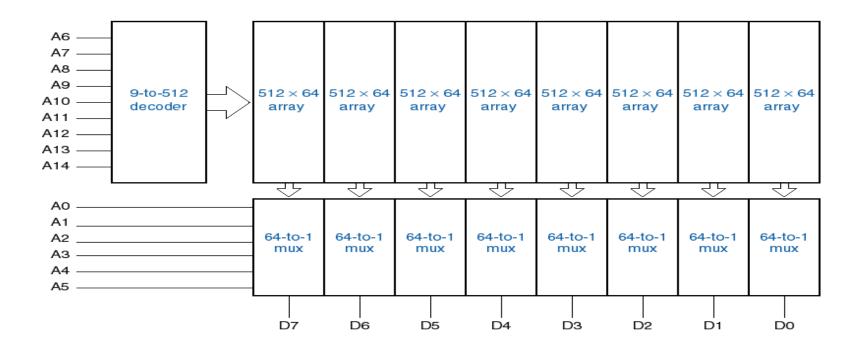


Typical commercial EEPROMs

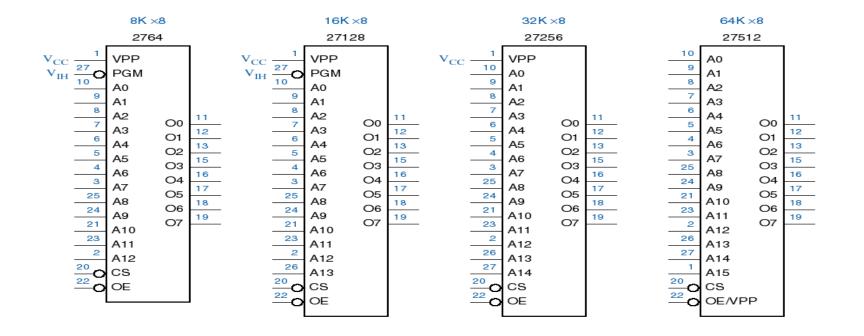

Microprocessor EPROM application

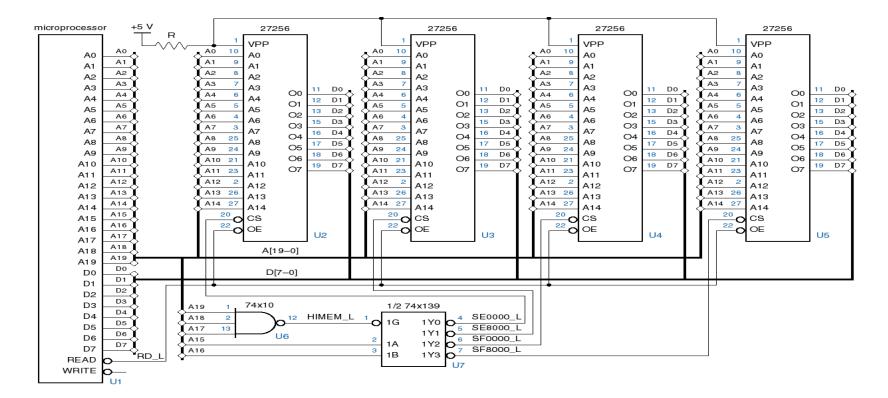

ROM Timing

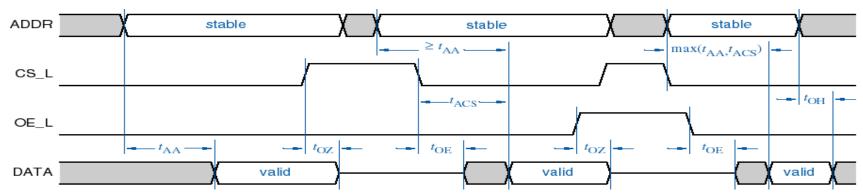


Memories and functions

- ROMs are actually combinational devices, not sequential ones!
 - You can store arbitrary data into a ROM, so the same address will always contain the same data.
 - You can think of a ROM as a combinational circuit that takes an address as input, and produces some data as the output.
- A ROM table is basically just a truth table.
 - The table shows what data is stored at each ROM address.


 \Box You can generate that data combinationally, using the address as the input.

Address	Data
$A_2A_1A_0$	$V_2V_1V_0$
000	000
001	100
010	110
011	100
100	101
101	000
110	011
111	011

Logic-in-ROM Example

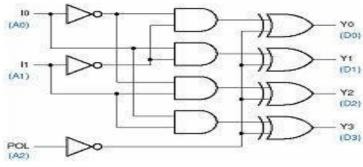


Inputs			Outputs			
A2	AI	AO	D3	D2	D1	Do
0	0	0	1	1	1	0
0	0	1	1	1	0	1
0	1	0	1	0	1	1
0	1	1	0	1	1	1
1	0	0	0	0	0	1
1	0	1	o	0	1	0
1	1	σ	0	1	0	0
1	1	1	1	0	0	0

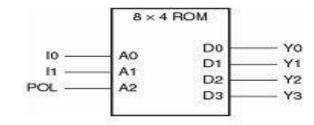


Reading RAM

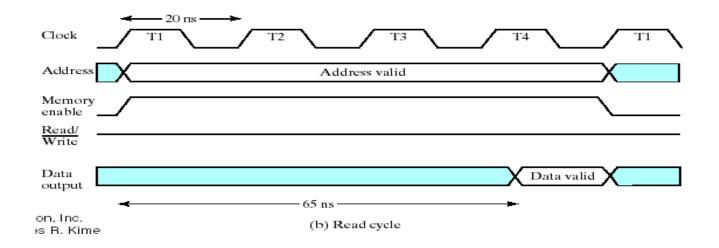- 50 MHz CPU 20 ns clock cycle time
- Memory access time= 65 ns
 - Maximum time from the application of the address to the appearance of the data at the Data Output




WRITING RAM

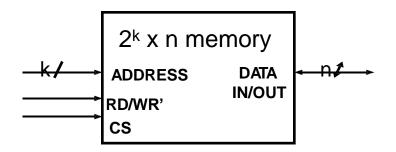

- \Box Enable the chip by setting CS = 1.
- \Box Select the write operation, by setting RD/WR' = 0.
- □ Send the desired address to the ADRS input.
- □ Send the word to store to the DATA IN/OUT.

WRITING RAM

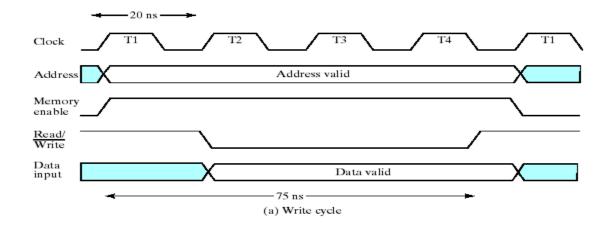- 50 MHz CPU 20 ns clock cycle time
- Write cycle time= 75 ns
 - Maximum time from the application of the address to the completion of all internal memory operations to store a word



Static memory

- How can you implement the memory chip?
- There are many different kinds of RAM.
 - We'll start off discussing static memory, which is most commonly used in caches and video cards.


□ Later we mention a little about dynamic memory, which forms the bulk of a computer's main memory.

- Static memory is modeled using one *latch* for each bit of storage.
- Why use latches instead of flip flops?


□ A latch can be made with only two NAND or two NOR gates, but a flipflop requires at least twice that much hardware.

- □ In general, smaller is faster, cheaper and requires less power.
- \Box The tradeoff is that getting the timing exactly right is a pain.


RAM Cell with SR Latch

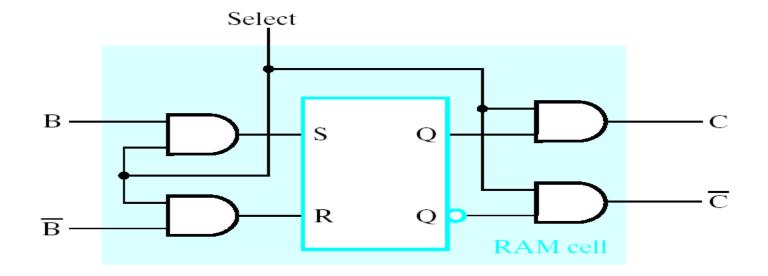


RAM Bit Slice Model

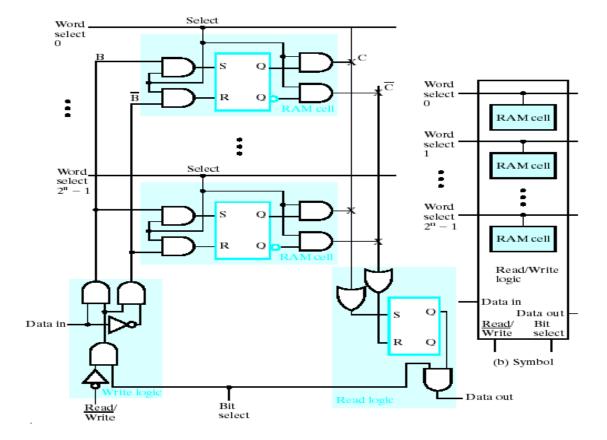

8x2 RAM Using a 4x4 RAM Cell Array

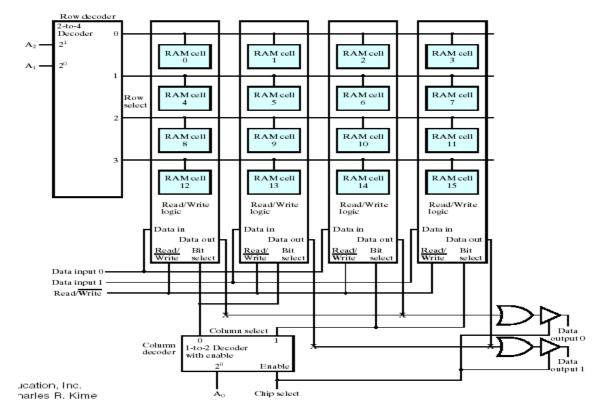


SRAM Devices

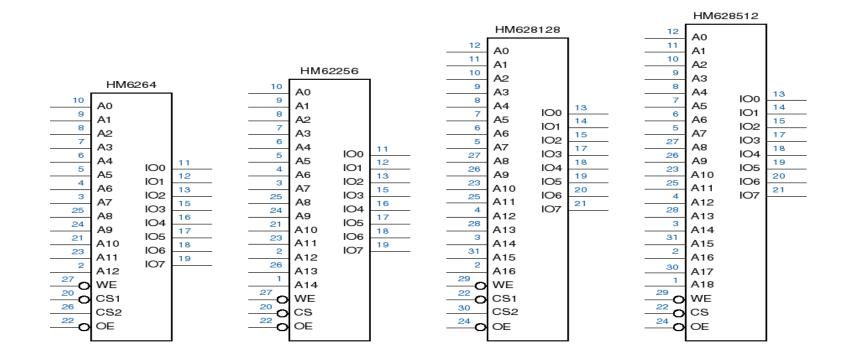

Dynamic memory

- Dynamic memory is built with capacitors.
 - □ A stored charge on the capacitor represents a logical 1.
 - □ No charge represents a logic 0.
- However, capacitors lose their charge after a few milliseconds. The memory requires constant refreshing to recharge the capacitors. (That's what's "dynamic" about it.)
- Dynamic RAMs tend to be physically smaller than static RAMs.
 - □ A single bit of data can be stored with just one capacitor and one transistor, while static RAM cells typically require 4-6 transistors.

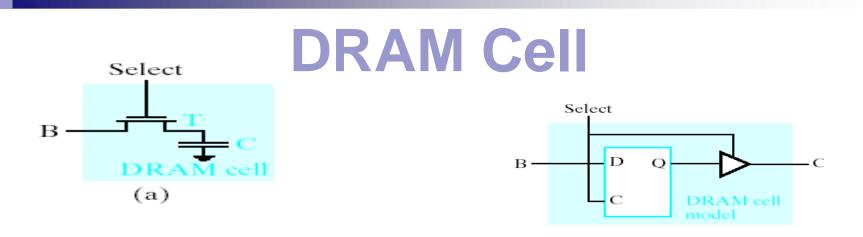
□ This means dynamic RAM is cheaper and denser—more bits can be stored in the same physical area.




(h)

- DRAM cell: One transistor and one capacitor
 - 1/0 = capacitor charged/discharged
- SRAM cell: Six transistors Costs 3 times more (cell complexity)
- Cost per bit is less for DRAM reason for why large memories are DRAMs

DRAM Bit Slice

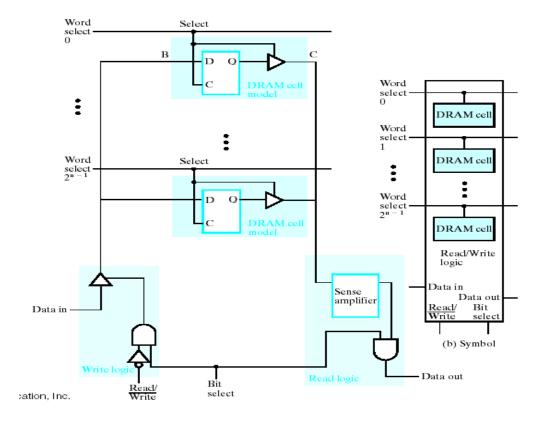

DRAM Including Refresh Logic

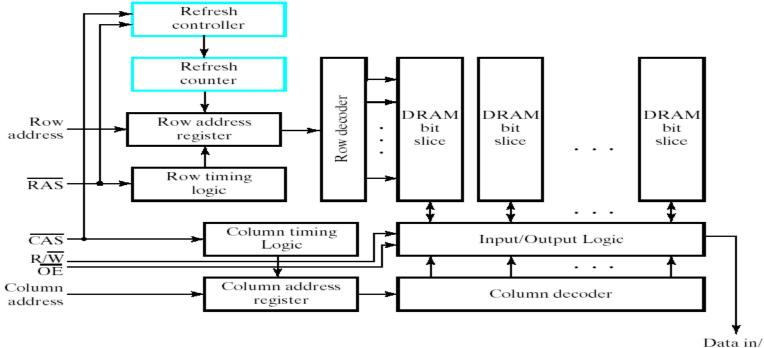

© 2004 Pearson Education, Inc.

Data in/ Data out