Hall Ticket No			Question Paper Code: AEE013		
INSTITUTE OF AERONAUTICAL ENGINEERING (Autonomous)					
B.Tech VI Semester End Examinations (Regular), November – 2020					
		Regulation: IARE–R16			
SOLID STATE ELECTRIC MOTOR DRIVES					
Гime: 2 Hours		(EEE)	Max Marks: 70		
	Answer a Answer a	ny Four Questions from ny Five Questions from	n Part A n Part B		
		$\mathbf{PART} - \mathbf{A}$			
1. Summarize the adva	drives [5M]				
2 Emploin the energies	on of normanative has	aling control of Do conies	noton by choppen control [FN/]		

4.	Explain the operation of regenerative braxing control of De series motor by chopper control.	
3.	Compare the VSI and CSI fed induction motor drives.	[5M]
4.	List the advantages and applications of slip power recovery schemes	[5M]
5.	Explain the operation of self controlled mode of synchronous motor drive.	[5M]
6.	Draw the speed torque characteristics of DC series motor fed with single phase full converter.	[5M]
7.	Explain the four quadrant operations with converters.	[5M]

8. Sketch the mechanical characteristics of a three phase induction motor with V/f method. [5M]

$\mathbf{PART} - \mathbf{B}$

- 9. A 200 V, 875 RPM, 150 A separately excited dc motor has an armature resistance of 0.06 Ω. It is fed from a single phase fully-controlled rectifier with an ac source voltage of 220V, 50Hz. Assuming continuous conduction, calculate firing angle for rated motor torque and 750 rpm. [10M]
- 10. Explain how the speed of a DC series motor is controlled using a single phase fully controlled converter by sketching the output voltage and current waveforms. [10M]
- 11. Explain how a DC motor can be operated in four quadrants with the help of a single phase dual converter.

[10M]

- 12. A 230V separately excited dc motor takes 50A at a speed of 800 rpm. The armature resistance of 0.4 ohm. This motor is controlled by a chopper with an input voltage 230V and frequency of 500Hz. Assuming continuous conduction throughout; calculate the speed of motoring operation at duty ratios of 0.3 and 0.6, regenerative braking operation duty ratios of 0.7 and 0.4. [10M]
- 13. Explain how induction motor control through V/F control (or) frequency control? [10M]
- 14. A 440 V, 3-phase, 50 Hz, 6-pole, 945 rpm, delta connected induction motor has the following parameters referred to the stator: $Rs=2 \Omega$, $Rr=2\Omega$, $Xs=3 \Omega$ and $Xr=4 \Omega$ When driving a fan load at rated voltage it runs at rated speed. The motor speed is controlled by stator voltage control. Determine motor terminal voltage, current and torque at 800 RPM. [10M]
- 15. Describe the speed control of slip ring induction motor using static Kramer system. [10M]
- 16. Discuss with the help of a block diagram the feed forward vector control of induction motor drives. [10M]
- 17. Explain the variable frequency control of multiple synchronous motor with a neat block diagram. [10M]
- 18. Sketch the block diagram of closed loop control operation of synchronous motor drives and explain its working.

[10M]