

**INSTITUTE OF AERONAUTICAL ENGINEERING**

(Autonomous)

Dundigal-500043, Hyderabad

**B.Tech VII SEMESTER END EXAMINATIONS (REGULAR) - FEBRUARY 2022**

Regulation: R18

**HVDC TRANSMISSION**

Time: 3 Hours

(EEE)

Max Marks: 70

Answer FIVE Questions choosing ONE question from each module  
(NOTE: Provision is given to answer TWO questions from any ONE module)

All Questions Carry Equal Marks

All parts of the question must be answered in one place only

**MODULE – I**

1. (a) With neat sketches explain the different kinds of DC links available. List out its merits and demerits. [7M]
- (b) Explain the comparison of AC and DC transmission in detail with reference to
  - i) Economics
  - ii) Technical performance
  - iii) Reliability. [7M]
2. (a) Compare the performance of EHVAC link with HVDC link for
  - i) Equal voltage (insulation level) ii) Equal power loss [7M]
- (b) Explain clearly what do you understand by surge impedance loading? How a voltage profile of AC line is governed by load and length of the line? [7M]

**MODULE – II**

3. (a) Explain circuit configuration for typical 6-pulse and 12 pulse converters? Discuss the advantages and limitations for 12 pulse converter configurations. [7M]
- (b) What is meant by pulse number of a converter? Explain the individual characteristics of a rectifier and an inverter with sketch. [7M]
4. (a) Derive the expression for input power, output power and power factor of 6-pulse bridge converter with delay angle  $\alpha$ . Assume there is no overlap. [7M]
- (b) With neat diagrams explain about single phase and 3 phase pulse width modulation techniques in HVDC systems. [7M]

**MODULE – III**

5. (a) Explain the role of shunt capacitor and synchronous condensers in reactive power control of HVDC systems. [7M]
- (b) What are the basic characteristics of converter control? Draw and explain combined characteristics of rectifier and an inverter. [7M]
6. (a) Explain the working of band pass and high pass filters used in HVDC systems. Describe the term detuning and state its importance in the design of filters for HVDC systems. [7M]
- (b) With neat diagram explain basic concepts of DC circuit interruption. Discuss the characteristics of DC circuit breakers. [7M]

## MODULE – IV

7. (a) Write a short note on synchronous and asynchronous links in power modulation of HVDC systems. [7M]
- (b) With the help of neat diagram and characteristic waveforms explain voltage stability analysis in AC/DC systems. [7M].
8. (a) What is transient stability and steady state stability? Write briefly about voltage stability and frequency stability. [7M]
- (b) Explain about power modulation for low frequency oscillations and also explain about reactive power modulation. [7M]

## MODULE – V

9. (a) What is MTDC system and what are the major additions that could be made to it? Explain the working of modular multi level DC system. [7M]
- (b) Write about modular multi level converters in HVDC system. What are the advantages of multi-terminal DC links? [7M]
10. (a) Explain with a neat sketch the parallel operation of MTDC system. Draw the VI characteristics under steady state operation. [7M]
- (b) What are the types of parallel MTDC system. Give the comparison between series and parallel MTDC systems. [7M]

– ○ ○ ○ ○ ○ –