

--	--	--	--	--	--	--	--	--	--



# INSTITUTE OF AERONAUTICAL ENGINEERING

(Autonomous)

B.Tech IV Semester End Examinations (Regular), November – 2020

Regulation: IARE–R18

## Analog and Pulse Circuits

(ECE)

Time: 2 Hours

Max Marks: 70

Answer any Four Questions from Part A

Answer any Five Questions from Part B

### PART – A

1. Elaborate the working principle of RC coupled transistor amplifiers. [5M]
2. Obtain the expression for current series feedback amplifier. [5M]
3. Elucidate the operation of class B complementary-symmetry push pull power amplifier. [5M]
4. Elaborate the working principle of sampling gate. [5M]
5. Summarize the working principle of operation of symmetrical triggering of bistable circuit. [5M]
6. What will be the lower and upper cut-off frequencies of the multistage amplifier? [5M]
7. Describe the transformer coupled class A power amplifier. [5M]
8. Write about the working principle of bi-directional sampling gates. [5M]

### PART – B

9. A multistage amplifier is to be constructed using four identical stages, each of which has a lower cut-off frequency, 15 kHz and upper cut-off frequency, 30 kHz. [10M]
10. Summarize the darlington pair amplifier. Interpret hybrid  $\pi$  common emitter transistor model. [10M]
11. Derive the input resistance of i) Voltage series feedback ii) Current series feedback iii) Current shunt feedback iv) Voltage shunt feedback [10M]
12. An amplifier with open loop voltage gain of 1000 delivers 10W of power output at 10% second harmonic distortion when i/p is 10 mV. If 40dB negative feedback is applied and output power is to remain at 10W, determine required input signal ( $V_s$ ) and second harmonic distortion with feedback. [10M]
13. Draw the circuit of RC phase shift oscillator and explain its working. Also obtain the expression for frequency of oscillator and condition for damped oscillation. [10M]
14. Analyze the principle of operation and derive the expression for frequency of oscillation of wein bridge oscillator. [10M]
15. Draw the response of high pass RC circuit to the following input wave forms i) Step ii) Pulse iii) Square iv) Ramp [10M]
16. Obtain the response of low pass RC circuit and explain how low pass RC circuit acts as an integrator. [10M]
17. Analyze the working principle of monostable multivibrator and derive with the pulse width of collector. [10M]
18. Design an astable multivibrator to produce an unsymmetrical square wave of data  $T_A = 0.5$  msec and  $T_B = 0.4$  msec. The square wave amplitude is 15 V. Assume  $(h_{fc})_{min} = 20$ ,  $(I_C) = 5$  mA and  $(V_{CE})_{sat} = 0$ . [10M]