

--	--	--	--	--	--	--	--	--	--



INSTITUTE OF AERONAUTICAL ENGINEERING

(Autonomous)

Dundigal-500043, Hyderabad

B.Tech III SEMESTER END EXAMINATIONS (REGULAR) - FEBRUARY 2022

Regulation:UG-20

ANALOG AND DIGITAL ELECTRONICS

Time: 3 Hours

(CSE|IT|AIML|CS|CSIT)

Max Marks: 70

Answer ALL questions in Module I and II

Answer ONE out of two questions in Modules III, IV and V

NOTE: Provision is given to answer TWO questions from among one of the Modules III / IV / V

All Questions Carry Equal Marks

All parts of the question must be answered in one place only

MODULE – I

- (a) Explain the operation of half-wave rectifier with neat sketches and calculate its ripple factor. [7M]
- (b) Calculate the value of inductance to use in the inductor filter connected to a full-wave rectifier operating at 60 Hz to provide a DC output with 4% ripple for a 100 Ω load. [7M]

MODULE – II

- (a) Draw the hybrid model of CB, CE and CC configurations and write the voltage and current equations. [7M]
- (b) A CE amplifier has the h-parameters given by $h_{ie} = 1000\Omega$, $h_{re} = 2 \times 10^{-4}$, $h_{fe} = 50$, and $h_{oe} = 25 \mu\text{mho}$. If both the load and source resistances are 1 k Ω . Determine:
 - Current gain
 - Voltage gain. [7M]

MODULE – III

- (a) Explain the gray to binary and binary to gray conversion with examples. [7M]
- (b) Design a 4-bit even parity checker. Explain error checking mechanism using parity bit. [7M]
- (a) Explain the following with an example
 - Minterm
 - Maxterm
 - Canonical SOP
 - Canonical POS [7M]
- (b) Design the following logic function using NAND gates only:

$$F_1(A, B, C) = m(1, 2, 4, 7)$$

$$F_2(A, B, C) = m(1, 2, 3, 7).$$
 [7M]

MODULE – IV

- (a) Explain the working of 2 to 4 decoder and also implement a 2 to 4 decoder using 1 to 2 decoder. [7M]

- (b) Design 4-bit magnitude comparator and explain its operation in detail. [7M].
6. (a) Write short notes on the following:
- i) Weighted and Non-Weighted codes
 - ii) Excess – 3 codes [7M]
- (b) Design a 4-bit binary to BCD code converter and explain its operation. [7M]

MODULE – V

7. (a) What do you mean by triggering? Explain the various triggering modes with examples. [7M]
- (b) Construct a JK flip flop using a D flip flop, a 2x1 multiplexer and an inverter. [7M]
8. (a) What is race around condition and how to avoid it along with circuit diagram. [7M]
- (b) Draw the circuit diagram of Johnson counter using D-flip-flops and explain its operation with the help of bit pattern. [7M]

– o o ○ o o –