



# INSTITUTE OF AERONAUTICAL ENGINEERING

(Autonomous)  
(Dundigal-500043, Hyderabad)

**B.Tech III SEMESTER END EXAMINATIONS (REGULAR) - FEBRUARY 2022**

Regulation:UG-20

## NETWORK ANALYSIS

Time: 3 Hours

(EEE)

Max Marks: 70

Answer ALL questions in Module I and II

Answer ONE out of two questions in Modules III, IV and V

NOTE: Provision is given to answer TWO questions from among one of the Modules III / IV / V

All Questions Carry Equal Marks

All parts of the question must be answered in one place only

### MODULE – I

- In a series RL circuit, the inductance being 20mH, the impedance is  $17.85\Omega$ . The angle of lag of the input current from the applied voltage being  $63.5^\circ$  find the values of angular frequency and resistance of the circuit. [7M]
  - For the circuit shown in Figure 1, determine resonant frequency and the impedance at resonant frequency. [7M]

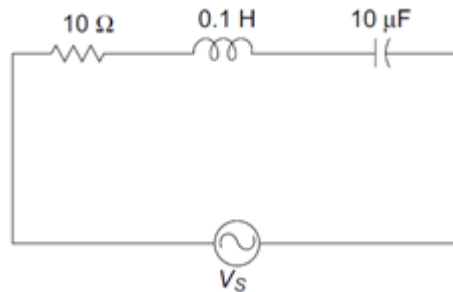


Figure 1

### MODULE – II

- Derive an expression for the current response in R-L series circuit with DC source. [7M]
  - In the circuit shown in Figure 2, obtain the equations for  $I_1(t)$  and  $I_2(t)$  when the switch is closed at  $t = 0$ . [7M]

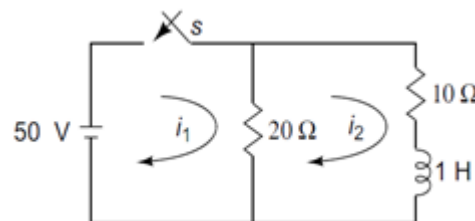


Figure 2

### MODULE – III

3. (a) What is locus diagram and show that the locus diagram of series RL circuit with variable R and fixed value of L is a semi-circle? [7M]
- (b) For a series RL circuit with variable R, plot the locus of the current, mark the range of I for maximum and minimum values of R, and maximum power consumed in the circuit. Assume  $X_L = 25\Omega$  and  $R = 50\Omega$ . The voltage is 200V, 50 Hz. [7M]
4. (a) State and explain the significance of poles and zeros in network function. [7M]
- (b) A network function is given by  $P(s) = \frac{2s}{(s+2)(s^2+2s+2)}$ . Obtain the pole-zero plot and determine the stability of the network. [7M]

### MODULE – IV

5. (a) Obtain the relation between line and phase current in a three-phase balanced star connected system. [7M]
- (b) The three RMS phase voltages of a balanced three phase supply are  $V_{RN} = 100\angle 0^\circ$ ,  $V_{YN} = 100\angle -120^\circ$  and  $V_{BN} = 100\angle -240^\circ$ . What are the magnitudes of line voltages? [7M].
6. (a) With the help of connection diagram and phasor diagram, show that two wattmeters are sufficient to measure active power in a three phase three wire system with balanced star connected load. [7M]
- (b) Two wattmeters are used to measure power in a 3-phase three wire load. Determine the total power, power factor and reactive power, if two wattmeter read 5000W each, both positive. [7M]

### MODULE – V

7. (a) What is a filter and classify filters based on frequency characteristics and relation between series and shunt arm impedances. [7M]
- (b) Design a constant K-low pass filter to match with a line having characteristic impedance of  $500\Omega$  and to pass frequency upto 5 kHz. [7M]
8. (a) With T and  $\pi$  configuration, explain constant K low pass filter and constant K high pass filter. [7M]
- (b) Design a proto type section of band pass filter having cut-off frequencies of 12KHz and 16 KHz and a design impedance of 600 ohm. [7M]

— o o ○ o o —