



INSTITUTE OF AERONAUTICAL ENGINEERING

(Autonomous)

Dundigal-500043, Hyderabad

B.Tech III SEMESTER END EXAMINATIONS (REGULAR/SUPPLEMENTARY) - FEBRUARY 2023

Regulation:UG20

ANALOG ELECTRONICS

Time: 3 Hours (ELECTRICAL AND ELECTRONICS ENGINEERING)

Max Marks: 70

Answer ALL questions in Module I and II

Answer ONE out of two questions in Modules III, IV and V

All Questions Carry Equal Marks

All parts of the question must be answered in one place only

MODULE – I

- (a) Illustrate the operation of a PN junction diode in forward and reverse bias condition with its V-I characteristics. [BL: Understand| CO: 1|Marks: 7]
- (b) Determine the parameters I_B , I_C , V_{CE} , V_C , V_E , V_B , V_{BC} for the emitter bias circuit shown in Figure 1. [BL: Apply| CO: 1|Marks: 7]

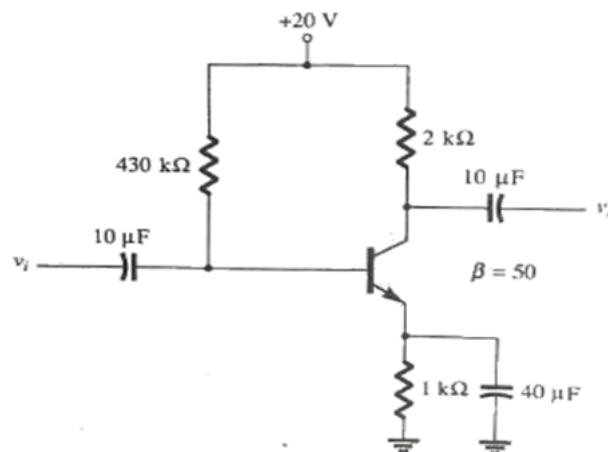


Figure 1

MODULE – II

- (a) Develop the expression for input impedance and output impedance for the common drain amplifier with the help of AC equivalent model. [BL: Understand| CO: 2|Marks: 7]
- (b) For N-channel enhancement MOSFET $V_{GS(Th)}=3V$, $I_{D(ON)}=3mA$, $V_{GS(ON)}=10V$. Calculate the result value of k for the MOSFET and draw the transfer characteristics when $V_{GS}=5V, 8V, 10V, 12V$. [BL: Apply| CO: 2|Marks: 7]

MODULE – III

- (a) With neat diagram explain series fed class A power amplifier and derive the expression for maximum efficiency. [BL: Understand| CO: 3|Marks: 7]

[BL: Apply| CO: 3|Marks: 7]

[BL: Understand| CO: 4|Marks: 7]

[BL: Apply| CO: 4|Marks: 7]

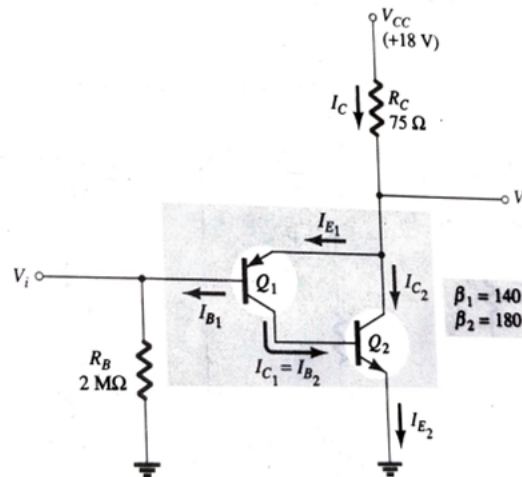


Figure 2

MODULE – IV

[BL: Understand| CO: 5|Marks: 7]

[BL: Apply| CO: 5|Marks: 7]

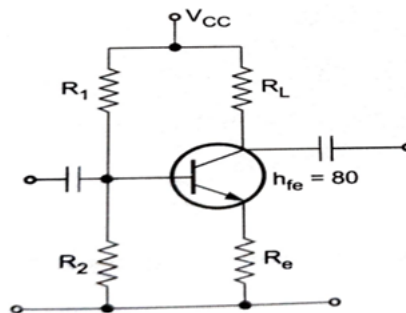


Figure 3

[BL: Understand| CO: 5|Marks: 7]

- (b) Design a RC phase shift oscillator to generate 5KHz sine wave with 20V peak to peak amplitude. Draw the designed circuit. Assume $h_{fe}=150$. [BL: Apply| CO: 5|Marks: 7]

MODULE – V

7. (a) Describe the operation of schmitt trigger using opamp and derive the expression for upper and lower threshold voltage. [BL: Understand| CO: 6|Marks: 7]
- (b) Calculate the output voltage of an inverting summing amplifier for the following set of voltages and resistors. Use $R_f=1M\Omega$,
- i) $V_1=1V$, $V_2=2V$, $V_3=3V$, $R_1=500K\Omega$, $R_2=1M\Omega$, $R_3=1M\Omega$
- ii) $V_1=-2V$, $V_2=3V$, $V_3=1V$, $R_1=200K\Omega$, $R_2=500k\Omega$, $R_3=1M\Omega$ [BL: Apply| CO: 6|Marks: 7]
8. (a) List the specifications of practical operational amplifier. With neat circuit diagram explain the operation of integrator. [BL: Understand| CO: 6|Marks: 7]
- (b) Design a practical differentiator for maximum frequency of 100Hz and draw the output waveform for 1V peak and 100Hz sine wave. [BL: Apply| CO: 6|Marks: 7]

— o o ○ o o —