

$\mathbf{MODULE}-\mathbf{I}$

- 1. (a) Determine the steady-state behavior in a series R-C circuit when exposed to sinusoidal excitation. Develop the essential equations with phasor diagrams. [BL: Understand] CO: 1|Marks: 7]
 - (b) A 50 Ω resistor is connected in series with an inductor having internal resistance, a capacitor and 100 V variable frequency supply as shown in Figure 1. At a frequency of 200 Hz, a maximum current of 0.7 A flows through the circuit and voltage across the capacitor is 200 V. Determine the circuit constants. [BL: Apply] CO: 1|Marks: 7]



Figure 1

$\mathbf{MODULE}-\mathbf{II}$

- (a) Determine the transient response of a series R-L circuit with DC input. Sketch the variation of current and the voltage across the inductor. [BL: Understand] CO: 2|Marks: 7]
 - (b) A series circuit shown in Figure 2 comprising of a resistance of 10 Ω and an inductance of 0.5 H, is connected to a 100 V source at t = 0. Determine the complete expression for the current i(t).

[BL: Apply| CO: 2|Marks: 7]





 $\mathbf{MODULE}-\mathbf{III}$

- 3. (a) Evaluate the attributes of the locus diagram for an RC circuit where resistance is variable and reactance is fixed. Provide a detailed explanation of how the impedance varies concerning frequency in this specific circuit configuration.
 [BL: Understand] CO: 3|Marks: 7]
 - (b) For the parallel circuit shown in Figure 3, V = 200V; $R_2 = 50\Omega$; $X_1 = 25 \Omega$. R_l is varied from 10Ω to 50Ω , draw the locus diagram. Find maximum and minimum values of source current.

[BL: Apply] CO: 3|Marks: 7]



Figure 3

4. (a) What is the substantial impact of poles and zeros on the behavior of network functions, and how do these elements provide insights into the dynamic characteristics of systems?

[BL: Understand] CO: 3 [Marks: 7]

(b) For the network shown in Figure 4, obtain the transfer functions $G_{21}(S)$, $Z_{21}(S)$, and driving-point impedance $Z_{11}(S)$. [BL: Apply] CO: 3|Marks: 7]





$\mathbf{MODULE}-\mathbf{IV}$

5. (a) Describe the arrangement of a three-phase system through star (wye) and delta connections, offering flexibility based on application requirements and electrical characteristics.

[BL: Understand] CO: 4|Marks: 7]

(b) A symmetrical three-phase, three-wire 440 V supply is connected to a star-connected load as shown in Figure 5. The impedances in each branch are $Z_R = (2 + j3) \Omega$, $Z_Y = (1 - j2) \Omega \& Z_B = (3 + j4) \Omega$. Find its equivalent delta-connected load. The phase sequence is RYB. [BL: Apply] CO: 4[Marks: 7]





6. (a) Elaborate three-phase unbalanced delta-connected load, accompanied by a clear sketch. Further, derive the relevant equations for current and voltage in this configuration.

[BL: Understand] CO: 4|Marks: 7]

- (b) The two-wattmeter method is used to measure power in a three-phase load. The wattmeter readings are 400 W and -35 W. Calculate
 - i) Total active power
 - ii) Power factor
 - iii) Reactive power.

[BL: Apply] CO: 4|Marks: 7]

MODULE - V

- 7. (a) Develop the equation for a T-network filter by explaining its components and applying impedance relationships within the network. [BL: Understand| CO: 5|Marks: 7]
 - (b) Design a T and π network of a constant-k low-pass filter having cut-off frequency of 1 kHz, design impedance of 400 Ω . [BL: Apply] CO: 5|Marks: 7]
- 8. (a) Describe the bandpass filter and deduce equations for characteristic impedance, elucidating how this filter allows a specific range of frequencies while maintaining signal quality.

[BL: Understand| CO: 5|Marks: 7]

(b) Design a band-elimination filter having a design impedance of 600Ω and cut-off frequencies $f_1=2$ kHz and $f_2=6$ kHz. [BL: Apply] CO: 5|Marks: 7]

 $-\circ\circ\bigcirc\circ\circ-$