



# INSTITUTE OF AERONAUTICAL ENGINEERING

(Autonomous)  
(Dundigal-500043, Hyderabad)

**B.Tech IV SEMESTER END EXAMINATIONS (REGULAR) - JULY 2022**

**Regulation: UG20**

## ANALOG AND PULSE CIRCUITS

**Time: 3 Hours (ELECTRONICS AND COMMUNICATION ENGINEERING)**

**Max Marks: 70**

**Answer ALL questions in Module I and II**

**Answer ONE out of two questions in Modules III, IV and V**

(NOTE: Provision is given to answer TWO questions from among one of the Modules III / IV / V)

**All Questions Carry Equal Marks**

**All parts of the question must be answered in one place only**

### MODULE – I

1. (a) Discuss the operation of the CE – CE amplifiers with relevant diagrams. List the special features of Darlington pair and cascode amplifiers? [BL: Understand| CO: 1|Marks: 7]
- (b) A CE-CB (cascode) amplifier uses  $R_S = 1K\Omega$ ,  $R_{C1} = 25K\Omega$ ,  $R_E = 100\Omega$ ,  $R_3 = 200K\Omega$ ,  $R_4 = 10K\Omega$ . The h-parameters  $h_{ie} = 2K$ ,  $h_{re} = 0$ ,  $h_{fe} = 100$ ,  $h_{oe} = 0$ ,  $R_1 = 10K\Omega$ ,  $R_2 = 10K\Omega$ . Compute individual & overall  $A_I$  &  $A_V$ ,  $R_i$ ,  $R_o$  &  $R_{ot}$ . [BL: Apply| CO: 1|Marks: 7]

### MODULE – II

2. (a) Enumerate the operation of a current series feedback amplifier with relevant terminologies. [BL: Understand| CO: 2|Marks: 7]
- (b) An amplifier has mid-band gain of 150 and a bandwidth of 300KHz.
  - i) If 4% negative feedback is introduced, find the new bandwidth and gain.
  - ii) If bandwidth is restricted to 1MHz, find the feedback ratio. [BL: Apply| CO: 2|Marks: 7]

### MODULE – III

3. (a) With relevant circuit diagram, explain the operation of Wien-bridge oscillator. [BL: Understand| CO: 3|Marks: 7]
- (b) Determine the following for the circuit given in Figure 1. Consider the base current of 10mA.
  - i) Output power
  - ii) Input power
  - iii) Collector efficiency [BL: Apply| CO: 3|Marks: 7]

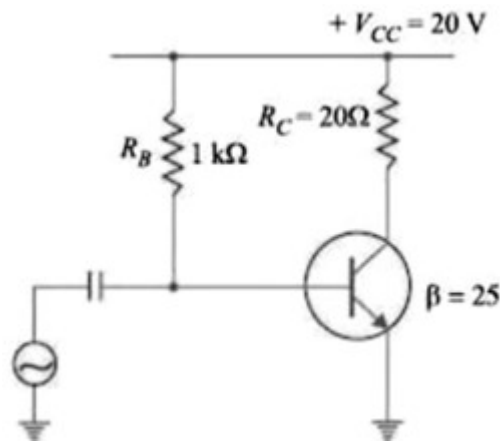


Figure 1

4. (a) With relevant circuit diagram, analyze the operation of Colpitts oscillator.

[BL: Understand| CO: 4|Marks: 7]

- (b) A quartz crystal has the following values after being cut,  $R_s = 1k\Omega$ ,  $C_s = 0.05 \text{ pF}$ ,  $L_s = 3\text{H}$  and  $C_p = 10 \text{ pF}$ . Calculate the crystals series and parallel oscillating frequencies.

[BL: Apply| CO: 4|Marks: 7]

#### MODULE – IV

5. (a) Analyze the responses of low pass RC circuit with square wave input. Compare the difference between sampling gate & logic gate. [BL: Understand| CO: 5|Marks: 7]

- (b) In the circuit given in Figure 2,  $R_L = R_1 = 100k\Omega$ ,  $R_2 = 50k\Omega$  and the signal has a peak value of 20 V. Find

- (i) Gain (A).  
(ii) Minimum positive control voltage, ( $V_{C(min)}$ ).  
(iii) Minimum negative control voltage, ( $V_{n(min)}$ )

[BL: Apply| CO: 5|Marks: 7]

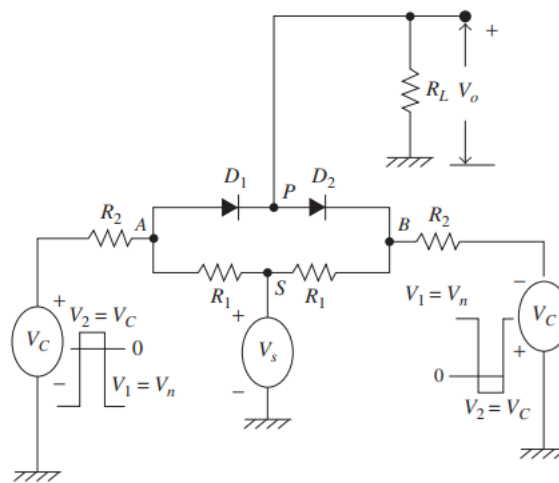


Figure 2

6. (a) With a neat circuit diagram and waveforms explain the operation of high pass RC circuit as a differentiator. [BL: Understand| CO: 5|Marks: 7]

- (b) For the four-diode gate shown in Figure 3, with a divider resistance  $R$  used,  $V_s = 25\text{V}$ ,  $R_f = 20\Omega$ ,  $R_L = R_c = 200K\Omega$  and  $R = 100\Omega$ . Find ( $V_c$ )min, A and ( $V_n$ )min [BL: Apply| CO: 5|Marks: 7]

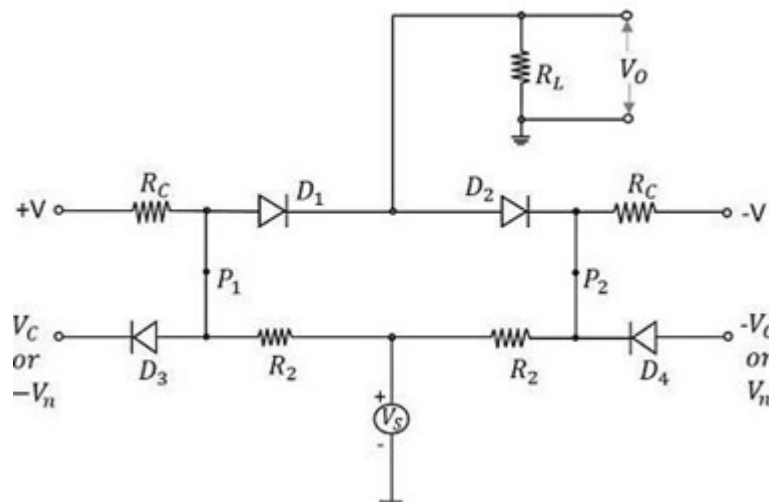


Figure 3

## MODULE – V

7. (a) With a neat circuit diagram and waveforms explain the operation of transistor based monostable multivibrator. [BL: Understand| CO: 6|Marks: 7]
- (b) For the astable multivibrator in Figure 4,  $R_1 = 20k\Omega$ ,  $R_2 = 30k\Omega$ ,  $R_{c1} = 10k\Omega$ ,  $R_{c2} = 10k\Omega$ ,  $C_1 = C_2 = C = 0.01\mu F$ . Find the time period, duty cycle and the frequency. [BL: Apply| CO: 6|Marks: 7]

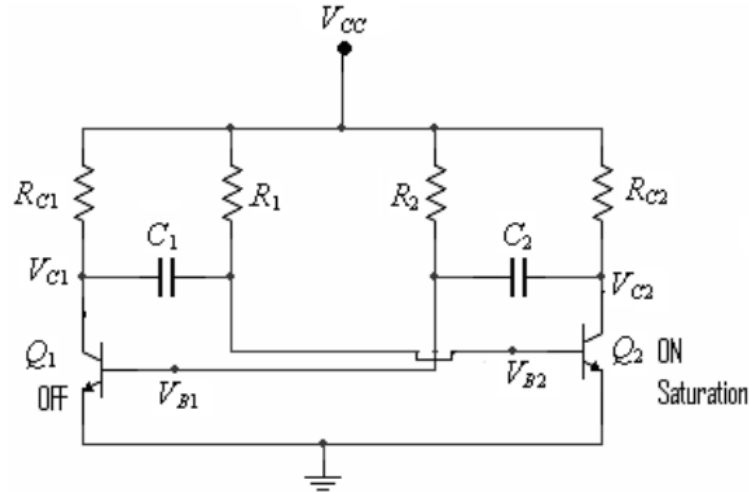


Figure 4

8. (a) With a neat circuit diagram and waveforms explain the operation of transistor based astable multivibrator. [BL: Understand| CO: 6|Marks: 7]
- (b) Consider the schmitt trigger with germanium transistor having  $h_{fe} = 20$ . The circuit parameter are  
 $V_{CC} = 15V$ ,  $R_S = 2K\Omega$ ,  $R_{C1} = 4K\Omega$ ,  $R_1 = 1K\Omega$ ,  
 $R_2 = 10K\Omega$  and  $R_e = 6K\Omega$ .  
 Find LTP and UTP. [BL: Apply| CO: 6|Marks: 7]

— o o ○ o o —