

Code: 13A99302

R13

B.Tech II Year I Semester (R13) Regular Examinations December 2014  
**ELECTRICAL & ELECTRONICS ENGINEERING**  
 (Mechanical Engineering)

Time: 3 hours

Max. Marks: 70

Answer all questions  
 All questions carry equal marks  
 Use separate booklets for part A and part B

\*\*\*\*\*

**PART – A**  
 (Electrical Engineering)

**UNIT – I**

- 1 (a) (i) Explain the operation of 3-point starter used in DC motors with neat diagram.  
 (ii) Deduce the relation between torque and armature current of DC motor.
- OR
- 2 (b) (i) Explain any one type of DC generators.  
 (ii) A short shunt compound generator supplies 200 A at 100 V. The resistance of armature, series field and shunt field are  $0.04 \Omega$ ,  $0.03 \Omega$  and  $60 \Omega$  respectively. Find E.M.F generated.

**UNIT – II**

- 3 (a) (i) Define efficiency and regulation of single phase transformer.  
 (ii) Derive the E.M.F equation of transformer.
- OR
- 4 (b) On what factors the induced EMF in the transformer windings depends. Justify the answer with appropriate derivation.

**UNIT – III**

- 5 (a) (i) Explain the principle of operation of induction motor.  
 (ii) Define the regulation of an alternator and explain how will you find the regulation by synchronous impedance method
- OR
- 6 (b) (i) What is an alternator? Write advantages of stationary armature.  
 (ii) Write short notes on salient pole type alternator.

**PART – B**  
 (Electronics Engineering)

**UNIT – I**

- 7 (a) (i) Explain the formation of n type semiconductor.  
 (ii) Explain the V-I characteristics of a diode.
- OR
- 8 (b) (i) Prove that the voltage regulation for a half wave rectifier is  $[(R_s + R_f)/R_L] * 100$ .  
 (ii) How does the reverse saturation current of diode varies with temperature? Explain.

**UNIT – II**

- 9 (a) (i) Explain the active region, saturation region, cutoff region in transistor characteristics.  
 (ii) With help of neat diagram explain the operation of an N –channel JFET
- OR
- 10 (b) (i) If the base current in a transistor is  $30 \mu\text{A}$  when the emitter current is  $7.2 \text{ mA}$ , what are the values of  $\alpha$  and  $\beta$  and also calculate the collector current.  
 (ii) Draw and explain the drain characteristics of n- channel enhancement type MOSFET.

**UNIT – III**

- 11 (a) (i) Convert the following binary numbers into decimals:  
 (1) 101.01      (2) 10101.0101  
 (ii) Construction of AND, OR and NOT gate by using NOR gate.
- OR
- 12 (b) (i) Simplify the logical expression  $(A+B).(A+\bar{B}).(\bar{A} + B)$ .  
 (ii) Convert the octal  $(1745.246)_8$  number into hexadecimal number.

\*\*\*\*\*