

Code No: 113BR

R13

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD

B.Tech II Year I Semester Examinations, December-2014

BASIC ELECTRICAL ENGINEERING

(Common to CSE, IT)

Time: 3 Hours

Max. Marks: 75

Note: This question paper contains two parts A and B.
Part A is compulsory which carries 25 marks. Answer all questions in Part A.
Part B consists of 5 Units. Answer any one full question from each unit.
Each question carries 10 marks and may have a, b, c as sub questions.

Part- A

(25 Marks)

- 1.a) State and explain KCL and KVL. [2M]
- b) State and explain Norton's theorem. [3M]
- c) Define RMS and Average value of an alternating quantity. [2M]
- d) A coil has a resistance of 4Ω and an inductance of 9.55 mH . Calculate (i) the reactance, (ii) the impedance, and (iii) the current taken from a 240 V , 50 Hz supply. [3M]
- e) Why rating of the transformer is given in KVA? Explain. [2M]
- f) Draw and explain the phasor diagram of single phase transformer on no load. [3M]
- g) Explain the principle of DC motor operation. [2M]
- h) Write the similarities between transformer and induction motor. [3M]
- i) What are the different types torques acting on the moving system of measuring instrument? [2M]
- j) Explain how the deflecting torque provided in a moving system of a measuring instrument? [3M]

Part-B

(50 Marks)

- 2.a) For the circuit shown in Figure 1, calculate the current I and voltage V_{ab} when
i) $R_x = 0 \Omega$ ii) $R_x = 15 \text{ K}\Omega$ iii) $R_x = \infty \Omega$.

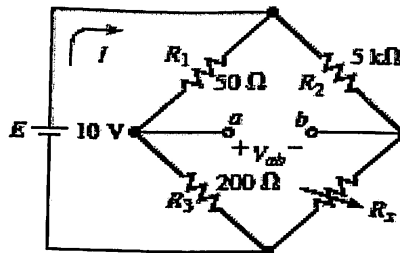


Figure 1

- b) For the arrangement shown in Figure 2 find:
 i) the equivalent capacitance of the circuit and
 ii) the voltage across a $4.5 \mu\text{F}$ capacitor.

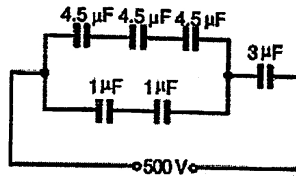


Figure 2
OR

- 3.a) Find the value of R_L for maximum power transfer in the circuit shown in Figure 3. Find the maximum power.

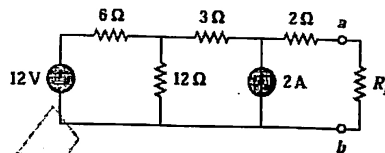


Figure 3

- b) State and explain thevenin's theorem with an example.
- 4.a) Calculate:
 i) The admittance Y
 ii) The conductance G and
 iii) Susceptance B of a circuit consisting of a resistor of 10Ω in series with an inductor of 0.3 H , when the frequency is 50 Hz .
- b) A resistance of 10 Ohms , an inductive reactance of 5 Ohms , and a capacitive reactance of 10 Ohms are connected in parallel with each other across a supply of $230 \angle 45^\circ \text{ Volts}$. Calculate
 i) Impedance and admittance of each branch
 ii) Current in each branch
 iii) Total current drawn from the supply
 iv) Draw the phasor diagram.

OR

- 5.a) A 20Ω resistance and 30 mH inductance are connected in series and the circuit is fed from a 220 V , 50 Hz AC supply. Find
 i) Reactance across the inductance, impedance, admittance, current
 ii) Voltage across the resistance
 iii) Voltage across the inductance
 iv) Real, reactive and active powers
 v) Power factor
- b) The waveform shown in Figure 4 is a half-wave rectified sine wave. Find the rms value and the amount of average power dissipated in a 10Ω resistor.

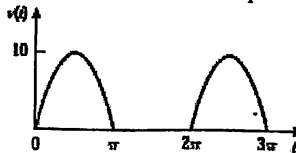


Figure 4

- 6.a) Explain the working principle of single phase transformer.
- b) A 5 KVA single-phase transformer has a turns ratio of 10:1 and is fed from a 2.5 kV supply. Neglecting losses, determine:
- the full-load secondary current
 - the minimum load resistance which can be connected across the secondary winding to give full load KVA
 - the primary current at full load KVA.

OR

- 7.a) Enumerate the various losses in a transformer. How can these losses be minimized?
- b) A 2400 V/400 V single-phase transformer takes a no load current of 0.5 A and the core loss is 400 W. Determine the values of the magnetizing and core loss components of the no load current. Draw to scale the no-load phasor diagram for the transformer.

- 8.a) Based on the type of excitation classify the DC generators.
- b) A 4-pole armature of a d.c. machine has 1000 conductors and a flux per pole of 20 mWb. Determine the e.m.f. generated when running at 600 rev/min when the armature is:
- wave-wound
 - lap-wound.

OR

- 9.a) Explain the working principle of three phase induction motor.
- b) A 3-phase, 60-Hz induction motor has 2 poles. If the slip is 2% at a certain load, determine:
- the synchronous speed
 - the speed of the rotor and
 - the frequency of the induced e.m.f.'s in the rotor.

10. With the help of a neat sketch explain the construction and operation of PMMC instrument.

OR

- 11.a) Discuss the classification of electrical instruments.
- b) Explain the significance of controlling torque and damping torque relevant to the operation of indicating instrument.