

Code No: 113BS

R13

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD

B.Tech II Year I Semester Examinations, December-2014

DIGITAL LOGIC DESIGN

(Computer Science and Engineering)

Time: 3 Hours

Max. Marks: 75

Note: This question paper contains two parts A and B.

Part A is compulsory which carries 25 marks. Answer all questions in Part A.

Part B consists of 5 Units. Answer any one full question from each unit.

Each question carries 10 marks and may have a, b, c as sub questions.

Part- A

(25 Marks)

- 1.a) What are the simplest technique for detecting errors? [2M]
- b) What are the basic operations in Boolean algebra? [3M]
- c) What is race around condition? How it is avoided? [2M]
- d) What is maxterm? [3M]
- e) What is a ripple carry-adder? [2M]
- f) What is a priority encoder? [3M]
- g) What is a full modulus counter? [2M]
- h) What are the various methods used for triggering flip-flops? [3M]
- i) What are types of ROM? [2M]
- j) What is PLA? [3M]

Part- B

(50 Marks)

- 2.a) Covert 105.15_{10} to binary, octal, hexadecimal.
 - b) What is hamming code? How is the hamming code word tested and corrected.
- OR**
- 3.a) Simplify the following Boolean expressions using the Boolean theorems.
 - i) $(A+B+C)(B'+C) + (A+D)(A'+C)$
 - ii) $(A+B)(A+B')(A'+B)$
 - b) Why a NAND and NOR gates are known as universal gates? Simulate all the gates.
- 4.a) Simplify $Y = \sum m(3, 6, 7, 8, 10, 12, 14, 17, 19, 20, 21, 24, 25, 27, 28)$ using K-map method.
 - b) Obtain
 - i) minimal SOP and
 - ii) minimal POS expressions for the following function
$$F(A, B, C, D) = \sum m(0, 1, 5, 8, 9, 10)$$
- OR**
5. Obtain the minimal SOP expression for the switching function using k-map.
$$Y = \sum m(1, 5, 7, 13, 14, 15, 17, 18, 21, 22, 25, 29) + \sum d(6, 9, 19, 23, 30)$$
Draw and explain the logic diagram.

- 6.a) Draw the schematic diagram and truth table for full adder. Explain the design approach for full adder using universal gates. Draw the relevant logic diagrams with necessary expressions.
- b) Draw and explain the operation of 2's complement adder-subtractor.

OR

- 7.a) Explain the differences between a MUX and a DEMUX. Realize 16-input multiplexer by cascading of two 8-input multiplexers 74151.
- b) Realize the function $f(A, B, C, D) = \prod(1, 4, 6, 10, 14) + d(0, 8, 11, 15)$ using
i) 16:1 MUX ii) 8:1 MUX.

- 8.a) What is meant by 'edge triggered'? Differentiate SR-FF and JK-FF with their functional operation and excitation tables.
- b) Draw and explain the circuit diagram of positive edge triggered J-K flip-flop using NOR gates with its truth table. How race around conditions are eliminated?

OR

- 9.a) Discuss about synchronous and ripple counters. Compare their merits and demerits.
- b) What do you mean by universal shift register? Draw and explain its circuit diagram and operation.

- 10.a) Tabulate the PLA programming table for the following Boolean functions.

$$A(x, y, z) = \sum m(0, 2, 3, 7)$$

$$B(x, y, z) = \sum m(1, 3, 4, 6)$$

$$C(x, y, z) = \sum m(1, 4)$$

Draw and explain the relevant logic diagram.

- b) Design, draw and explain 128×8 ROM using 32×8 ROM.

OR

- 11.a) Using PLA logic, implement a BCD to excess-3 code converter. Draw and explain its truth table and logic diagram.
- b) Explain in brief, about logic construction of 32×4 ROM. Draw and explain the relevant logic diagram.