

--	--	--	--	--	--	--	--	--	--



INSTITUTE OF AERONAUTICAL ENGINEERING

(Autonomous)

Four Year B.Tech III Semester End Examinations (Regular) - November, 2018

Regulation: IARE – R16

NETWORK ANALYSIS

Time: 3 Hours

(EEE)

Max Marks: 70

Answer ONE Question from each Unit

All Questions Carry Equal Marks

All parts of the question must be answered in one place only

UNIT – I

- (a) Deduce the relationship between phase and line quantities of voltage and currents in a 3Φ , 3-wire star connected system. [7M]

(b) A three phase balanced delta connected load of $(4+j8)\ \Omega$ is connected across a 400V, 3Φ balanced supply. Determine the phase current and line current. Assume RYB phase sequence. Calculate the power drawn by the load. [7M]
- (a) Sketch the circuit waveforms and the phasor diagram for a Y-connected generator with phase sequence RYB. Repeat for a generator with sequence BYR. Explain why the phase sequence is necessary. [7M]

(b) The power readings of two wattmeters are +15kW and -4kW for a three phase load. If the supply voltage is balanced 440V. Find the true power drawn by the load, the power factor and line current. [7M]

UNIT – II

- (a) Briefly, discuss the transient response in RL circuit with DC excitation. [7M]

(b) In a RC series circuit $R = 1\ \Omega$ and $C = 0.5F$. A DC voltage $V=10v$ is suddenly applied at $t=0$. Obtain $i(t)$. Assume no initial charge in the capacitor. [7M]
- (a) A time dependent voltage $V(t)$ is applied to a series connection of RLC network. Find s-domain impedance and current. Assume initial condition of the voltage in inductor to be assisting the input current and that in capacitor opposing the input current. Draw the t-domain and s-domain circuits. [7M]

(b) In a series R-L-C circuit, $R = 5\ \Omega$, $L = 1H$ and $C = 1F$. A DC voltage of 20V is applied at $t=0$. Obtain $i(t)$. [7M]

UNIT – III

5. (a) Define network function. Classify the different types of network functions and explain. [7M]
 (b) Compute the driving point impedance of the circuit shown in Figure 1 [7M]

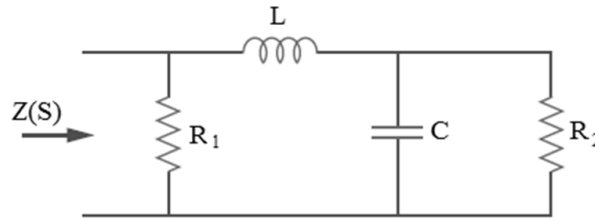


Figure 1

6. (a) State and explain the significance of poles and zeros in network function. [7M]
 (b) For the given network function, draw the pole zero plot. And also compute the time domain response of $V(s) = 24 (S^2+9) / (S + 2)(S + 8)$. [7M]

UNIT – IV

7. (a) Compute the open circuit parameters of two port network shown in Figure 2. [7M]

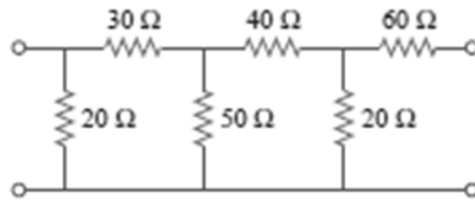


Figure 2

- (b) In the bridge circuit of Figure 3 , $I_1 = 10\text{ A}$ and $I_2 = -4\text{ A}$. Find V_1 and V_2 using Y parameters. [7M]

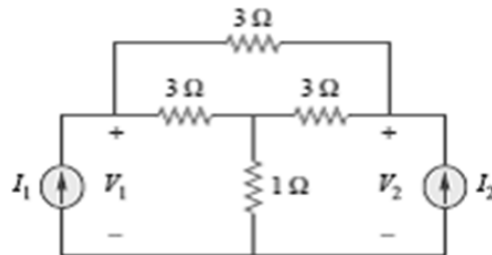


Figure 3

8. (a) Discuss the condition of reciprocity and symmetry in h-parameter representation. [7M]
 (b) In a two port network, $Z_{11}=2\Omega$, $Z_{21}=Z_{12}=5\Omega$, $Z_{22}= 1\Omega$ Find: [7M]
 (i) Y-parameters
 (ii) h-parameters
 (iii) ABCD parameters

UNIT – V

9. (a) A filter section is required to have a nominal impedance of 600Ω , a cut-off frequency of 5 kHz and a frequency of infinite attenuation at 5.50 kHz. Design (i) An appropriate ‘m-derived’ T section (ii) An appropriate ‘m-derived’ π section. [7M]
 (b) A high-pass T section filter has a cut-off frequency of 500 Hz and a nominal impedance of 600Ω . Determine the frequency at which the characteristic impedance of the section is (i) Zero (ii) 300Ω (iii) 590Ω [7M]
10. (a) A filter section is to have a characteristic impedance at zero frequency of 600Ω and a cut-off frequency at 5 MHz. Design (i) A low-pass T section filter (ii) A low-pass π section filter to meet these requirements. [7M]
 (b) Determine for each of the filter sections shown in Figure 4, (i) The cut-off frequency (ii) The nominal impedance. [7M]

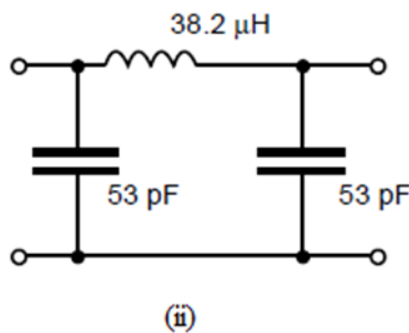
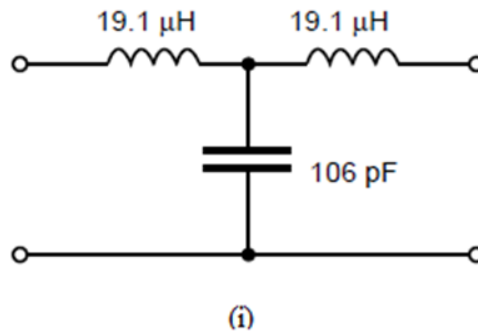


Figure 4