

--	--	--	--	--	--	--	--	--	--



INSTITUTE OF AERONAUTICAL ENGINEERING

(Autonomous)

Four Year B.Tech V Semester End Examinations (Regular) - November, 2018

Regulation: IARE – R16

POWER ELECTRONICS

Time: 3 Hours

(EEE)

Max Marks: 70

Answer ONE Question from each Unit

All Questions Carry Equal Marks

All parts of the question must be answered in one place only

UNIT – I

1. (a) Distinguish between the power MOSFET and BJT. [7M]
- (b) The trigger circuit of a thyristor has a source voltage of 15V and line has a slope of -120V per ampere. The minimum gate current to turn-on the SCR is 25mA. Compute the [7M]
 - i. Source resistance required in the gate circuit
 - ii. The trigger voltage and trigger current for an average gate power dissipation of 0.4Watts.
2. (a) Explain the various types of commutation circuits for SCR. [7M]
- (b) For an SCR, gate-cathode characteristics is given by $V_g = 1 + 10I_g$. Gate source voltage is a rectangular pulse of 15V with 20 μ sec duration. For an average gate power dissipation of 0.3W and a peak gate drive power of 5W, compute [7M]
 - i. The resistance to be connected in series with the SCR gate,
 - ii. The duty cycle of the triggering pulse.

UNIT – II

3. (a) Explain the working of a single phase fully - controlled bridge converter in the inversion mode. [7M]
- (b) With suitable circuit topology, voltage and current waveforms, reflect the effect of input source impedance on the average output of a single phase fully controlled converter. [7M]
4. (a) Discuss the various performance factors of line commutated converters. [7M]
- (b) A single phase fully controlled bridge converter supplies an inductive load. Assume that the output - current is virtually constant, and is equal to I_d , determine the following performance parameters. The supply voltage is 230V and firing angle is maintained at $(\pi/6)$ radians. [7M]
 - i. Average output voltage
 - ii. Supply RMS
 - iii. fundamental power factor.
 - iv. Voltage ripple factor.

UNIT – III

5. (a) Describe the operation of single phase full wave AC voltage controller with the help of voltage and current waveforms. [7M]
- (b) A single phase voltage controller is employed for controlling the power flow from 230V, 50 Hz source into a load circuit consisting of $R=3\Omega$ and $\omega L=4\Omega$, Calculate [7M]
- i. The control range of firing angle
- ii. The Maximum value of rms load current
6. (a) Explain the principle of operation and working of single phase to single phase step-up cycloconverter. [7M]
- (b) Explain the advantages and disadvantages of Cycloconverter and AC Voltage controller. [7M]

UNIT – IV

7. (a) Explain the current limit control method of the output voltage control of choppers. A step - up chopper is used to deliver load voltage of 500 V from a 220 V DC source. If the blocking period of the thyristor is $80 \mu s$. Compute the required pulse width. [7M]
- (b) Explain the working of a Cuk converter with a neat circuit diagram and associated voltage and current waveforms. [7M]
8. (a) Describe the working principle of buck-boost converter with necessary circuit and waveforms. [7M]
- (b) For type A chopper feeding RLE load, obtain maximum value of average current rating for the thyristor in case load current remains constant. [7M]

UNIT – V

9. (a) Discuss the functioning of three phase voltage source inverter in 120 degree operating mode with relevant waveforms and obtain the expression for voltage. [7M]
- (b) A single phase full bridge inverter is fed from a DC source such that fundamental component of output voltage is 230V. Find the RMS value of thyristor and diode current for $R=2 \Omega$ load. [7M]
10. (a) Compare the Voltage Source and Current Source Inverters. [7M]
- (b) Explain the working of a basic parallel inverter with neat circuit and related circuit voltage and current waveforms. [7M]

