

# **ELECTRICAL AND ELECTRONICS ENGINEERING LABORATORY**

## **LAB MANUAL**

<b>Year</b>	<b>:</b>	<b>2017- 2018</b>
<b>Subject Code</b>	<b>:</b>	<b>AEE101</b>
<b>Regulations</b>	<b>:</b>	<b>R16</b>
<b>Class</b>	<b>:</b>	<b>B. Tech II Semester</b>
<b>Branch</b>	<b>:</b>	<b>CSE</b>

### **Prepared by**

Ms. Lekha chandran  
Associate Professor

Mr. K Lingaswamy Reddy  
Assistant Professor

Mr. P Mabu Hussain  
Assistant Professor

Mr. N Shivaprasad  
Assistant Professor



**Electrical and Electronics Engineering**

**INSTITUTE OF AERONAUTICAL ENGINEERING**

(Autonomous)

Dundigal, Hyderabad - 500 043



# INSTITUTE OF AERONAUTICAL ENGINEERING

(Autonomous)

Dundigal, Hyderabad - 500 043

## ELECTRICAL AND ELECTRONICS ENGINEERING

<b>Program Outcomes</b>	
<b>PO1</b>	<b>Engineering Knowledge:</b> Apply the knowledge of mathematics, science, engineering fundamentals, and an engineering specialization to the solution of complex engineering problems.
<b>PO2</b>	<b>Problem Analysis:</b> Identify, formulate, review research literature, and analyze complex engineering problems reaching substantiated conclusions using first principles of mathematics, natural sciences, and engineering sciences.
<b>PO3</b>	<b>Design / Development of Solutions:</b> Design solutions for complex engineering problems and design system components or processes that meet the specified needs with appropriate consideration for the public health and safety, and the cultural, societal, and environmental considerations.
<b>PO4</b>	<b>Conduct Investigations of Complex Problems:</b> Use research-based knowledge and research methods including design of experiments, analysis and interpretation of data, and synthesis of the information to provide valid conclusions.
<b>PO5</b>	<b>Modern Tool Usage:</b> Create, select, and apply appropriate techniques, resources, and modern engineering and IT tools including prediction and modeling to complex engineering activities with an understanding of the limitations.
<b>PO6</b>	<b>The engineer and society:</b> Apply reasoning informed by the contextual knowledge to assess societal, health, safety, legal and cultural issues and the consequent responsibilities relevant to the professional engineering practice.
<b>PO7</b>	<b>Environment and Sustainability:</b> Understand the impact of the professional engineering solutions in societal and environmental contexts, and demonstrate the knowledge of, and need for sustainable development.
<b>PO8</b>	<b>Ethics:</b> Apply ethical principles and commit to professional ethics and responsibilities and norms of the engineering practice.
<b>PO9</b>	<b>Individual and Team Work:</b> Function effectively as an individual, and as a member or leader in diverse teams, and in multidisciplinary settings.
<b>PO10</b>	<b>Communication:</b> Communicate effectively on complex engineering activities with the engineering community and with society at large, such as, being able to comprehend and write effective reports and design documentation, make effective presentations, and give and receive clear instructions.
<b>PO11</b>	<b>Project Management and Finance:</b> Demonstrate knowledge and understanding of the engineering and management principles and apply these to one's own work, as a member and leader in a team, to manage projects and in multidisciplinary environments.
<b>PO12</b>	<b>Life - Long Learning:</b> Recognize the need for, and have the preparation and ability to engage in independent and life-long learning in the broadest context of technological change.
<b>Program Specific Outcomes</b>	
<b>PSO1</b>	<b>Professional Skills:</b> The ability to research, understand and implement computer programs in the areas related to algorithms, system software, multimedia, web design, big data analytics, and networking for efficient analysis and design of computer-based systems of varying complexity.
<b>PSO2</b>	<b>Problem - Solving Skills:</b> The ability to apply standard practices and strategies in software project development using open-ended programming environments to deliver a quality product for business success.
<b>PSO3</b>	<b>Successful Career and Entrepreneurship:</b> The ability to employ modern computer languages, environments, and platforms in creating innovative career paths, to be an entrepreneur, and a zest for higher studies.

## INDEX

S. No.	List of Experiments	Page No.
1	Verification of KVL and KCL.	6-8
2	Verification of Superposition theorem	9-10
3	Verification of Thevenin's theorems.	11-12
4	Verification of Norton's theorems.	13-14
5	Verification of Maximum power transfer theorem.	15-17
6	Verification of KVL and KCL using digital simulation.	18-20
7	Verification of Superposition theorem and Thevenin's theorem using digital simulation.	21-23
8	Verification of Norton's theorem and Maximum power transfer theorem using digital simulation.	24-26
9	Volt ampere characteristics of P-N junction diode	27-29
10	Zener diode V-I Characteristics	30-34
11	Application of diode as half wave rectifier and full wave rectifier	35-44
12	Verify the characteristics of common base transistor.	45-48
13	Verify the characteristics of common emitter transistor.	49-53

## ATTAINMENT OF PROGRAM OUTCOMES & PROGRAM SPECIFIC OUTCOMES

<b>Exp. No.</b>	<b>Experiment</b>	<b>Program Outcomes Attained</b>	<b>Program Specific Outcomes Attained</b>
1	Verification of KVL and KCL.	P01,P02,P03,P012	PSO1,PSO2
2	Verification of Superposition theorem	P01,P02,P03,P012	PSO1,PSO2
3	Verification of Thevenin's theorems.	P01,P02,P03,P012	PSO1,PSO2
4	Verification of Norton's theorems.	P01,P02,P03,P012	PSO1,PSO2
5	Verification of Maximum power transfer theorem.	P01,P02,P03,P012	PSO1,PSO2
6	Verification of KVL and KCL using digital simulation.	P01,P02,P03,P012	PSO1,PSO2
7	Verification of Superposition theorem and Thevenin's theorem using digital simulation.	P01,P02,P03,P012	PSO1,PSO2
8	Verification of Norton's theorem and maximum power transfer theorem using digital simulation.	P01,P02,P03,P012	PSO1,PSO2
9	Volt Ampere characteristics of P-N junction diode	P01,P02,P03,P012	PSO1,PSO2
10	Zener diode V-I Characteristics	P01,P02,P03,P012	PSO1,PSO2
11	Application of diode as half wave rectifier and full wave rectifier	P01,P02,P03,P012	PSO1,PSO2
12	Verify the characteristics of common base transistor.	P01,P02,P03,P012	PSO1,PSO2
13	Verify the characteristics of common emitter transistor.	P01,P02,P03,P012	PSO1,PSO2

# ELECTRICAL AND ELECTRONICS LABORATORY

## OBJECTIVE:

This lab complements the electrical and electronics devices circuits' course. Students will gain practical experience with identification of all the basic electrical and electronic components. After going through this course the student gets a thorough knowledge on basic electrical circuits, With which he / she can able to apply the above conceptual things to real-world electrical and electronics problems and applications.

## OUTCOMES:

Upon the completion of electrical and electronics practical course, the student will be able to:

1. **Understand** the circuit theorems and various electrical components.
2. **Design** the electrical circuit theorems by using digital simulation.
3. **Analyze** the characteristics of various electronics components.

## EXPERIMENT - 1

### VERIFICATION OF KVL AND KCL

#### AIM:

To verify Kirchoff's voltage law (KVL) and Kirchoff's current law (KCL) in a passive resistive network

#### APPARATUS:

S.No.	Equipment	Range	Type	Quantity
1.	Ammeter			
2.	Voltmeter			
3.	R.P.S			
4.	Bread Board			
5.	Resistors			
6.	Connecting Wires			As required

#### CIRCUIT DIAGRAMS:

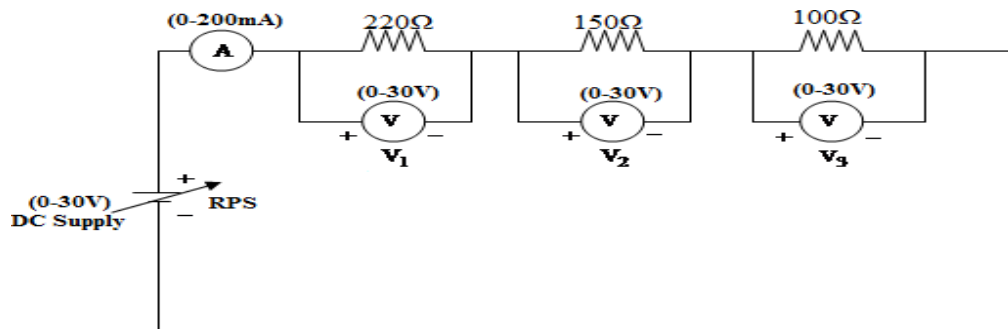


Figure – 1.3.1 Verification of KVL

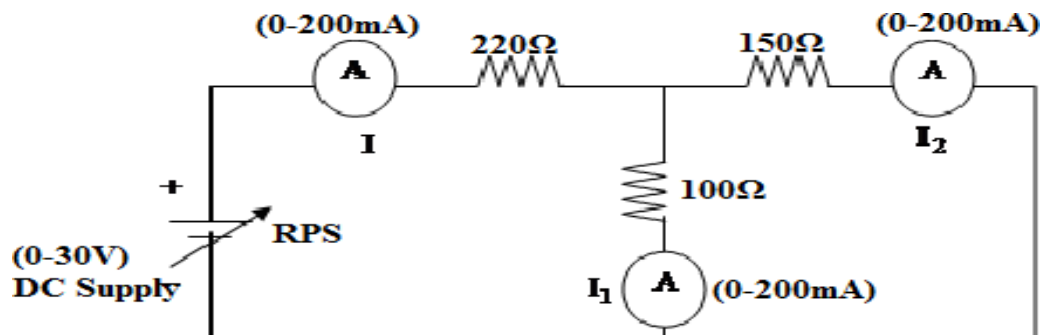


Figure – 1.3.2 Verification of KCL

**PROCEDURE:****To Verify KVL**

1. Connect the circuit diagram as shown in Fig. 1.3.1.
2. Switch ON the supply to RPS.
3. Apply the voltage (say 5V) and note the voltmeter readings.
4. Gradually increase the supply voltage in steps.
5. Note the readings of voltmeters.
6. Sum up the voltmeter readings (voltage drops) , that should be equal to applied voltage .
7. Thus KVL is verified practically.

**To Verify KCL**

1. Connect the circuit diagram as shown in Fig. 1.3.2.
2. Switch ON the supply to RPS.
3. Apply the voltage (say 5V) and note the Ammeter readings.
4. Gradually increase the supply voltage in steps.
5. Note the readings of Ammeters.
6. Sum up the Ammeter readings ( $I_1$  and  $I_2$ ), that should be equal to total current ( $I$ ).
7. Thus KCL is Verified practically

**OBSERVATIONS:****For KVL**

Applied Voltage V (volts)	$V_1$ (volts)		$V_2$ (volts)		$V_3$ (volts)		$V_1+V_2+V_3$ (volts)	
	Theoretical	Practical	Theoretical	Practical	Theoretical	Practical	Theoretical	Practical

**For KCL**

Applied Voltage V (volts)	I (A)		$I_1$ (A)		$I_2$ (A)		$I_1+I_2$ (A)	
	Theoretical	Practical	Theoretical	Practical	Theoretical	Practical	Theoretical	Practical

**PRECAUTIONS:**

1. Check for proper connections before switching ON the supply
2. Make sure of proper color coding of resistors
3. The terminal of the resistance should be properly connected.

**RESULT:****PRE LAB VIVA QUESTIONS:**

1. Define current.
2. Define voltage.
3. Describe resistance?
4. State ohm's law.
5. What is KCL and KVL?

**POST LAB VIVA QUESTIONS:**

1. What do you mean by junction?
2. Derive current division rule.
3. What are the positive and negative signs in KVL?
4. Describe the colour coding of resistors.
5. What are the precautions to be taken while doing the experiment?
6. What is the range of ammeters and voltmeters you used in this experiment?



## EXPERIMENT - 2

### VERIFICATION OF SUPERPOSITION THEOREM

#### AIM:

To verify superposition theorem theoretically and practically

#### APPARATUS:

S.No.	Equipment	Range	Type	Quantity
1.	Ammeter			
2.	Voltmeter			
3.	R.P.S			
4.	Bread Board			
5.	Resistors			
6.	Connecting Wires			As required

#### CIRCUIT DIAGRAM:

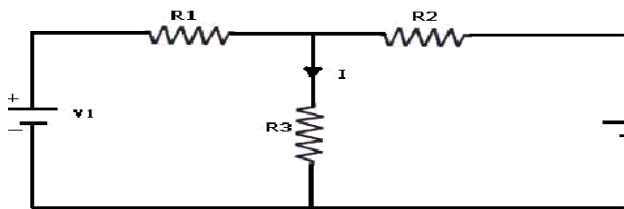


Fig- 2.3.1 Both Voltage Sources are acting ( $V_1$  &  $V_2$ )

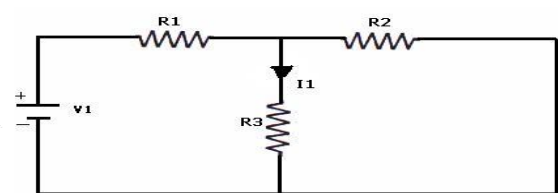


Fig - 2.3.2 Voltage Source  $V_1$  is acting alone

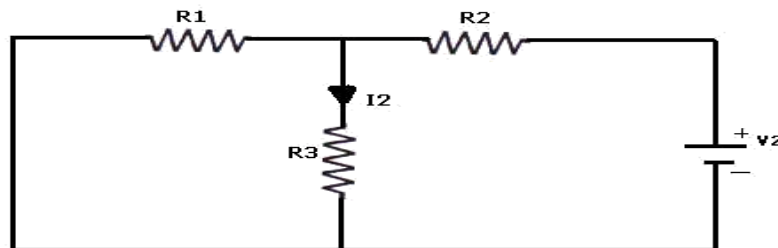


Fig - 2.3.3 Voltage Source  $V_2$  is acting alone

#### PROCEDURE:

1. Connect the circuit as shown in fig. (2.3.1) and note down the current flowing through  $R_3$  and let it be  $I$ .
2. Connect the circuit as shown in fig. (2.3.2) and note down the ammeter Reading, and let it be  $I_1$ .
3. Connect the circuit as shown in fig. (2.3.3) and note down the ammeter reading, and let it be  $I_2$ .
4. Verify for  $I=I_1+I_2$ .
5. Compare the practical & theoretical currents.

#### PRECAUTIONS:

1. Check for proper connections before switching ON the supply
2. Make sure of proper colour coding of resistors
3. The terminal of the resistance should be properly connected.

**RESULT:**

**PRE LAB VIVA QUESTIONS:**

1. Define voltage.
2. Define current.
3. Ammeter is connected in series or parallel?
4. Voltmeter is connected in series or parallel?
5. Define mesh.
6. State ohm's law
7. State superposition theorem.

**LAB ASSIGNMENT:**

1. Explain KVL & KCL with required circuits

**POST LAB VIVA QUESTIONS:**

1. Discuss the current division rule.
2. Discuss the voltage division rule.
3. State KCL.
4. State KVL.
5. Explain the color coding of resistors.

## EXPERIMENT - 3

### VERIFICATION OF THEVENIN'S THEOREM

#### AIM:

To verify Thevenin's theorem

#### STATEMENT:

Any linear, bilateral network having a number of voltage, current sources and resistances can be replaced by a simple equivalent circuit consisting of a single voltage source in series with a resistance, where the value of the voltage source is equal to the open circuit voltage and the resistance is the equivalent resistance measured between the open circuit terminals with all energy sources replaced by their internal resistances

#### APPARATUS:

S.No.	Equipment	Range	Type	Quantity
1.	Ammeter			
2.	Voltmeter			
3.	R.P.S			
4.	Bread Board			
5.	Resistors			
6.	Connecting Wires			As required

#### CIRCUIT DIAGRAM:

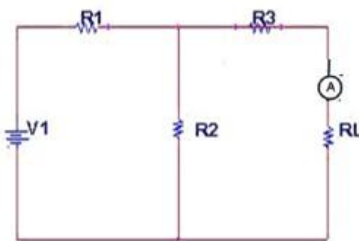


Fig-3.4.1 Measurement of  $I_L$

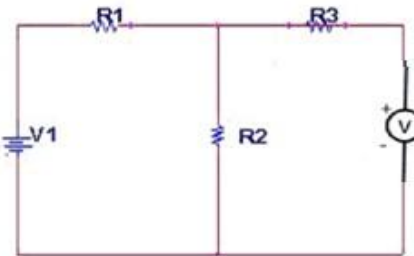


Fig – 3.4.2 Measurement of  $V_{TH}$

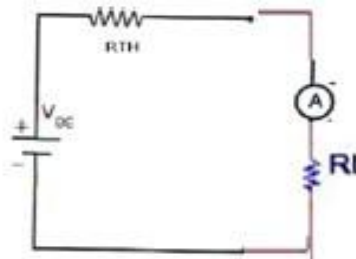


Fig – 3.4.3 Measurement of  $I_L$  ( $I_L = V_{TH}$  or  $V_{OC} / R_{TH} + R_L$ )

**PROCEDURE:**

1. Connect the circuit diagram as shown in fig. 3.4.1
2. Measure current in  $R_L$
3. Connect the circuit as shown in fig. 3.4.2.
4. Measure open circuit voltage  $V_{oc}$  by open circuiting terminals i.e.  $V_{TH}$
5. Draw the Thevenin's equivalent circuit as shown in fig. 3.4.2
6. Measurement current in  $R_L$

**RESULT:****PRE LAB VIVA QUESTIONS:**

1. What is load resistance?
2. How will you calculate thevenin's resistance  $R_{TH}$ ?
3. How will you calculate thevenin's voltage  $V_{TH}$ ?

**LAB ASSIGNMENT:**

1. Solve the theoretical value of thevenin's theorem for different circuits

**POST LAB VIVA QUESTIONS**

1. Explain series connection.
2. Explain parallel connection.
3. State Thevenin's theorem.

## EXPERIMENT - 4

### VERIFICATION OF NORTON'S THEOREM

#### AIM:

To verify Norton's theorem

#### STATEMENT:

Any linear, bilateral network with current sources, voltage sources and resistances can be replaced by an equivalent circuit consisting of a current source in parallel with a resistance. The value of the current source is the short circuit current between the short circuit terminals of the network and the resistance is the equivalent resistance measured between the terminals of the network with all the energy sources replaced by their internal resistances.

#### APPARATUS:

S.No.	Equipment	Range	Type	Quantity
1.	Ammeter			
2.	Voltmeter			
3.	R.P.S			
4.	Bread Board			
5.	Resistors			
6.	Connecting Wires			As required

#### CIRCUIT DIAGRAM:

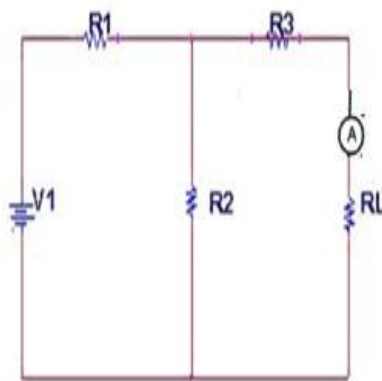


Fig – 4.3.1 Measurement of  $I_L$

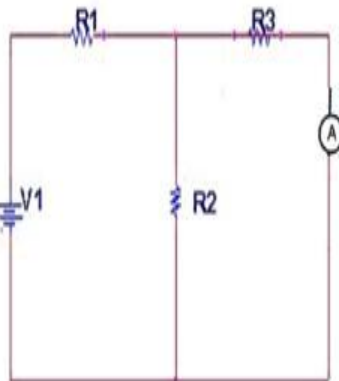


Fig – 4.3.2 Measurement of  $I_N$

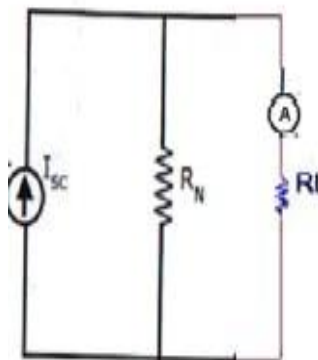


Fig – 4.3.3 Measurement of  $I_L$

**PROCEDURE:**

1. Connect the circuit diagram as shown in fig. 4.3.1.
2. Measure current in  $R_L$
3. Connect the circuit diagram as shown in fig. 4.3.2.
4. Measure the short circuit current  $I_{sc}$  (or)  $I_N$  by short circuiting the load resistance
5. Draw Norton's equivalent circuit by connecting  $I_N$  &  $R_N$  in parallel as shown in fig. 4.3.3,
6. Note down the load current  $I_L$

**TABULAR COLUMN:**

Parameters	Theoretical Values	Practical Values
$V_{OC}$		
$I_{SC}$		
$R_{TH}$		
$I_{RL}$		

**RESULT:****PRE LAB VIVA QUESTIONS:**

1. What is load resistance?
2. How will you calculate Norton's resistance  $R_N$ ?
3. How will you calculate Norton's current  $I_N$ ?
4. What is Norton's current?

**LAB ASSIGNMENT:**

1. Solve the theoretical value of Norton's current for different circuits.

**POST LAB VIVA QUESTION**

1. State Norton's theorem.
2. Explain series connection.
3. Explain parallel connection.

## EXPERIMENT – 5

### MAXIMUM POWER TRANSFER THEOREM

#### AIM:

To verify maximum power transfer theorem

#### STATEMENT:

The maximum power transfer theorem states that maximum power is delivered from a source resistance to a load resistance when the load resistance is equal to source resistance.  $R_s = R_L$  is the condition required for maximum power transfer.

#### APPARATUS:

S.No.	Equipment	Range	Type	Quantity
1.	Ammeter			
2.	Voltmeter			
3.	R.P.S			
4.	Bread Board			
5.	Resistors			
6.	Connecting Wires			As required

#### CIRCUIT DIAGRAM:

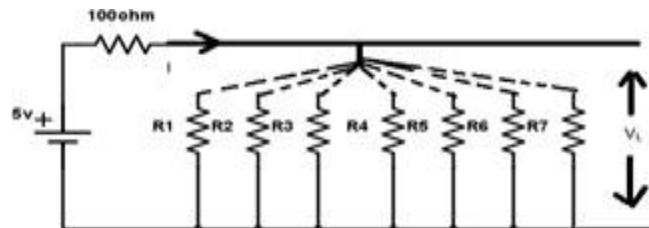


Fig – 5.4.1 Circuit Diagram

#### PROCEDURE:


1. Connect the circuit as shown in fig. 5.4.1.
2. Vary the load resistance in steps and note down voltage across the load and current flowing through the circuit.
3. Calculate power delivered to the load by using formula  $P=V*I$ .
4. Draw the graph between resistance and power (resistance on X- axis and power on Y-axis).
5. Verify the maximum power is delivered to the load when  $R_L = R_s$  for DC.

**TABULAR COLUMN:**

S. No	$R_L$	$V_L$	$I_L$	$P=VI$
1				
2				
3				
4				
5				

**MODEL GRAPH:**

Graph should be drawn in a logarithmic graph sheet

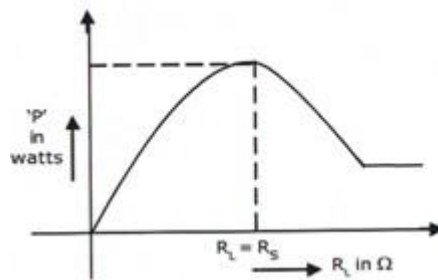

**Fig – 5.7.1 Expected graph**

**RESULT:**

**PRE LAB VIVA QUESTIONS:**

1. State maximum power transfer theorem.
2. Define voltage.
3. Define current.
4. What is the load resistance?
5. What is the source resistance?



**LAB ASSIGNMENT:**

1. Solve the theoretical value of maximum power for different circuits.
2. State and prove maximum power transfer theorem.
3. State and prove maximum power transfer theorem.

**POST LAB VIVA QUESTIONS:**

1. What are conditions for maximum power transfer theorem?

## EXPERIMENT – 6

### Verification of KVL and KCL using digital simulation

#### AIM:

To verify Kirchhoff's voltage law (KVL) and Kirchhoff's current law (KCL) using digital simulation.

#### APPARATUS:

S. No	SOFTWARE USED	DESK TOP QUANTITY
1	MATLAB	01

#### CIRCUIT DIAGRAMS:


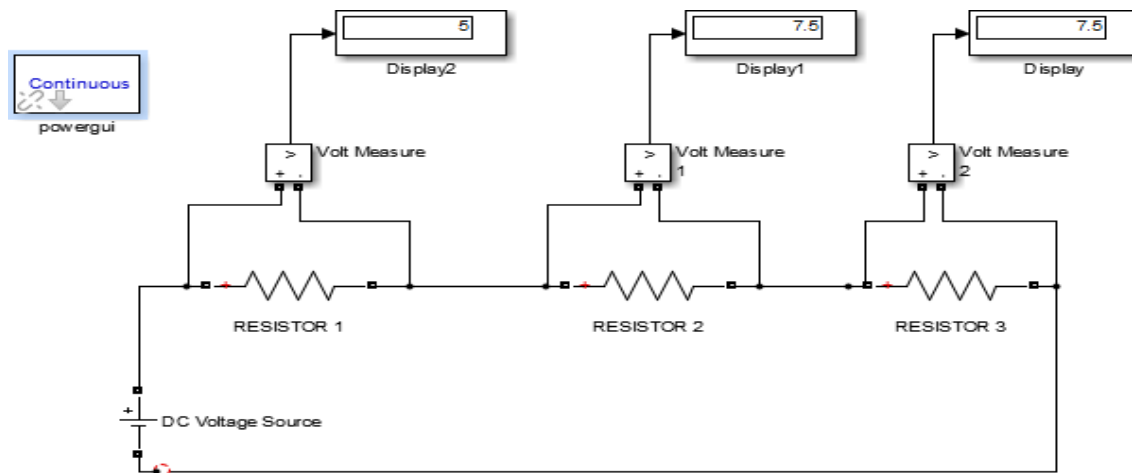


Figure – 6.3.1 Verification of KVL

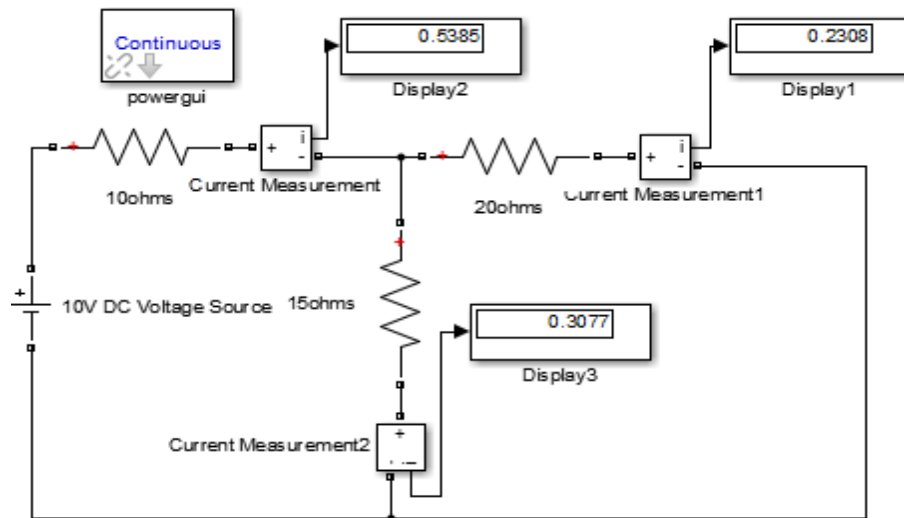

**Figure – 6.3.2 Verification of KCL**

**PROCEDURE:**

1. Make the connections as shown in the circuit diagram by using MULTISIM/MATLAB Simulink.
2. Measure the voltages and currents in each resistor.
3. Verify the KVL and KCL.

**OBSERVATIONS:**

**For KVL**

Applied Voltage	V <sub>1</sub> (volts)		V <sub>2</sub> (volts)		V <sub>3</sub> (volts)		V <sub>1</sub> +V <sub>2</sub> +V <sub>3</sub> (volts)	
	Theoretical	Practical	Theoretical	Practical	Theoretical	Practical	Theoretical	Practical
V (volts)								

**For KCL**

Applied Voltage	I (A)		I <sub>1</sub> (A)		I <sub>2</sub> (A)		I <sub>1</sub> +I <sub>2</sub> (A)	
	Theoretical	Practical	Theoretical	Practical	Theoretical	Practical	Theoretical	Practical
V (volts)								

**RESULT:**

**PRE LAB VIVA QUESTIONS:**

1. Define current.
2. Define voltage.
3. What is resistance?
4. State ohm's law.
5. What is KCL and KVL?

**POST LAB VIVA QUESTIONS:**

1. Define junction.
2. State KCL.
3. State KVL.
4. Which precautions to be taken while doing the experiment?
5. Compare hard ware results with digital simulation result.

## EXPERIMENT – 7

### VERIFICATION OF SUPERPOSITION THEOREM AND THEVENIN'S THEOREM USING DIGITAL SIMULATION

#### AIM:

To verify Superposition theorem and Thevenin's theorem using digital simulation.

#### APPARATUS:

S. No	SOFTWARE USED	DESK TOP QUANTITY
1	MATLAB	01

#### CIRCUIT DIAGRAMS:

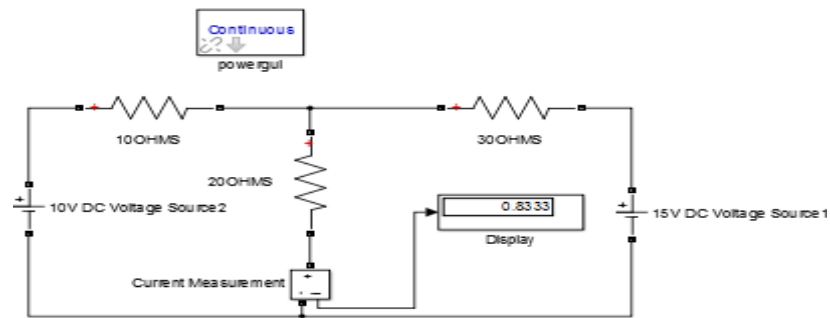


Figure – 7.3.1. Total response in 20 ohms



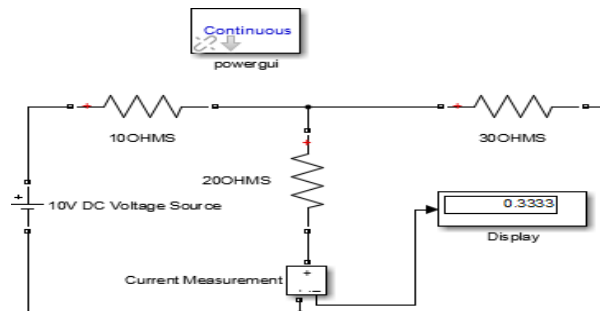



Figure – 7.3.2. Response in 20 ohms due to 10V

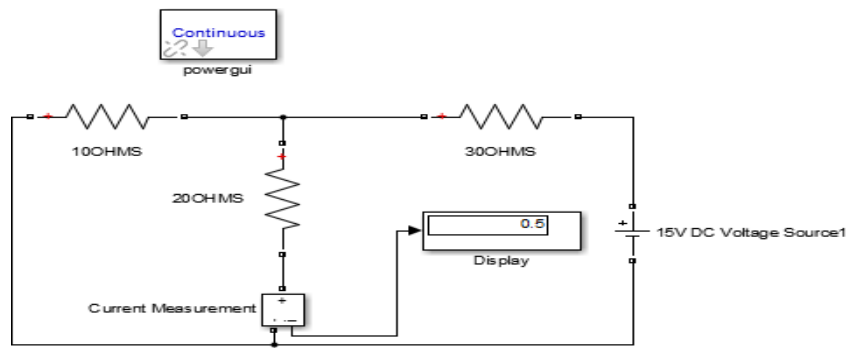


**Figure – 7.3.3. Response in 20 ohms due to 15V**

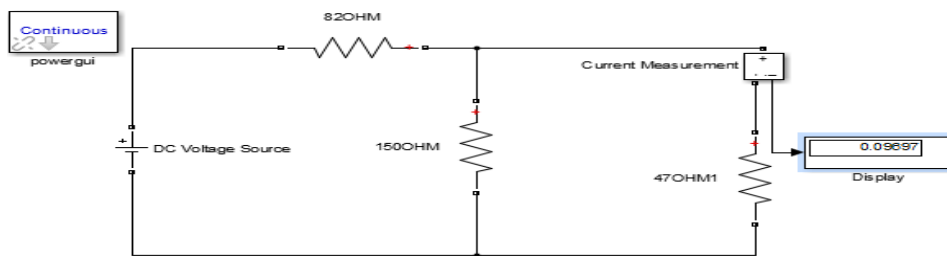

**Figure – 7.3.4. Measurement of load current**

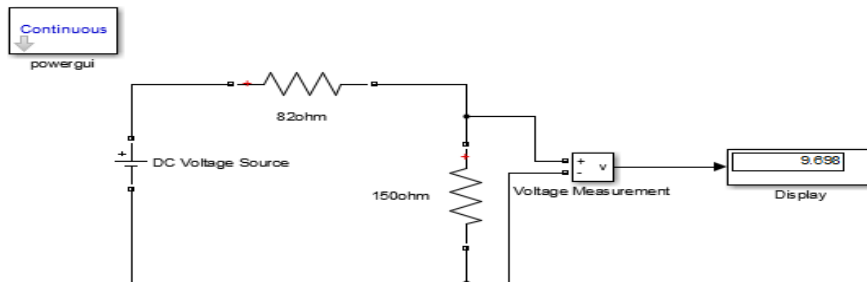

**Figure – 7.3.5. Measurement of Thevenin's voltage**

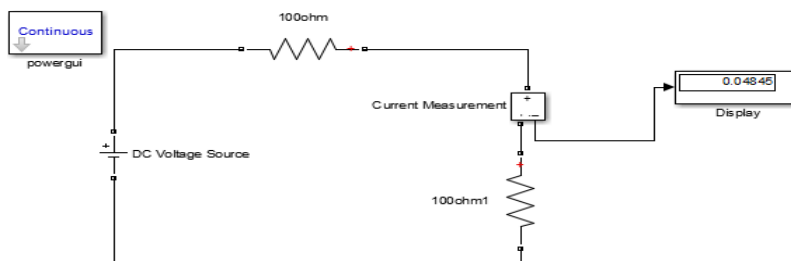

**Figure – 7.3.6. Measurement of load current using Thevenin's theorem**

**PROCEDURE:**

1. Make the connections as shown in the circuit diagram by using MULTISIM/MATLAB Simulink.
2. Measure the voltages and currents in the resistor, to be calculated.
3. Verify the superposition and Thevenin's theorem.

**RESULT:****PRE LAB VIVA QUESTIONS:**

1. Define active elements.
2. Define passive elements.
3. Ammeter is connected in series or parallel?
4. Voltmeter is connected in series or parallel?
5. Define mesh.
6. What is ohms law?
7. State superposition theorem.
8. State thevenin's theorem.
9. Define circuit.

**LAB ASSIGNMENT:**

1. Explain KVL & KCL with required circuits.
2. Explain superposition theorem calculations with examples.

**POST LAB VIVA QUESTIONS:**

1. Discuss the current division rule.
2. Discuss the voltage division rule.
3. State superposition theorem.
4. State Thevenin's theorem.

## EXPERIMENT – 8

### VERIFICATION OF NORTON'S THEOREM AND MAXIMUM POWER TRANSFER THEOREM USING DIGITAL SIMULATION

#### AIM:

To verify Norton's theorem and Maximum Power Transfer theorem using digital simulation

#### APPARATUS:

S. No	SOFTWARE USED	DESK TOP QUANTITY
1	MATLAB	01

#### CIRCUIT DIAGRAMS:

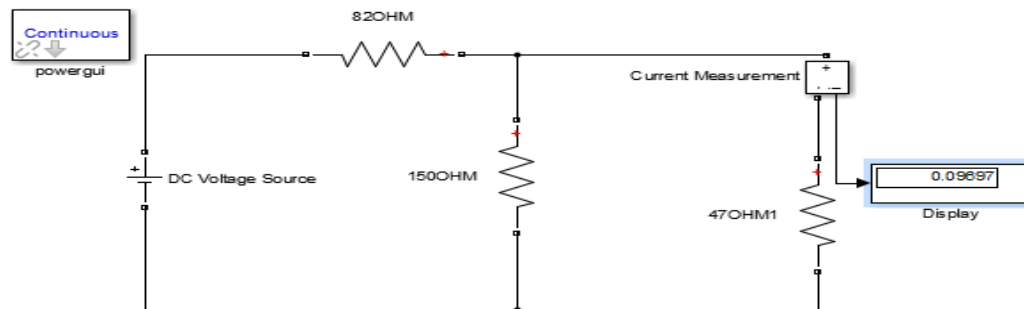


Figure – 8.3.1. Measurement of load current

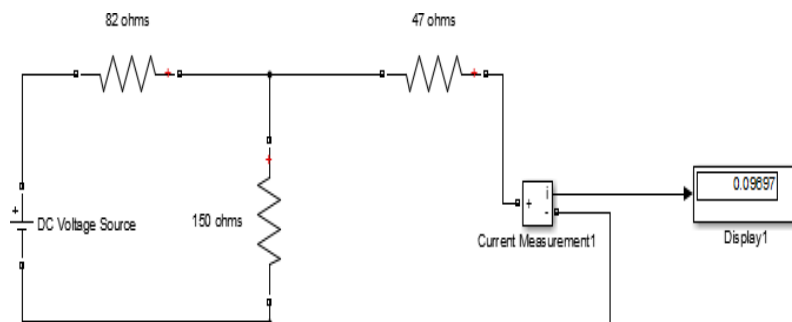
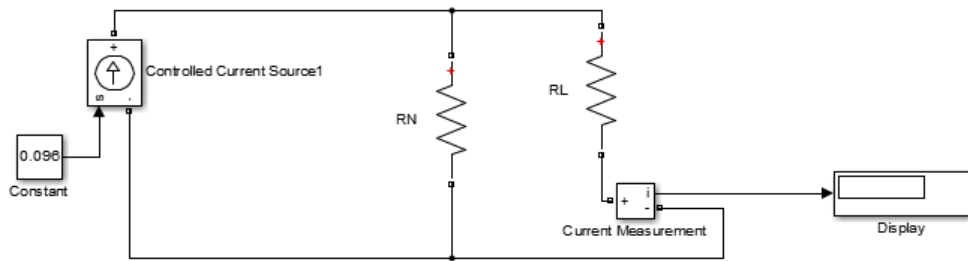
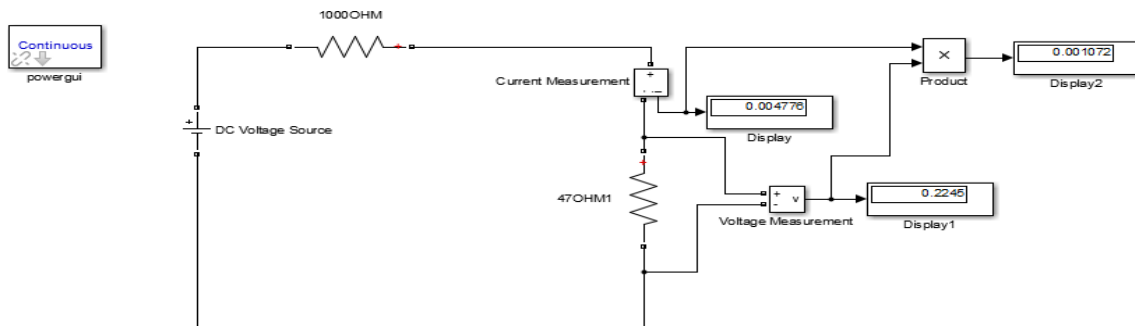


Figure – 8.3.2. Measurement of Norton's current

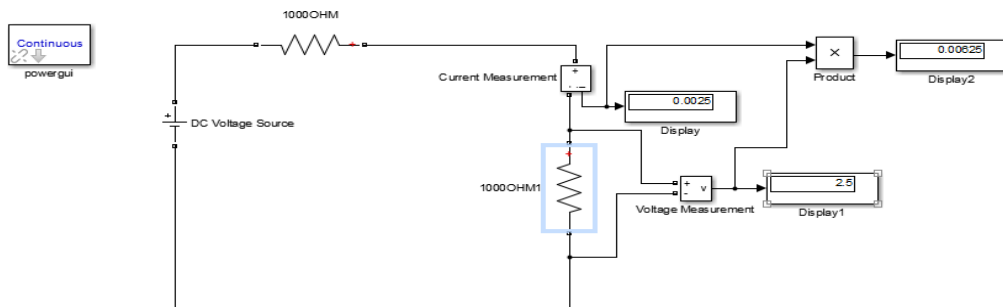





**Figure – 8.3.3. Measurement of load current using Norton’s theorem**



**Figure – 8.3.4. Verification of Maximum Power Transfer theorem**



**Figure – 8.3.5. Verification of Maximum Power Transfer theorem**

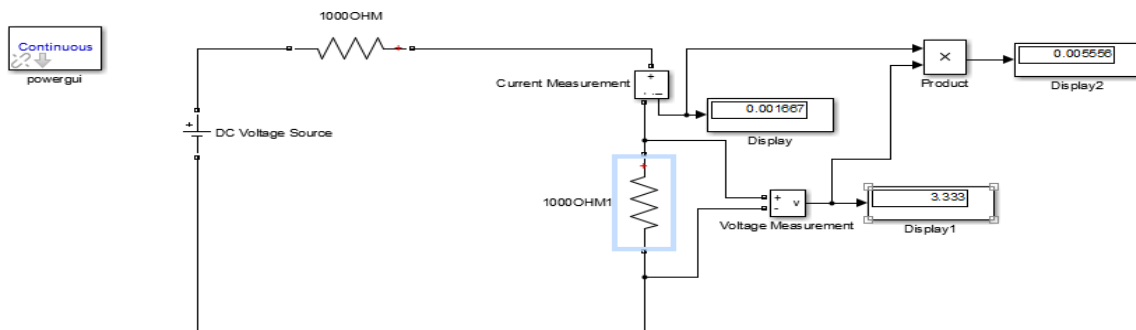

**Figure – 8.3.6. Verification of Maximum Power Transfer theorem**

### **PROCEDURE:**

1. Make the connections as shown in the circuit diagram by using MULTISIM/MATLAB Simulink.
2. Measure the voltages and currents in the resistor, to be calculated.
3. Verify the superposition and Thevenin's theorem.

### **RESULT:**

### **PRE LAB VIVA QUESTIONS**

1. Define power.
2. State the maximum power transfer theorem.
3. Ammeter is connected in series or parallel?
4. Voltmeter is connected in series or parallel?
5. Define mesh.
6. State ohm's law and write equations.
7. State Norton's theorem.

### **LAB ASSIGNMENT**

1. Determine Norton's current with an example.

### **POST LAB VIVA QUESTIONS**

1. Discuss the current division rule.
2. Discuss the voltage division rule.
3. State KCL.
4. State KVL.
5. Compare circuit and network.
6. Compare hardware result with digital simulation result.

## EXPERIMENT – 9

### VOLT AMPERE CHARACTERISTICS OF P-N JUNCTION DIODE

**AIM:**

To plot the V-I characteristics of a P-N junction diode in both forward and reverse directions, determine Cut in voltage (knee voltage), static and dynamic resistance in forward direction at forward current of 2mA & 8mA respectively and find static and dynamic resistance at 10V in reverse bias condition.

**APPARATUS:**

S.No	Device	Range/Rating	Quantity (in No.s)
1.	Semiconductor diode trainer Board Containing DC Power Supply. Diode (Silicon) Diode (Germanium) Carbon Film Resistor	(0-15) V 1N 4007 OA79 1 K $\Omega$ , 1/2 W	1 1 1 1
2.	DC Voltmeter DC Voltmeter	(0-1) V (0-20) V	1 1
3.	DC Ammeter DC Ammeter	(0-200) $\mu$ A (0-20) mA	1 1
4.	Connecting wires	5A	10

**CIRCUIT**

**DIAGRAMS:**


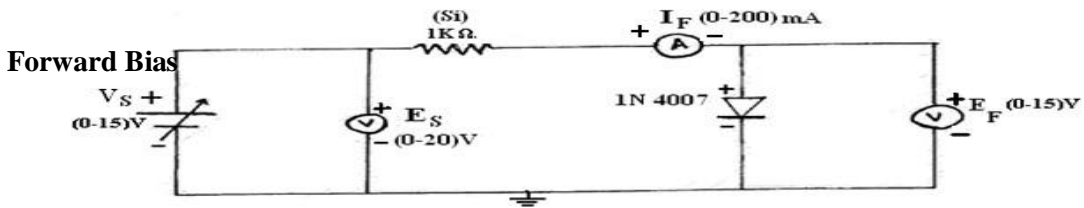


Figure – 9.3.1. Forward Bias Circuit


**Reverse Bias**

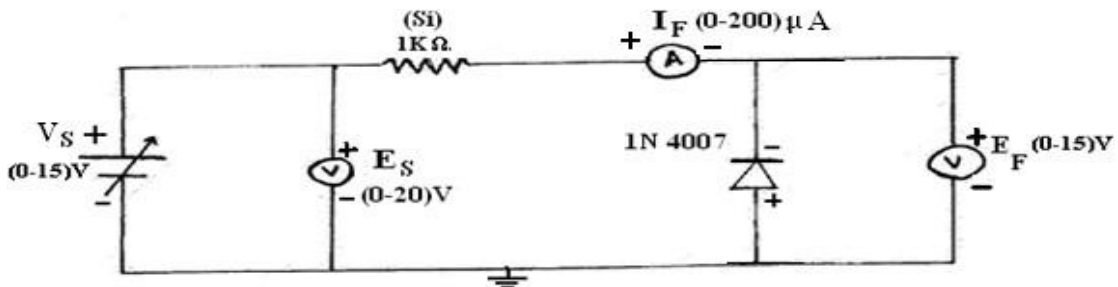

### Figure – 9.3.2. Reverse Bias Circuit

---

**EXPECTED GRAMS:**

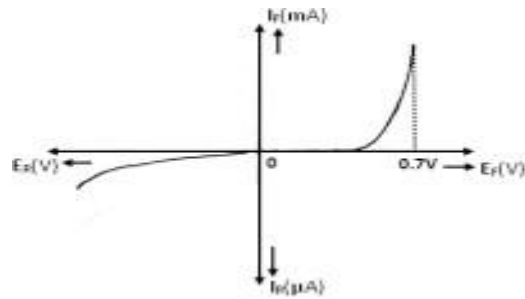

**Figure – 9.4.1.** Volt Ampere Characteristics of P-N Junction Diode

**TABULAR COLUMN:**

**FORWARD BIAS**

$E_s$ (volts)	$E_f$ (volts)	$I_f$ (mA)
0.1		
0.2		
0.3		
0.4		
0.5		
0.6		
0.7		
0.8		
0.9		
1		
2		
4		
6		
8		
10		
12		
14		

**REVERSE BIAS**

$E_s$ (volts)	$E_r$ (volts)	$I_r$ ( $\mu$ A)
0.1		
0.2		
0.3		
0.4		
0.5		
0.6		
0.7		
0.8		
0.9		
1		
2		
4		
6		
8		
10		
12		
14		

### **PRECAUTIONS:**

1. Ensure that the polarities of the power supply and the meters as per the circuit diagram.
2. Keep the input voltage knob of the regulated power supply in minimum position both when switching ON or switching OFF the power supply.
3. No loose contacts at the junctions.
4. Ensure that the ratings of the meters are as per the circuit design for precision.

### **CALCULATIONS:**

#### **Forward Bias**

Static Resistance at 8mA =  $E_f / I_f =$

Static resistance at 2mA =  $E_f / I_f =$

Dynamic resistance at 8mA =  $\Delta E_f / \Delta I_f =$

Dynamic resistance at 8mA =  $\Delta E_f / \Delta I_f =$

#### **Reverse Bias**

Static Resistance at (10V) =  $E_r / I_r =$

Dynamic resistance at (10V) =  $\Delta E_r / \Delta I_r =$

### **RESULT:**

### **PRE LAB QUESTIONS:**

1. Define depletion region of a diode.
2. What is meant by transition and space charge capacitance of a diode?
3. Is the V-I relationship of a diode Linear or Exponential?
4. Draw the ideal characteristics of P-N junction diode.
5. What is the diode equation?

### **POST LAB QUESTIONS:**

1. Define cut-in voltage of a diode and specify the values for Si and Ge diodes.
2. What are the applications of a p-n diode?
3. What is PIV?
4. Define break down voltage.
5. What is the effect of temperature on PN junction diodes?

## EXPERIMENT NO: 10

### ZENER DIODE CHARACTERISTICS AND VOLTAGE REGULATOR

#### AIM:

Plot the V-I characteristics of a Zener diode, find Zener breakdown voltage in reverse bias condition, find static and dynamic resistance in both forward and reverse bias conditions and perform Zener diode voltage regulator.

#### APPARATUS:

S.NO	DEVICES	RANGE /RATING	QUANTITY (in No.s)
1.	Zener diode trainer Board Containing a) DC Power Supply. b) Zener Diode c) Zener Diode d) Carbon Film Resistor	(0-15) V 4.7 V 6.2 V 1 K $\Omega$ , 1/2 W	1 1 1 1
2.	DC Voltmeter DC Voltmeter	(0-1) V (0-20) V	1 1
3.	a) DC Ammeter b) DC Ammeter	(0-200) $\mu$ A (0-20) mA	1 1
4.	Connecting wires	5A	10

#### CIRCUIT DIAGRAMS:

##### Forward Bias

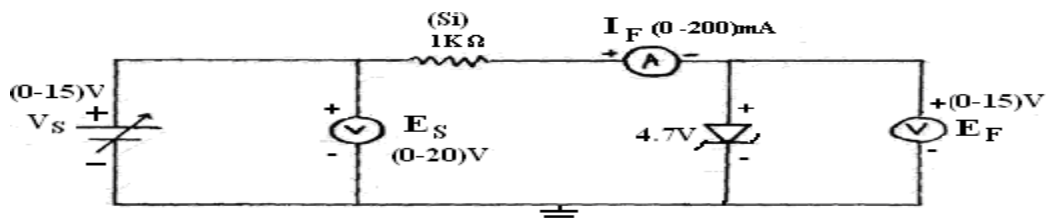


Figure – 10.4.1. Forward Bias Circuit

##### Reverse Bias

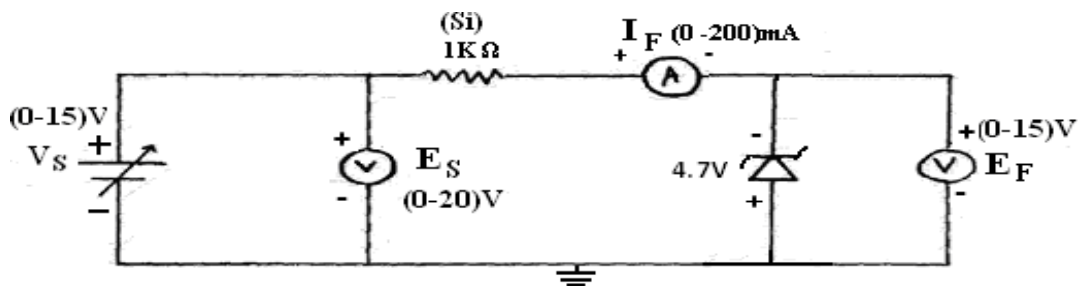


Figure – 10.4.2. Reverse Bias Circuit

## Zener Diode as Voltage Regulator

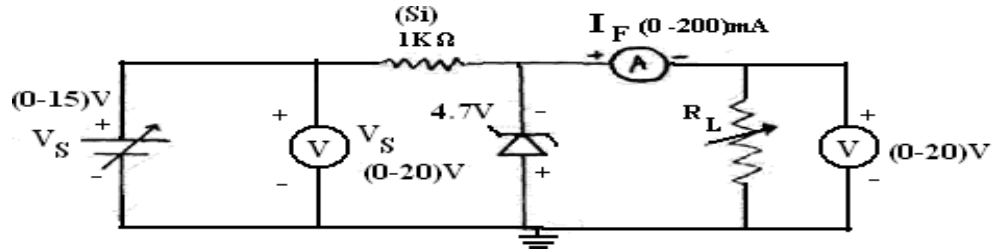


Figure – 10.4.3. Zener Diode as Voltage Regulator

### PROCEDURE:

#### Forward Bias

1. Connect the circuit as shown in figure 10.4.1.
2. Vary the supply voltage  $E_s$  in steps and note down the corresponding values of  $E_f$  and  $I_f$  as shown in the tabular column.

#### Reverse Bias

1. Connect the circuit as shown in figure 10.4.2.
2. Repeat the procedure as in forward bias and note down the corresponding values of  $E_r$  and  $I_r$  as shown in the tabular column

### EXPECTED GRAPH:

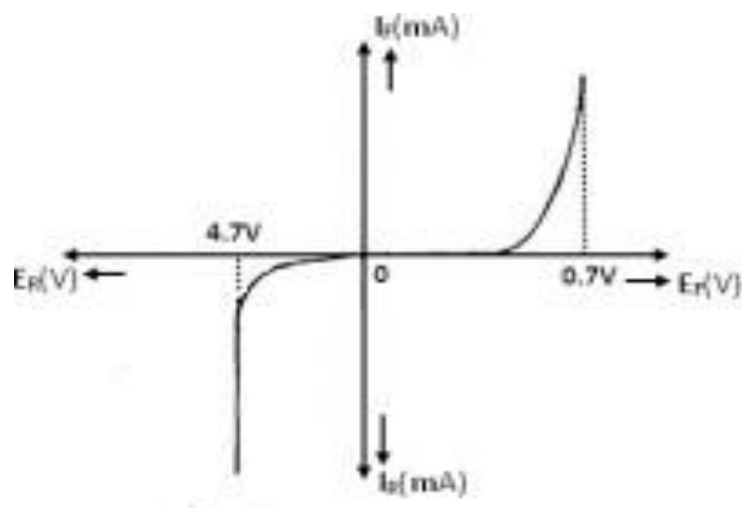


Figure – 10.4.3. Zener Diode as Voltage Regulator



**TABULAR COLUMN:**

**Forward Bias**

$E_s$ (volts)	$E_f$ (volts)	$I_f$ (mA)
0.1		
0.2		
0.3		
0.4		
0.5		
0.6		
0.7		
0.8		
0.9		
1		
2		
4		
6		
8		
10		
12		
14		

**Reverse Bias**

$E_s$ (volts)	$E_r$ (volts)	$I_r$ (mA)
0.1		
0.2		
0.3		
0.4		
0.5		
0.6		
0.7		
0.8		
0.9		
1		
2		
4		
6		
8		
10		
12		
14		

**Zener Diode as Voltage Regulator:**

$V_{in}=15V,$        $V_{NL}=\underline{\hspace{2cm}}$

$R_L=15K$

$R_L(\Omega)$	$V_{FL}$ (volts)	$I_L$ (mA)	%Regulation
100			
200			
500			
1K			
2K			
5K			
10K			
20K			

$E_s$ (volts)	$E_{FL}$ (volts)	$I_L$ (mA)
1		
2		
4		
6		
8		
10		
12		
14		

**PRECAUTIONS:**

1. Ensure that the polarities of the power supply and the meters as per the circuit diagram.
2. Keep the input voltage knob of the regulated power supply in minimum position both when switching ON or switching OFF the power supply.
3. No loose contacts at the junctions.
4. Ensure that the ratings of the meters are as per the circuit design for precision.

**CALCULATIONS:**

Forward Static resistance at 6 mA =  $E_f / I_f$

Forward Dynamic resistance at 6mA =  $\Delta E_f / \Delta I_f$

Reverse Static resistance at 6 mA =  $E_r / I_r$

Reverse Dynamic resistance at 6mA =  $\Delta E_r / \Delta I_r$

**RESULT:**

1. V-I characteristics of Zener diode are plotted and verified in both forward and reverse directions.
2. Zener breakdown voltage for 4.7V zener diode = 4.7V.
3. (i) Forward Bias:
  - a) Static resistance at 6 mA =
  - b) Dynamic resistance at 6 mA =(ii) Reverse Bias:

Static resistance at 6 mA =

Dynamic resistance at 6 mA =

**PRE LAB QUESTIONS:**

1. What type of temperature Coefficient does the zener diode have?
2. If the impurity concentration is increased, how the depletion width effected?
3. How the breakdown voltage of a particular diode can be controlled?
4. What type of temperature coefficient does the Avalanche breakdown has?

**LAB ASSIGNMENT:**

1. To plot the V-I characteristics of a Zener diode (6.1V) in both forward and reverse directions by using multisim.

**POST LAB QUESTIONS:**

1. Explain briefly about avalanche and Zener breakdowns.
2. Draw the Zener equivalent circuit.
3. Differentiate between line regulation & load regulation.
4. In which region Zener diode can be used as a regulator?

## EXPERIMENT – 11(A)

### HALF WAVE RECTIFIERS WITH / WITHOUT FILTER

#### AIM:

Examine the input and output waveforms of a half wave rectifier without and with filters. Calculate the ripple factor with load resistance of  $500\Omega$ ,  $1\text{ K}\Omega$  and  $10\text{ K}\Omega$  respectively. Calculate ripple factor with a filter capacitor of  $100\mu\text{F}$  and the load of  $1\text{ K}\Omega$ ,  $2\text{ K}\Omega$  and  $10\text{ K}\Omega$  respectively.

#### APPARATUS:

S.No	Device	Range/Rating	Quantity in No.
1	Rectifier and Filter trainer Board Containing a) AC Supply. b) Silicon Diodes c) Capacitor	(9-0-9) V 1N 4007 $0.47\mu\text{F}$	1 7 1
2	a) DC Voltmeter b) AC Voltmeter	(0-20) V (0-20) V	1 1
3	DC Ammeter	(0-50) mA	1
4	Cathode Ray Oscilloscope	(0-20) MHz	1
5	Decade Resistance Box	$10\Omega$ - $100\text{ K}\Omega$	1
6	Connecting wires	5A	12

#### CIRCUIT DIAGRAMS:


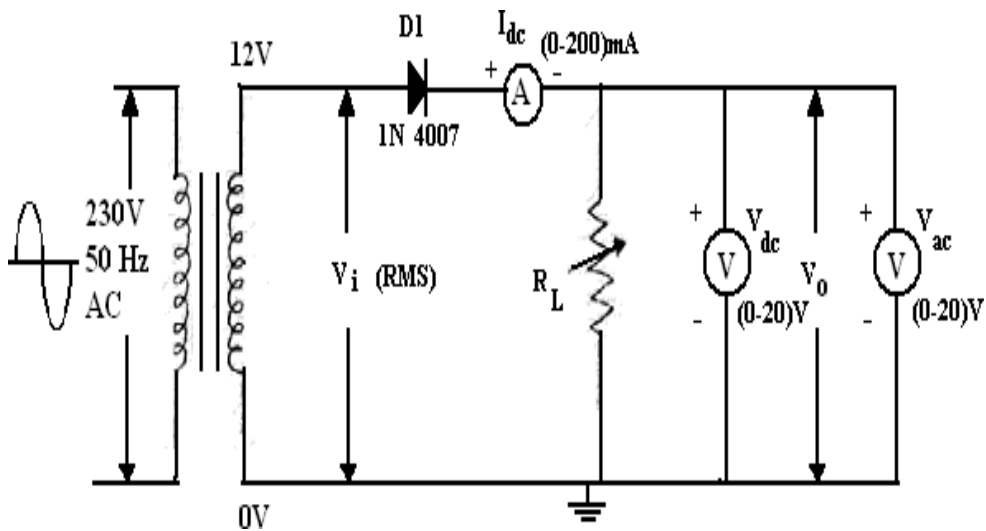


Figure – 11.4.1. Half Wave Rectifier without Filter

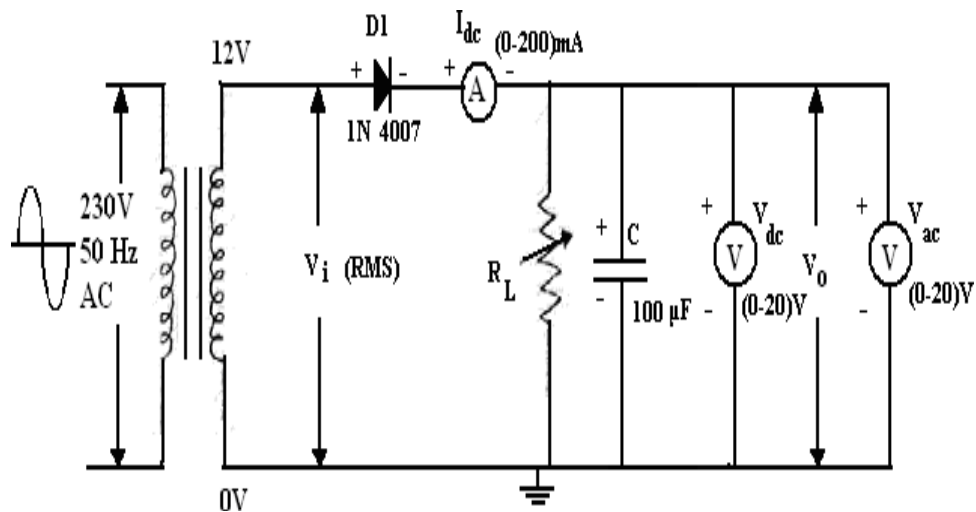

**Figure – 11.4.2. Half Wave Rectifier with Filter**

## PROCEDURE:


### Half Wave Rectifier without filter

1. Connect the circuit as shown in figure 11.4.1.
2. Adjust the load resistance,  $R_L$  to  $500\Omega$ , and note down the readings of input and output voltages through oscilloscope.
3. Note the readings of dc current, dc voltage and ac voltage.
4. Now, change the resistance the load resistance,  $R_L$  to  $1\text{ K}\Omega$  and repeat the procedure as above. Also repeat for  $10\text{ K}\Omega$ .
5. Readings are tabulated as per the tabular column.

### Half Wave Rectifier with filter

1. Connect the circuit as shown in figure 11.4.2 and repeat the procedure as for half Wave rectifier without filter.

**EXPECTED GRAPHS:**

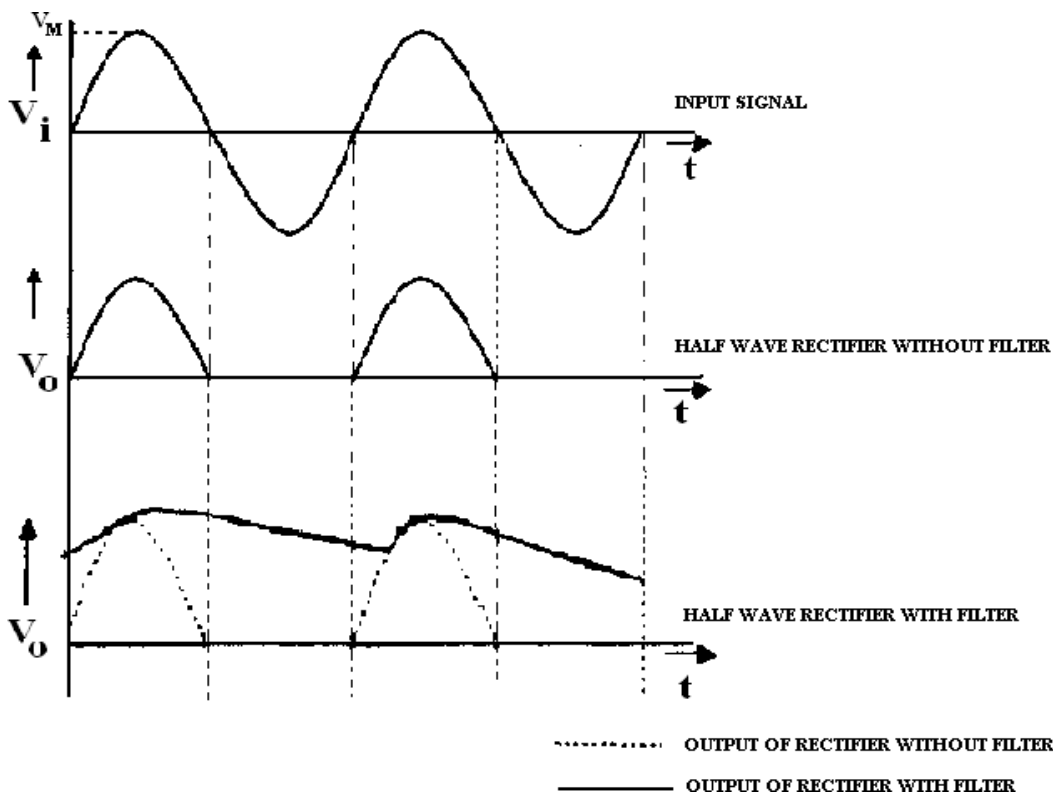

**PRECAUTIONS:**

1. No loose contacts at the junctions.
2. Meters of correct ranges must be used for precision

**TABULAR COLUMNS:**

**Half Wave Rectifier without Filter**

S.No	Load Resistance (RL)	Input Voltage Peak (Vm)	Output Voltage Peak (Vo)	Average dc current (Idc)	Average Dc voltage (Vdc)	RMS Voltage (Vac)	Ripple Factor $\gamma = \frac{V_{ac}}{V_{dc}}$
1.	500Ω						
2.	1KΩ						
3.	10KΩ						

**Half Wave Rectifier with Filter C=10μF**

S.No	Load Resistance (R <sub>L</sub> )	Input Voltage Peak (V <sub>m</sub> )	Output Voltage Peak (V <sub>o</sub> )	Average dc current (I <sub>dc</sub> )	Average Dc voltage (V <sub>dc</sub> )	RMS Voltage (V <sub>ac</sub> )	Ripple Factor $\gamma = \frac{V_{ac}}{V_{dc}}$
1.	1KΩ						
2.	2KΩ						
3.	10KΩ						

**PRE LAB QUESTIONS:**

1. What is a rectifier?
2. How Diode acts as a rectifier?
3. What is the significance of PIV? What is the condition imposed on PIV?
4. Define regulation.
5. Define time constant.

**LAB ASSIGNMENT:**

1. Plot the wave forms of Half wave rectifier with R=5000 ohms, C = 680μF.

**POST LAB QUESTIONS:**

1. Draw the o/p wave form without filter.
2. Draw the o/p wave form with filter.
3. What is meant by ripple factor? For a good filter whether ripple factor should be high or low?
4. What happens to the o/p wave form if we increase the capacitor value?
5. What happens if we increase the capacitor value?

## RESULT:

1. Input and Output waveforms of a half-wave with /without filter are observed and plotted.
2. For Half-wave rectifier without filter-  
 $\gamma$ , Ripple factor at  $500\Omega$ =

1K $\Omega$ =

10 K $\Omega$ =

3. For Half-wave rectifier with filter:-  
 $\gamma$ , Ripple factor at 1K $\Omega$ , 100 $\mu$ F =

2K $\Omega$ , 100 $\mu$ F =

10 K $\Omega$ , 100 $\mu$ F =



## EXPERIMENT – 11(B)

### FULLWAVE RECTIFIERS WITH/WITHOUT FILTER

#### AIM:

Examine the input and output waveforms of a full wave (center tapped) rectifier without and with filters.

Calculate the ripple factor with load resistance of  $500\Omega$ ,  $1\text{ K}\Omega$  and  $10\text{ K}\Omega$  respectively.

Calculate ripple factor with a filter capacitor of  $100\mu\text{F}$  and the load of  $1\text{ K}\Omega$ ,  $2\text{ K}\Omega$  and  $10\text{ K}\Omega$  respectively.

#### APPARATUS:

S.No	Device	Range /Rating	Quantity (in No.s)
1	Rectifier and Filter trainer Board Containing a) AC Supply. b) Silicon Diodes c) Capacitor	(9-0-9) V 1N 4007 $0.47\mu\text{F}$	1 7 1
2	a) DC Voltmeter b) AC Voltmeter	(0-20) V (0-20) V	1 1
3	DC Ammeter	(0-50) mA	1
4	Cathode Ray Oscilloscope	(0-20) MHz	1
5	Decade Resistance Box	$10\Omega$ - $100\text{ K}\Omega$	1
6	Electrolytic Capacitor	$100\mu\text{F}$	1
7	Connecting wires	5A	12

#### CIRCUIT DIAGRAMS:


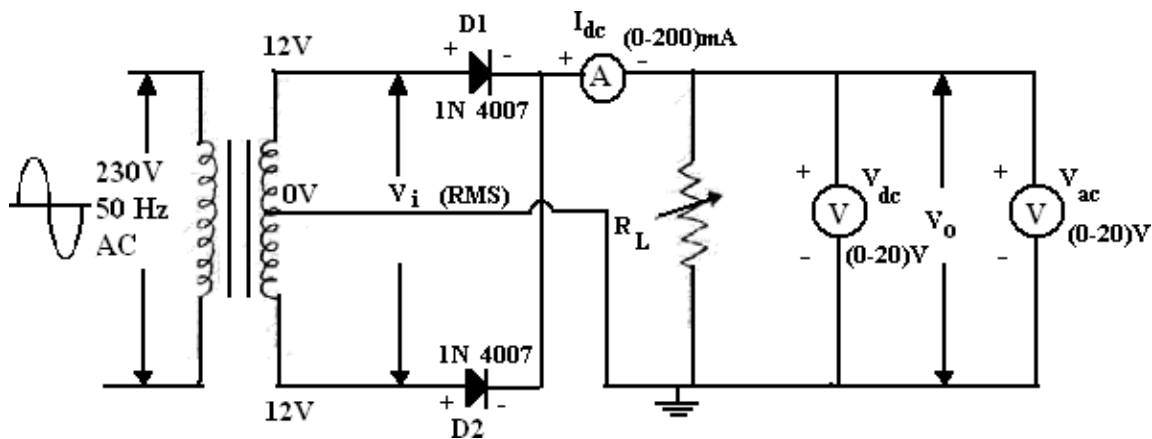


Figure – 11.15.1. Full Wave Rectifier (Center-tap) Without Filter

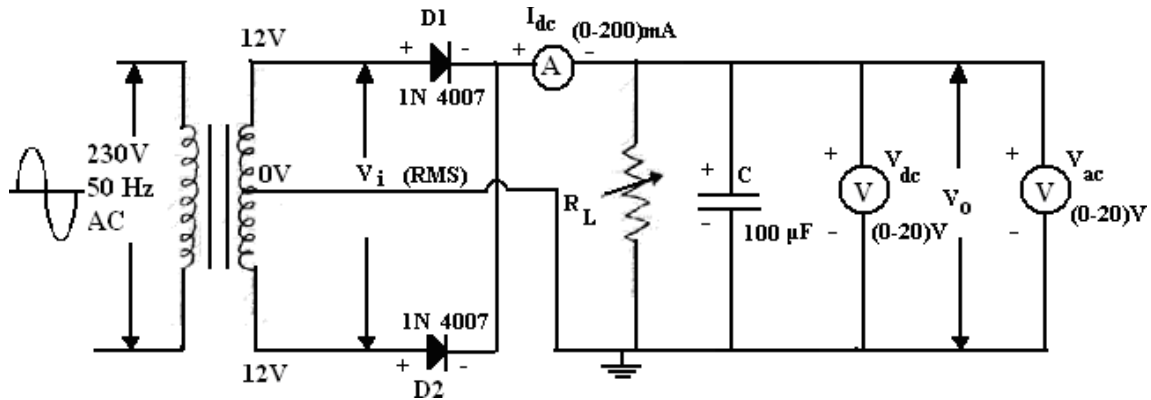

**Figure – 11.15.2. Full Wave Rectifier (Center-tap) With Filter**

### PROCEDURE:


#### Full-wave Rectifier without filter

1. Connect the circuit as shown in the figure (a).
2. Adjust the load resistance  $R_L$  to  $500\Omega$  and connect a capacitor of  $100\mu F$  value in parallel with the load and note the readings of input and output voltages through Oscilloscope.
3. Note the readings of DC current, DC voltage and AC voltage.
4. Now change the load resistance  $R_L$  to  $2000\Omega$  and repeat the procedure as the above.
5. Readings are tabulate as per the tabular column.

#### Full-wave Rectifier with filter

1. Connect the circuit as shown in the figure (b).
2. Adjust the load resistance  $R_L$  to  $1K\Omega$  and connect a capacitor of  $100\mu F$  values in parallel with the load and note the readings of input and output voltages through Oscilloscope.
3. Note the readings of DC current, DC voltage and AC voltage.
4. Now change the load resistance  $R_L$  to  $2K\Omega$  and repeat the procedure as the above. Also repeat for  $10K$ ,  $100\mu F$  values
5. Readings are tabulate as per the tabular column.

**EXPECTED GRAPHS:**

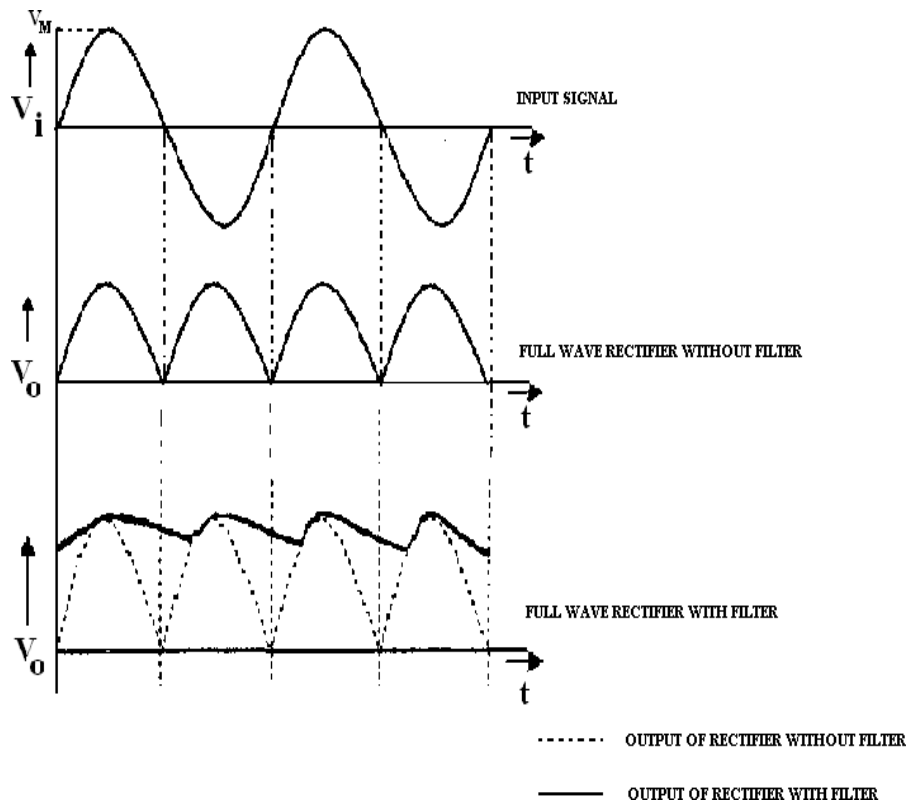

**PRECAUTIONS:**

1. No loose contacts at the junctions.
2. Meters of correct range must be used for precision.

**TABULAR COLUMNS:**

**Full wave Rectifier (Center-tap) Without Filter**

S.No	Load Resistance ( $R_L$ )	Input Voltage Peak ( $V_m$ )	Output Voltage Peak ( $V_o$ )	Average dc current ( $I_{dc}$ )	Average Dc voltage ( $V_{dc}$ )	RMS Voltage ( $V_{ac}$ )	Ripple Factor $\gamma = \frac{V_{ac}}{V_{dc}}$
1	500 $\Omega$						
2	1K $\Omega$						
3	10K $\Omega$						

**Full wave Rectifier (Center-tap) With Filter      C = ---  $\mu$ F**

S.No	Load Resistance ( $R_L$ )	Input Voltage Peak ( $V_m$ )	Output Voltage Peak ( $V_o$ )	Average dc current ( $I_{dc}$ )	Average Dc voltage ( $V_{dc}$ )	RMS Voltage ( $V_{ac}$ )	Ripple Factor $\gamma = \frac{V_{ac}}{V_{dc}}$
1	500 $\Omega$						
2	1K $\Omega$						
3	10K						

**PRE LAB QUESTIONS:**

1. What is a full wave rectifier?
2. How Diode acts as a rectifier?
3. What is the significance of PIV requirement of Diode in full-wave rectifier?
4. Compare capacitor filter with an inductor filter.
5. What is the theoretical maximum value of ripple factor for a full wave rectifier?

**LAB ASSIGNMENT:**

Plot the wave forms of full wave rectifier with R=500 ohms, C = 470 $\mu$ F.

**POST LAB QUESTIONS:**

1. Draw the o/p wave form without filter? Draw the O/P? What is wave form with Filter.
2. Define ripple factor. For a good filter whether ripple factor should be high or low? What happens to the ripple factor if we insert the filter?
3. Define regulation. Why regulation is poor in the case of inductor filter?
4. Define time constant.
5. What happens to the o/p wave form if we increase the capacitor value? What happens if we increase the capacitor value?

**RESULT:**

1. Input and Output waveforms of a full-wave (center tapped) and bridge rectifier with /without filters are observed and plotted.
2. For Full-wave rectifier(center tapped) without filter-
  - i.  $\gamma$ , Ripple factor at  $500\Omega$ ,  $100\mu\text{F}$  =
    - a.  $2\text{K}\Omega$ ,  $100\mu\text{F}$  =
3. For full-wave rectifier (Center tapped) with filter-
  - i.  $\gamma$ , Ripple factor at  $500\Omega$ ,  $100\mu\text{F}$  =
    - a.  $2\text{K}\Omega$ ,  $100\mu\text{F}$  =

## EXPERIMENT – 12

### TRANSISTOR CB CHARACTERISTICS

#### AIM:


Plot the input and output characteristics of a transistor connected in Common Base configuration.

Calculate the input resistance  $R_i$  at  $I_c = 12 \text{ mA}$ , output resistance  $R_o$  at  $V_{CB} = 8 \text{ V}$  and current gain at  $V_{CB} = 6 \text{ V}$ .

#### APPARATUS:

S.No.	Device	Range /Rating	Quantity (in No.s)
1.	Transistor CB trainer Board Containing a) DC Power Supply. b) PNP Transistor c) Carbon Film Resistor	(0-12) V CK100 470 $\Omega$ , 1/2 W	2 1 2
2.	a) DC Voltmeter b) DC Voltmeter	(0-1) V (0-20) V	1 1
3.	DC Ammeter	(0-50) mA	2
4.	Connecting wires	5A	12

#### CIRCUIT DIAGRAM:

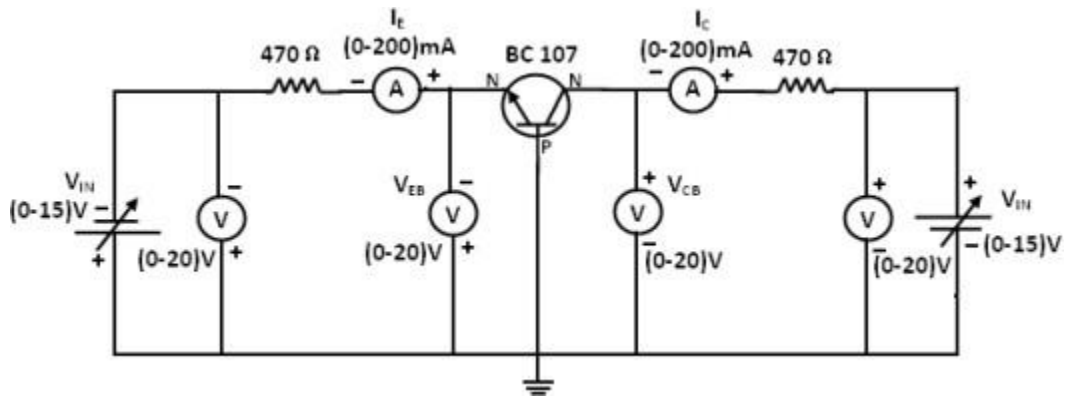

**Figure – 12.3.1. Transistor CB Characteristics**

#### PROCEDURE:

##### Input

##### Characteristics:

1. Connect the transistor as shown in figure 12.3.1
2. Keep the  $V_{CB}$  constant at 4V and 8V. Vary the  $V_{EB}$  in steps and note corresponding  $I_E$  values as per tabular form.




**Output Characteristics:**

1. Keep the  $I_E$  constant at 4mA and 8mA. Vary the  $V_{CB}$  in steps and note Corresponding  $I_C$  values.
2. Readings are tabulated as shown in tabular column


**EXPECTED GRAPHS:**

**Input Characteristics:**

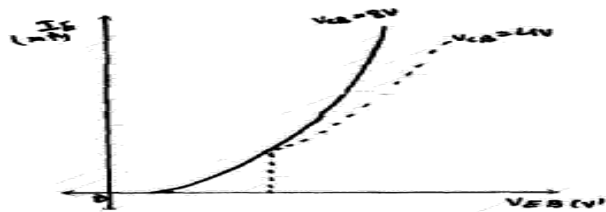

**Figure – 12.5.1. Transistor CB Input Characteristics**

**Output characteristics:**

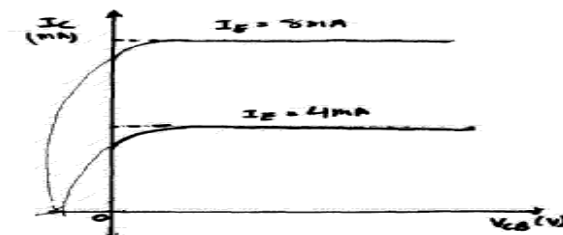

**Figure – 12.3.1. Transistor CB output Characteristics**



**PRECAUTIONS:**

1. Keep the knobs of supply voltages  $V_{EB}$  &  $V_{CB}$  at minimum positions when switching ON or switching OFF the power supply.
2. No loose contacts at the junctions.
3. Do not overload the meters above its rated ranges.

**TABULAR COLUMN:**

**Input Characteristics**

$V_{CB} = -4V$		$V_{CB} = -8V$	
$V_{EB}$ (Volts)	$I_E$ (mA)	$V_{EB}$ (Volts)	$I_E$ (mA)

**Output Characteristics**

$I_E = 8mA$		$I_E = 4mA$	
$V_{CB}$ (Volts)	$I_C$ (mA)	$V_{CB}$ (Volts)	$I_C$ (mA)

**CALCULATIONS:**

- Input Resistance ( $I_E = 12 \text{ mA}$ ) =  $\Delta V_{EB} / \Delta I_E =$   
At  $V_{EB} = 4V$
- Input Resistance ( $I_E = 12 \text{ mA}$ ) =  $\Delta V_{EB} / \Delta I_E =$   
At  $V_{EB} = 8V$
- Output resistance ( $I_E = 8mA$ ) =  $\Delta V_{CB} / \Delta I_C =$   
At  $V_{CB} = -8V$ .
- Output resistance ( $I_E = 4mA$ ) =  $\Delta V_{CB} / \Delta I_C =$   
At  $V_{CB} = -8V$ .
- Current Amplification Factor ' $\alpha$ ' =  $\Delta I_C / \Delta I_E =$

### PRE LAB QUESTIONS:

1. What is the range of  $\alpha$  for the transistor?
2. Draw the input and output characteristics of the transistor in CB configuration?
3. Identify various regions in output characteristics?
4. What is the relation between  $\alpha$  and  $\beta$ ?

### LAB ASSIGNMENT:

Plot the I/O characteristics of CB configuration for  $V_{cc} = 12V$ ,  $V_{EE} = 6V$ ,  $R_E = 100K$  ohms,  $R_c = 1K$  ohms,  $\alpha = 0.98$ ,  $V_{be} = 0.7V$ .

### POST LAB QUESTIONS:

1. Discuss the applications of CB configuration?
2. What are the input and output impedances of CB configuration?
3. Define  $\alpha$  (alpha)?
4. What is EARLY effect?
5. Discuss the power gain of CB configuration

### RESULT:

1. Input and output curves are plotted.
2.  $R_i$  Input Resistance:
  - (i)  $V_{EB} = 4V$  and  $I_E = 12$  mA,  $R_i =$
  - (ii)  $V_{EB} = 8V$  and  $I_E = 12$  mA,  $R_i =$
3.  $R_o$  Output Resistance:
  - (i)  $V_{CB} = 8V$  and  $I_E = 8$  mA,  $R_o =$
  - (ii)  $V_{CB} = 8V$  and  $I_E = 4$  mA,  $R_o =$
4. Current Amplification factor  
' $\alpha$ ' =  
  
(at  $V_{CB} = 6V$ )

## EXPERIMENT NO: 13

### TRANSISTOR CE CHARACTERISTICS

#### AIM:

Plot the input and output characteristics of a transistor connected in Common Emitter configuration. Calculate the input resistance  $R_i$  at  $I_B = 20 \mu\text{A}$ , output resistance  $R_O$  at  $V_{CE} = 10\text{V}$  and current gain at  $V_{CE} = 10\text{V}$ .

#### APPARATUS:

S. No	Devices	Range / Rating	Quantity (in No's)
1.	Transistor CE trainer Board Containing		
	a) DC Power Supply.	(0-12) V BC	2
	b) NPN Transistor	107	1
	c) Carbon Film Resistor	$470\Omega$ , 1/2 W $100\text{K}\Omega$ , 1/2 W	1 1
2.	a) DC Voltmeter	(0-1) V	1
	b) DC Voltmeter	(0-20) V	1
3.	DC Ammeter	(0-50) mA (0-200) $\mu\text{A}$	1 1
4.	Connecting wires	5A	12

#### CIRCUIT DIAGRAM:

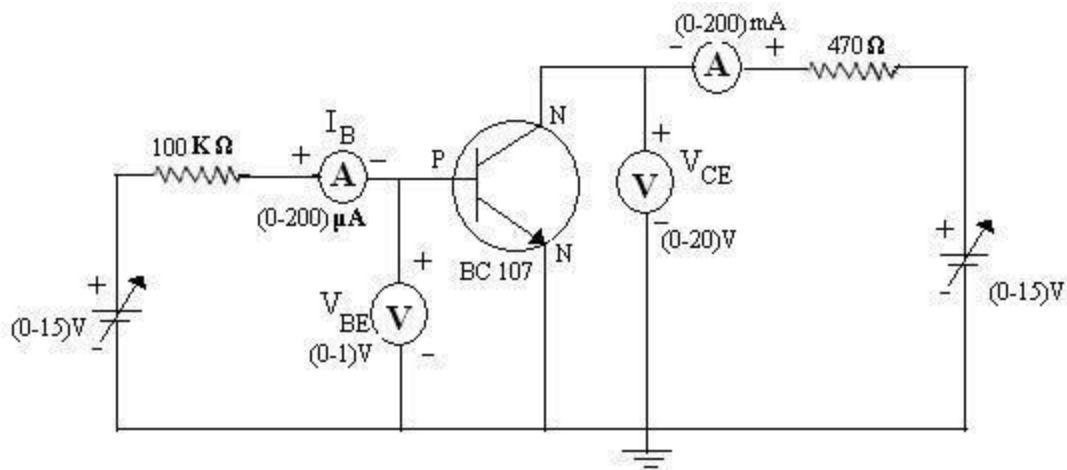


Figure – 13.3.1. Transistor CE Characteristics

## PROCEDURE:

### Input

#### Characteristics:

1. Connect the transistor as shown in figure 13.3.1
2. Keep the  $V_{CE}$  constant at 2V and 6V.
3. Vary the  $I_B$  in steps and note down the corresponding  $V_{EB}$  values as per tabular column.

#### Output Characteristics:

1. Keep the  $I_B$  constant at 20  $\mu\text{A}$  and 40  $\mu\text{A}$ .
2. Vary the  $V_{CE}$  in steps and note corresponding  $I_C$  values.
3. Readings are tabulated as shown in tabular column.

## EXPECTED GRAPHS:

### Input Characteristics:

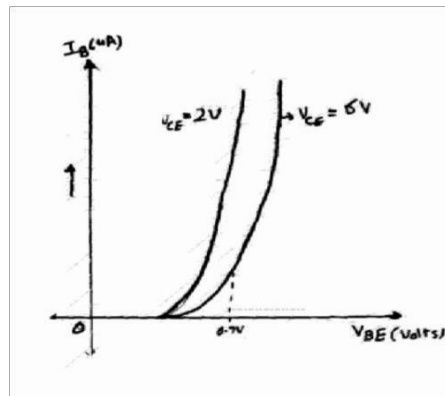


Figure – 13.5.1. Transistor CE Input characteristics

### Output characteristics:

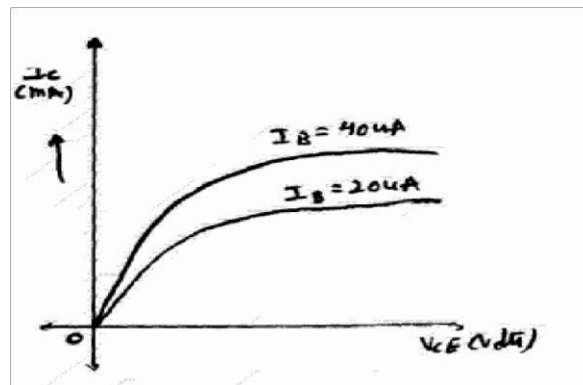


Figure – 13.5.2. Transistor CE Output Characteristics

**PRECAUTIONS:**

1. Keep the knobs of supply voltages  $V_{BE}$  &  $V_{CE}$  at minimum positions when switching ON or switching OFF the power supply.
2. No loose contacts at the junctions.
3. Do not overload the meters above its rated ranges.

**TABULAR COLUMNS: Input****Characteristics:**

$V_{CB} = 2V$		$V_{CB} = 6V$	
$V_{BE}$ (Volts)	$I_B$ ( $\mu A$ )	$V_{BE}$ (Volts)	$I_B$ ( $\mu A$ )
	0		0
	0.2		0.2
	0.4		0.4
	0.6		0.6
	0.8		0.8
	1		1
	2		2
	4		4
	6		6
	8		8
	10		10
	20		20
	30		30
	40		40
	50		50
	60		60

**Output characteristics:**

$I_B = 20\mu A$	
$V_{CE}$ (Volts)	$I_C$ (mA)
0	
0.5	
1	
2	
3	
4	
5	
6	
7	
8	
9	
10	
11	
12	

$I_B = 40\mu A$	
$V_{CE}$ (Volts)	$I_C$ (mA)
0	
0.5	
1	
2	
3	
4	
5	
6	
7	
8	
9	
10	
11	
12	

**CALCULATIONS:**

Input Resistance ( $I_B=20\mu A$ ) =  $\Delta V_{BE}/\Delta I_B$  = At  $V_{CE}$   
= 2V

Input Resistance ( $I_B =20\mu A$ ) =  $\Delta V_{BE}/\Delta I_B$  = At  
 $V_{CE}= 6V$

Output resistance ( $V_{CE}=10V$ ) =  $\Delta V_{CE}/\Delta I_C$  = At  
 $I_B=20\mu A$

Output resistance ( $V_{CE}=10V$ ) =  $\Delta V_{CE}/\Delta I_C$  = At  
 $I_B=20\mu A$

Current Amplification Factor ' $\beta$ ' =  $\Delta I_C/\Delta I_B$  =

### RESULT:

1. Input and Output curves are plotted.
2.  $R_i$ , Input Resistance:
  - a.  $V_{CE} = 2V$  and  $I_B = 20 \mu A$ ,  $R_i =$
  - b.  $V_{CE} = 6V$  and  $I_B = 20 \mu A$ ,  $R_i =$
3.  $R_o$ , Output Resistance:
  - a.  $V_{CE} = 10V$  and  $I_B = 20 \mu A$ ,  $R_o =$
  - b.  $V_{CE} = 10V$  and  $I_B = 40 \mu A$ ,  $R_o =$
4. Current Amplification factor ' $\beta$ ' =  
(at  $V_{CE} = 10V$ )

### PRE LAB QUESTIONS:

1. What is the range of ' $\beta$ ' for the transistor?
2. What are the input and output impedances of CE configuration?
3. Identify various regions in the output characteristics?
4. What is the relation between ' $\alpha$ ' and ' $\beta$ '?

### POST LAB QUESTIONS:

1. Define current gain in CE configuration.
2. Why CE configuration is preferred for amplification?
3. What is the phase relation between input and output?
4. Draw diagram of CE configuration for PNP transistor.
5. What is the power gain of CE configuration?
6. What are the applications of CE configuration?