



INSTITUTE OF AERONAUTICAL ENGINEERING (AUTONOMOUS)

Dundigal, Hyderabad -500 043

CIVIL ENGINEERING TUTORIAL QUESTION BANK

Course Name	:	ELECTRICAL AND ELECTRONICS ENGINEERING
Course Code	:	A30203
Class	:	II B. Tech I Semester
Branch	:	Civil Engineering
Year	:	2016 – 2017
Course Faculty	:	Mr. A Sathishkumar, Assistant Professor Mr. M Diva kumar, Assistant Professor




OBJECTIVES







Electrical And Electronics Engineering course is belongs to basic knowledge of high voltage and low voltage Circuits. This course introduces the basic concepts of circuit analysis which is the Foundation for all subjects of the Electrical Engineering discipline. The course deals with the basic analysis of single phase circuits, DC machines, AC machines and principles of indicating instruments. It also emphasis on basics of electronics, semiconductors devices and their characteristics and operational features


S. No	Question	Blooms Taxonomy Level	Course Outcome
UNIT-I			
Electrical circuits and Instruments			
SHORT ANSWER TYPE QUESTIONS			
1	State Ohm's law	Remember	1
2	State Kirchhoff's voltage law	Understand	1
3	Give two applications of both series and parallel combination	Remember	1
4	Write short notes on resistor with relevant expression	Remember	2
5	Given that the resistors Ra, Rb and Rc are connected electrically in star. Write the equations for resistors in equivalent delta	Understand	2
6	What are the types of measuring instruments	Remember	3
7	Basic definitions of current and voltage, power	Understand	1
8	Write short notes on spring control mechanism	Remember	1
9	What is mean by instrument? Different types of instrument	Remember	1
10	Write different types of torques.	Remember	2
11	State Kirchhoff's Current law	Understand	2
12	Write short notes on capacitor with relevant expression	Remember	1
13	Write short notes on inductor with relevant expression	Remember	1
14	Define controlling torque	Remember	3
15	Define damping torque	Understand	3
LONG ANSWER QUESTIONS			
1	Derive star-delta conversion equations?	Apply	1
2	Derive delta-star conversion equations?	Understand	1

S. No	Question	Blooms Taxonomy Level	Course Outcome
3	Describe different types of elements with examples	Creating	1
4	Describe about series and parallel resistive networks	Apply	1
5	Explain working principle of permanent magnet moving coil instrument	Apply	1
6	Describe working principle of moving iron attraction type instrument	Understand	1
7	Describe working principle of moving iron repulsion type instrument	Apply	3
8	Discuss working of different types of torques produced in indicating instruments	Understand	2
9	Explain the classification of basic elements	Apply	1
10	Describe about series and parallel inductance networks	Understand	1
11	Describe about series and parallel capacitance networks	Understand	3
12	Explain spring control in measuring instruments	Understand	4
13	Explain gravity control in measuring instruments	Apply	1
14	Describe eddy current damping in measuring instruments	Understand	3
15	Describe air friction damping in measuring instruments	Apply	1

ANALYTICAL QUESTIONS

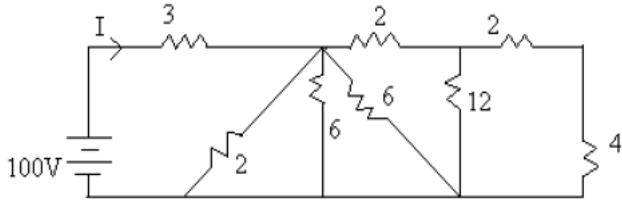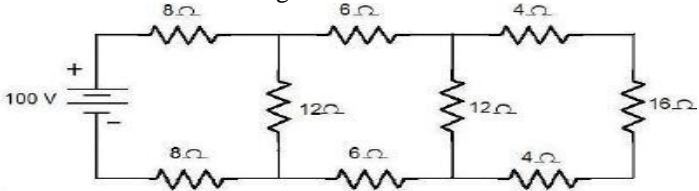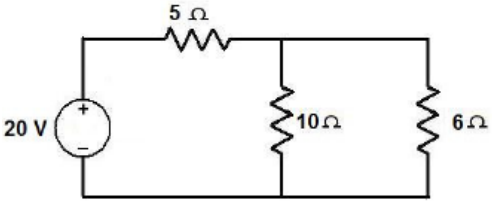1	A voltage of 200 V is applied to a tapped resistor of 500Ω. Find the resistance between the tapping points connected to a load, needing 0.1A at 25 V. Also calculate the Total power consumed	Apply	1
2	An inductor having inductance of 2mH is charged to a current of 1A. Calculate the stored energy in joules	Understand	1
3	If 3 capacitors of values 2mF, 4mF, 5mF are connected in parallel. Calculate the effective capacitance.	Apply	3
4	Determine the current I in the circuit shown in figure. All resistances are in ohms. 	Understand	2
5	Calculate a) the equivalent resistances across the terminals of the supply, b) total current supplied by the source and c) power delivered to 16 ohm resistor in the circuit shown in the figure shown below. 	Apply	1
6	Find the power consumed by each resistor 	Understand	1
7	Determine the current through 800 ohm resistor in the network shown in figure	Understand	3

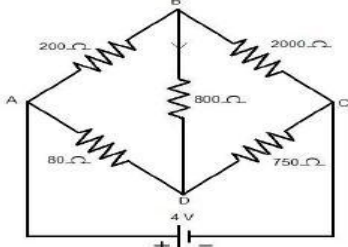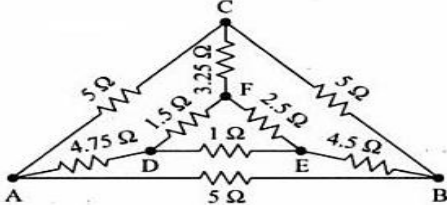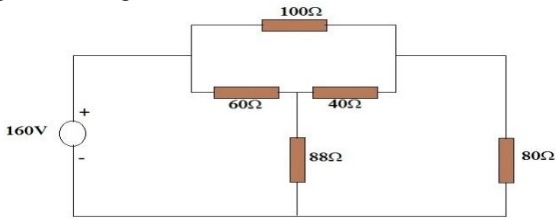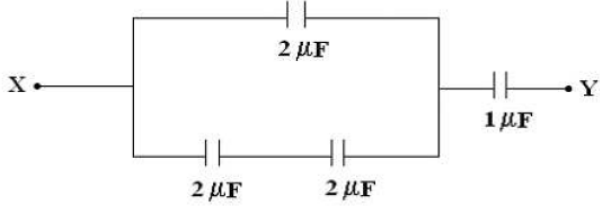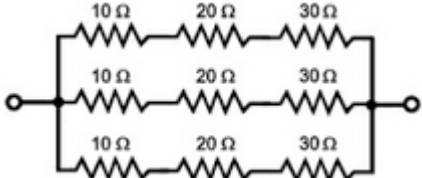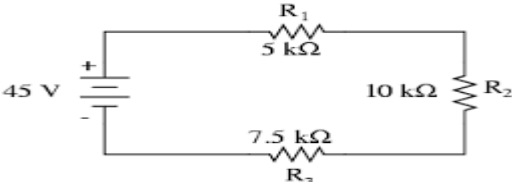S. No	Question	Blooms Taxonomy Level	Course Outcome
			
8	<p>Find the resistance between the A and B by using star delta conversion</p> 	Understand	3
9	<p>Determine the resistance between the terminals A&B and hence find the current through the voltage source</p> 	Apply	1
10	<p>Find the equivalent capacitance of the combination shown figure below across X and Y.</p> 	Understand	3
11	<p>An inductor having capacitance of $5\mu\text{F}$ is charged to a voltage of 10V. Calculate the stored energy in joules</p>	Apply	1
12	<p>Find the equivalent resistance between the terminals</p> 	Apply	1
13	<p>Find power across each element in the given circuit</p> 	Apply	3

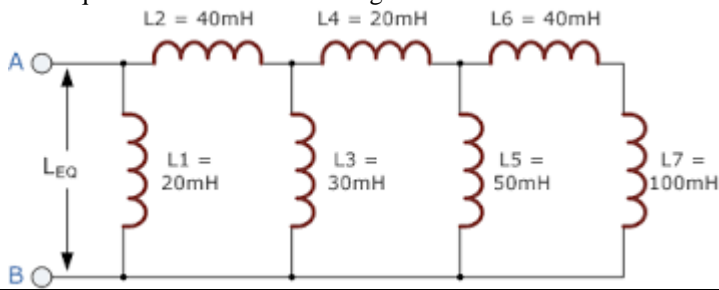S. No	Question	Blooms Taxonomy Level	Course Outcome
14	Find equivalent inductance in the given circuit 	Apply	1
15	If three resistors 10Ω, 20Ω and 40Ω are connected in parallel find equivalent resistance.	Apply	3

UNIT – II
DC Machines

SHORT ANSWER TYPE QUESTIONS

1	State Fleming's Right Hand Rule.	Remember	4
2	What is the basic principle of a dc generator?	Remember	4
3	What are the basic parts of a dc generator?	Remember	4
4	What are the different types of dc generators?	Remember	4
5	What is back emf in d.c. motor?.	Remember	4
6	Draw the circuit diagram of a Dc series motor	Understand	4
7	What are the applications of DC motors?	Remember	4
8	What is the function of commutator?	Remember	4
9	Draw the open circuit characteristics of dc separately excited generator	Remember	4
10	What do you mean by residual EMF in a generator?	Remember	4
11	State faraday's laws of electro magnetic induction.	Remember	4
12	State flemings left hand rule	Remember	4
13	State flemings right hand rule	Evaluate	4
14	What are the functions of yoke?	Remember	4
15	What is the function of brushe in dc motors?	Remember	4

LONG ANSWER QUESTIONS

1	Describe the construction of dc machine with neat diagram?	Apply	4
2	Discuss the principle of operation of DC generator?	Evaluate	5
3	Derive the equation for induced EMF of a DC machine.	Apply	4
4	Explain the principle of operation of DC Motor	Apply	5
5	Give the classification of DC generator and explain with neat diagrams	Understand	5
6	Derive the torque equation of DC motor.	Apply	4
7	Discuss different types of characteristics of different types of generators	Understand	5
8	Explain three point starter for D.C. Shunt motor	Understand	4
9	Differentiate between self-excited and separately excited d.c. machines	Evaluate	5
10	Discuss Different types of characteristics of DC motors	Apply	5
11	Explain the windings used in de machines	Apply	5
12	Explain the open circuit characteristics of dc shunt generator	Understand	4
13	What are the applications of dc motors and generators?	Understand	4
14	Give the classification of DC motors and explain with neat diagrams	Evaluate	4
15	Explain lap winding in dc machines with neat sketch	Apply	4

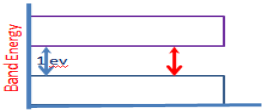

ANALYTICAL QUESTIONS

1	Calculate the e.m.f by 4 pole wave wound generator having 65 slots with 12 conductors per slot when driven at 1200 rpm the flux per pole is 0.02 wb	Remember	4
2	A 6 pole lap wound dc generator has 600 conductors on its armature flux per	Understand	4

S. No	Question	Blooms Taxonomy Level	Course Outcome
	pole is 0.02 wb. Calculate i. The speed at which the generator must be run to generate 300v. ii. What would be the speed if the generated were wave wound		
3	An 8-pole, lap wound armature rotated at 350 rpm is required to generate 260v. The useful flux per pole is 0.05 wb if the armature has 120 slots, calculate the number of conductors per slot.	Remember	4
4	A 440v Dc shunt generator has $R_a=0.25$ ohms and $R_{sh}= 220$ ohms while delivering a load current of 50 amps, it has a terminal voltage of 440v determine the generated e.m.f and power developed?	Understand	5
5	A Dc series generator has armature resistance of 0.5 ohms and series field resistance of 0.03 ohms it drives a load of 50 amps. if it has 6 turns/coil and total 540 coils on the armature and is driven at 1500 rpm calculate the terminal voltage at the load. Assume 4-poles, lap type winding, flux pole as 2 mwb and total brush drop as 2v.	Apply	5
6	A 4-pole lap wound dc shunt generator has a useful flux per pole of 0.07 wb. The armature winding consists of 220 turns, each of 0.04 ohms resistance. Calculate the terminal voltage when running at 900 rpm if the armature current is 50 amps.	Remember	5
7	A shunt generator supplies 96 amps at a terminal voltage of 200 volts the armature and shunt field resistances are 0.1 ohms and 50 ohms respectively. The iron and frictional losses are 2500 watts. Find i) E.m.f generated ii) copper losses	Apply	4
8	A 250 v shunt motor takes a total current of 20 amps the shunt field and armature resistances are 200 ohms and 0.3 ohms respectively determine i) Value of back E.m.f ii) gross mechanical power in the armature	Remember	4
9	Calculate the value of torque established by the armature of a 4pole motor having 774 conductors, two paths in parallel, 24 mwb flux per pole , when the total armature current is 50 amps.	Apply	4
10	A 230v dc shunt motor takes a current of 40 amps and runs at 1100 rpm if armature and shunt field resistances are 0.25 ohms and 230 ohms respectively. Find the torque developed by armature	Apply	5
11	Calculate the e.m.f by 6 pole wave wound generator having 75 slots with 6 conductors per slot when driven at 1200 rpm the flux per pole is 0.03 wb	Remember	4
12	An 8-pole, lap wound armature rotated at 450 rpm is required to generate 250v. The useful flux per pole is 0.06 wb if the armature has 100 slots, calculate the number of conductors per slot.	Apply	4
13	A 220v Dc shunt generator has $R_a=0.35$ ohms and $R_{sh}= 200$ ohms while delivering a load current of 50 amps, it has a terminal voltage of 220v determine the generated e.m.f and power developed?	Remember	4
14	A 6-pole lap wound dc shunt generator has a useful flux per pole of 0.06 wb. The armature winding consists of 220 turns, each of 0.06 ohms resistance. Calculate the terminal voltage when running at 1000 rpm if the armature current is 40 amps.	Apply	4
15	A 220v dc shunt motor takes a current of 20 amps and runs at 1200 rpm if armature and shunt field resistances are 0.35 ohms and 200 ohms respectively. Find the torque developed by armature	Remember	4
UNIT – III			
AC MACHINES			
SHORT ANSWER TYPE QUESTIONS			
1	Mention the difference between core and shell type transformers	Understand	5
2	Give the emf equation of a transformer and define each term	Understand	6
3	Define voltage regulation of a transformer.	Remember	6

S. No	Question	Blooms Taxonomy Level	Course Outcome
4	Define transformation ratio	Remember	6
5	State two types of induction motors	Understand	5
6	Derive maximum torque condition under running condition.	Remember	6
7	Draw torque slip characteristics of three phase induction motor.	Understand	6
8	Name the types of Alternator based on their rotor construction.	Remember	7
9	Define the term voltage regulation of Alternator	Understand	7
10	How synchronous impedance is calculated from OCC and SCC?	Understand	7
11	Define efficiency of a transformer	Remember	6
12	What is the function of transformer?	Understand	6
13	Classify the losses present in transformer	Remember	5
14	What is the expression for eddy current losses and define each term	Understand	5
15	What is the expression for hysteresis losses and define each term	Remember	6
16	What is the emf equation of alternator?	Remember	6
LONG ANSWER QUESTIONS			
1	Describe the construction details of single phase transformer.	Create	5
2	Explain the principle of operation of transformer.	Evaluate	6
3	Derive the EMF equation of a transformer.	Evaluate	6
4	Discuss about different types of losses in transformer.	Analyze	6
5	Describe the method to perform OC and SC test on a transformer.	Evaluate	7
6	Discuss the principle and operation of three phase induction motor.	Evaluate	7
7	Discuss about Different types of Induction motors depends upon the rotor construction.	Evaluate	7
8	Derive maximum torque condition under running and standstill condition of induction motor.	Remember	6
9	Describe the construction of alternator depends upon rotor construction.	Understand	6
10	Discuss about synchronous impedance method to find regulation of an alternator.	Understand	6
11	Draw the torque slip characteristics of induction motor.	Evaluate	5
12	Explain the working principle of alternator	Remember	5
13	Describe the construction details of induction motor	Understand	5
14	Describe the construction details of alternator	Understand	5
15	Derive the torque equation in induction motors	Understand	5
ANALYTICAL QUESTIONS			
1	A transformer supplied a load of 32A at 415V. If the primary voltage is 3320V, find the following: (a) Secondary volt ampere (b) Primary current (c) Primary volt ampere. Neglect losses and magnetizing current	Understand	5
2	A 125 KVA transformer having primary voltage of 2000V at 50 Hz has 182 primary and 40 secondary turns. Neglecting losses, calculate i) The full load primary and secondary currents. ii) The no-load secondary induced emf. iii) Maximum flux in the core	Evaluate	6
3	A single phase transformer has 50 primary and 1000 secondary turns. Net cross sectional area of the core is 500 cm ² . If the primary winding is connected to 50 Hz supply at 400 V, Calculate the value of Maximum flux density on core and the emf induced in the secondary.	Evaluate	6
4	A transformer with 40 turns on the high voltage winding is used to step down the voltage from 240V to 120V. Find the number of turns in the low voltage winding. Open circuit and short circuit tests on a 5 KVA, 220/400V, 50 Hz, single phase transformer gave the following results: OC Test: 220V, 2A, 100W (lv side) SC Test: 40V, 11.4A, 200W (hv side)	Evaluate	7

S. No	Question	Blooms Taxonomy Level	Course Outcome
	Obtain the equivalent circuit		
5	The efficiency of a 400 kva ,single phase transformer is 98.77% when delivering full-load at 0.8 pf lagging and 99.13% at half load at unity power factor calculate i) iron losses and full load copper losses	Apply	5
6	A 440/110 v transformer has a primary resistance of 0.03 ohms and secondary resistance of 0.02 ohms if iron losses at normal input is 150 watts determine the secondary current at which maximum efficiency will occur and the value of this maximum efficiency at a unity power factor load.	Apply	6
7	A 4 – pole 3 phase star connected alternator armature has 12 slots with 24 conductors per slot and the flux per pole is 0.1 Wb. Calculate line emf generated at 50 Hz. Calculate the distribution factor of a 36 slot, 4 pole single layer winding of an alternator.	Apply	7
8	A part of an alternator winding consists of six coils in series, each coil having an emf of 10V rms Induced in it. The coils are placed in successive slots and between each slot and the next; there is an Electrical phase displacement of 30 degrees. Calculate the emf of the six coils in series	Understand	6
9	In case of an 8-pole induction motor the supply frequency was 50 Hz and the shaft speed was 735 rpm. Compute i) Synchronous speed ii) Slip speed per unit slip iii)Percentage slip	Apply	6
10	A 6-pole, 50Hz squirrel cage induction motor runs on load at a shaft speed of 970 rpm. Calculate i) Percentage slip ii) The frequency of the induced current in the rotor	Apply	6
11	A single phase transformer has 50 primary and 1000 secondary turns. Net cross sectional area of the core is 400 cm ² . If the primary winding is connected to 50 Hz supply at 400 V, Calculate the value of Maximum flux density on core and the emf induced in the secondary.	Understand	6
12	A 125 KVA transformer having primary voltage of 2200V at 50 Hz has 180 primary and 40 secondary turns. Neglecting losses, calculate i) The full load primary and secondary currents. ii) The no-load secondary induced emf. iii) Maximum flux in the core	Apply	5
13	A transformer supplied a load of 20A at 230V. If the primary voltage is 2300V,find the following: (a) Secondary volt ampere (b) Primary current (c) Primary volt ampere. Neglect losses and magnetizing current	Apply	5
14	In case of an 6-pole induction motor the supply frequency was 50 Hz and the shaft speed was 925 rpm. Compute i) Synchronous speed ii) Slip speed per unit slip iii)Percentage slip	Apply	6
15	A 4-pole, 50Hz squirrel cage induction motor runs on load at a shaft speed of 1440 rpm. Calculate i) Percentage slip ii) The frequency of the induced current in the rotor	Apply	6
UNIT-IV			
DIODES AND TRANSISTORS			
SHORT ANSWER TYPE QUESTIONS			
1	Explain avalanche breakdown?	Understand	7
2	Differentiate intrinsic and extrinsic semiconductors?	Remember	7
3	Define static and dynamic resistance?	Remember	7

S. No	Question	Blooms Taxonomy Level	Course Outcome
4	Name the three energy bands in Solids materials 	Remember	8
5	Explain Active region?	Understand	8
6	Express importance of Cut in voltage?	Remember	8
7	Define transformer utility factor?	Remember	9
8	Design a circuit for transistor as a switch?	Synthesize	9
9	Define saturation region?	Remember	9
10	Identify the Anode and cathode in the given Diode and draw a circuit diagram for positive biasing. 	Remember	7
11	Derive relationship among α , β ?	Remember	7
12	Explain majority and minority carriers in a semiconductor?	Understand	7
13	Define efficiency?	Remember	8
14	Define ripple factor?	Remember	8
15	Define peak inverse voltage?	Remember	8
16	Define form factor?	Remember	8

LONG ANSWER QUESTIONS

1	Explain the theory of PN junction in semiconductors and explain how it acts as diode?	Understand	7
2	Explain different biasing conditions of the PN junction crystal diode	Understand	8
3	Discuss V-I characteristics of a silicon PN junction crystal diode and Analyze the significance of the knee voltage?	Apply	7
4	Analyze the effect of temperature on the volt – ampere characteristics of a diode	Apply	8
5	Zener diode works in reverse biased condition. How the Zener diode and it's breakdown mechanism work as regulator?	Evaluate	7
6	Describe the Diode current equation.	Apply	8
7	What is the importance of a filter in voltage rectification process and describe different types of filters.	Understand	8
8	Define rectifier? Describe all parameters for Half wave rectifier?	Remember	8
9	Define rectifier? Describe all parameters for Centre tapped full wave rectifier?	Understand	8
10	Define rectifier? Describe all parameters for bridge rectifier?	Remember	8
11	Discuss the difference between Half waves; centre tapped full wave and bridge rectifiers.	Apply	7
12	Explain the operation of SCR and its characteristics?	Understand	7
13	Explain the term α and β current gains and their relationship for N-P-N transistor?	Understand	7
14	Explain the operation of NPN and PNP transistor?	Understand	7
15	Illustrate with a diagram, how the BJT transistor acts as an amplifier?	Understand	7

ANALYTICAL QUESTIONS

1	A diode operating at 300 ⁰ K at a forward voltage of 0.4v carries a current of 10mA. when voltage is changed to 0.42V the current becomes twice. Calculate the value of reverse saturation current and efficiency for the diode	Apply	7
2	A PN junction diode as are verse saturation current of 30 μ A at a temperature of 125 ⁰ C. at same temperature, find the dynamic resistance for 0.2V bias in forward and reverse direction.	Apply	7
3	Determine the values of forward current in the case of PN junction diode, with $I_{0} = 10\mu A$ $V_f = 0.8V$ at $T = 300^0K$ Assume Si diode.	Apply	7

S. No	Question	Blooms Taxonomy Level	Course Outcome
4	In a full wave rectifier using an LC filter $L = 10H$, $C = 100\mu f$ and $R_L = 500\Omega$ calculate I_{dc} , V_{dc} , ripple factor for an input of $V_i = 30\sin(100\pi t)V$	Understand	7
5	A 230V, 60Hz voltage is applied to the primary of a 5 : 1 step down, center tapped transformer used in a full wave rectifier having a load of 900Ω . with diode resistance and secondary coil resistance together has a resistance of 100Ω determine i. DC voltage across the load ii. DC current flowing through the load iii. DC power delivered to the load iv. PIV across each diode v. Ripple voltage and its frequency	Apply	8
6	A full wave rectifier supplies a load requiring a 300V at 200mA. Calculate the transformer secondary voltage for i. A capacitor input filter using a capacitor of $10\mu f$ ii. A choke input filter using a choke of 10H and capacitance of $10\mu f$ neglect the resistance of choke.	Understand	8
7	Calculate the values of I_c and I_e for a transistor with $\alpha_{dc} = 0.99$ and $I_{cbo} = 5\mu A$, I_b is measured as $20\mu A$.	Understand	8
8	The reverse saturation current in a transistor is $8\mu A$ if the transistor common base current gain is 0.979; calculate collector and emitter current for $40\mu A$ base current.	Understand	7
9	A transistor operating in CB configuration has $I_c = 2.98mA$, $I_e = 3mA$, $I_{c0} = 0.01mA$, what current will flow in the collector circuit of this transistor when connected in CE configuration with a base current of $30\mu A$.	Evaluate	7
10	Given an npn transistor for which $\alpha = 0.98$, $I_{c0} = 2\mu A$. And $I_{ce0} = 1.6\mu A$. a common emitter connection is used and $V_{cc} = 12V$ and $R_L = 4K\Omega$ what is the minimum base current required in order that transistor enter into saturation region.	Understand	7
11	The brightness of a 100 W, 110 V lamps is to be varied by controlling firing angle of SCR full wave circuit. The RMS value of A.C. voltage appearing across each SCR is 110 V. Find the RMS voltage and current in the lamp at firing angle of 60° .	Analyze	8

UNIT-V
CATHODE RAY OSCILLOSCOPE
SHORT ANSWER TYPE QUESTIONS

1	Explain the function of deflection plates?	Understand	9
2	Explain is the function of accelerating anode?	Understand	10
3	Explain the function of vertical plates in CRT?	Understand	10
4	Describe the function of horizontal plates?	Remember	10
5	Define Fluorescence?	Remember	9
6	Explain the Principle of dual beam oscilloscope?	Remember	9
7	Explain the principle of sampling oscilloscope?	Understand	9
8	Mention the two modes of operation in dual trace oscilloscope	Remember	10
9	List the Disadvantages of storage cathode ray tube	Understand	10
10	Define Electric Field?	Remember	9
11	Define Magnetic Field?	Remember	9
12	Describe CRT?	Understand	9
13	Formulate Force between two charges?	Remember	9
14	Applications of Cathode Ray Oscilloscope	Understand	9
15	What are the advantages of CRT?	Understand	9

LONG ANSWER QUESTIONS

S. No	Question	Blooms Taxonomy Level	Course Outcome
1	Give the construction of a Cathode Ray tube using electrostatic focusing and deflection systems and describe the functions of various constituents.	Understand	9
2	Give the construction of a Cathode Ray tube using magnetic focusing and deflection systems and describe the functions of various constituents.	Create	10
3	Write the principle of CRT? Explain the different types of CROs?	Understand	10
4	Explain the Block diagram of CRO with neat sketch?	Create	10
5	Describe functional block diagram of CRT?	Understand	10
6	Explain the applications of CRO?	Create	9
7	Explain the electron gun construction and working?	Understand	9
8	How the magnetic deflection system works in CRT?	Apply	9
9	Explain the Electrostatic deflection system in CRT?	Understand	10
10	Differentiate Electrostatic and magnetic deflection systems?	Evaluate	10
11	Describe the voltage, current and frequency measurements using CROs.	Synthesize	10
ANALYTICAL QUESTIONS			
1	An electron moving with initial velocity of 10^6 m/s enters an uniform magnetic field at an angle of 30° with it. Calculate the magnetic flux density required in order that the radius of helical path be 1m. Also, calculate the time taken by the electron for one revolution and the pitch of the helix	Apply	9
2	An electrostatic cathode ray tube has a final anode voltage of 400 V. The deflection plates are 2 cm long and 1 cm apart. The screen is at a distance of 10 cm from the centre of the plates. A voltage of 20 V is applied to the deflection plates. Calculate i) Velocity of electron on reaching the field, ii) Acceleration due to deflection field, iii) Deflection produced on the screen and iv) Deflection sensitivity.	Evaluate	9
3	In a CRT, the distance of the screen from the centre of the magnetic field is 22 cm, the deflecting magnetic field of flux density 2×10^{-4} Wb/m ² extends for a length of 2.5 cm along the tube axis. The final anode voltage is 1250 V. Calculate the deflection of the spot in cm.	Evaluate	10

Prepared by: Mr. A Sathishkumar, Assistant Professor

HOD, CIVIL ENGINEERING